

# **CSC 252: Computer Organization**

## **Spring 2020: Lecture 12**

### **Processor Architecture**

Substitute Instructor: Sandhya Dwarkadas

Department of Computer Science  
University of Rochester

# Announcement

- Programming assignment 3 due soon
  - Details:  
<https://www.cs.rochester.edu/courses/252/spring2020/labs/assignment3.html>
  - Due on **Feb. 28**, 11:59 PM
  - You (may still) have 3 slip days

17	18	19	20	21	22
24	25 Today	26	27	28 Due	29

# Announcement

- Grades for lab2 are posted.
- If you think there are some problems
  - Take a deep breath
  - Tell yourself that the teaching staff like you, not the opposite
  - Email/go to Shuang or Sudhanshu's office hours and explain to them why you should get more points, and they will fix it for you

# Announcement

- Programming assignment 3 is in x86 assembly language. Seek help from TAs.
- TAs are best positioned to answer your questions about programming assignments!!!
- Programming assignments do NOT repeat the lecture materials. They ask you to synthesize what you have learned from the lectures and work out something new.

# Overview of Logic Design


## Fundamental Hardware Requirements

- **Communication**
  - How to get values from one place to another
- **Computation**
- **Storage**

## Bits are Our Friends

- **Everything expressed in terms of values 0 and 1**
- **Communication**
  - Low or high voltage on wire
- **Computation**
  - Compute Boolean functions
- **Storage**
  - Store bits of information


# Combinational Circuits

 

## Acyclic Network of Logic Gates

- Continuously responds to changes on primary inputs
- Primary outputs become (after some delay) Boolean functions of primary inputs

# Arithmetic Logic Unit

 

- **Combinational logic**
  - Continuously responding to inputs
- **Control signal selects function computed**
  - Corresponding to 4 arithmetic/logical operations in Y86
- **Also computes values for condition codes**


# Sequential Logic: Memory and Control

## Sequential:

- Output depends on the *current* input values and the *previous* sequence of input values.
- Are **Cyclic**:
  - Output of a gate feeds its input at some future time.
- **Memory**:
  - Remember results of previous operations
  - Use them as inputs.
- Example of use:
  - Build registers and memory units.




# Registers

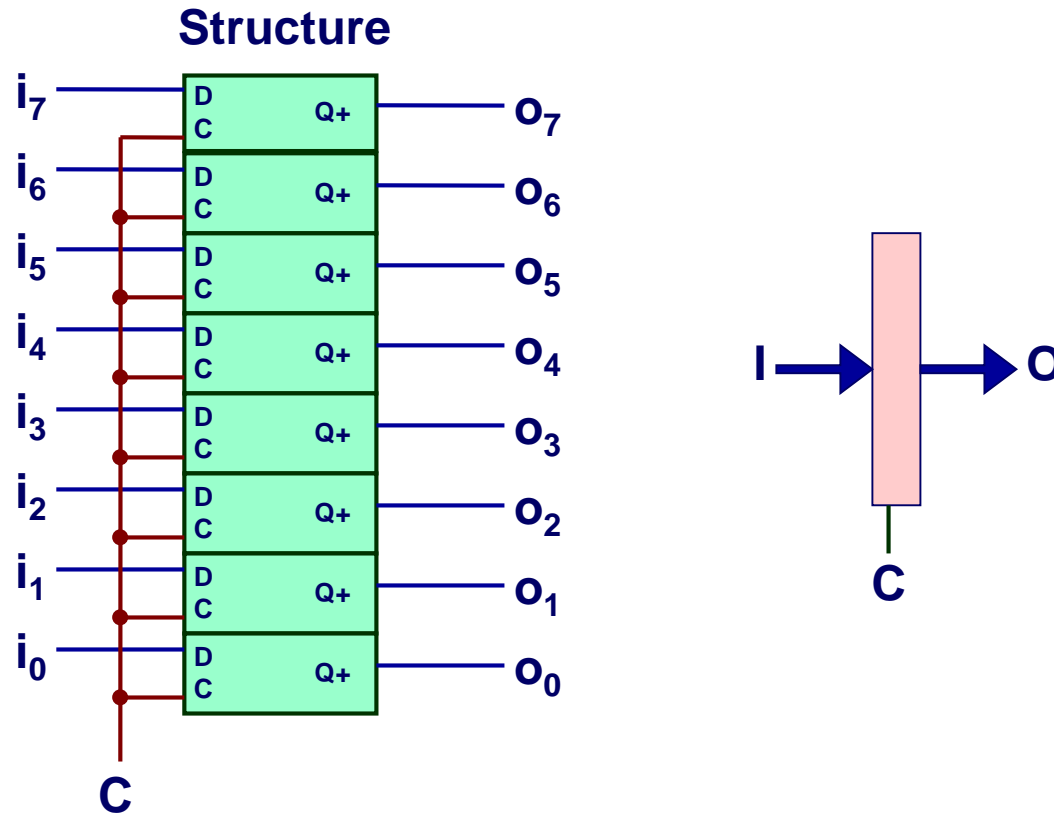

- Stores several bits of data
- Collection of edge-triggered latches (D Flip-flops)
- Loads input on rising edge of the C signal


# Register Operation

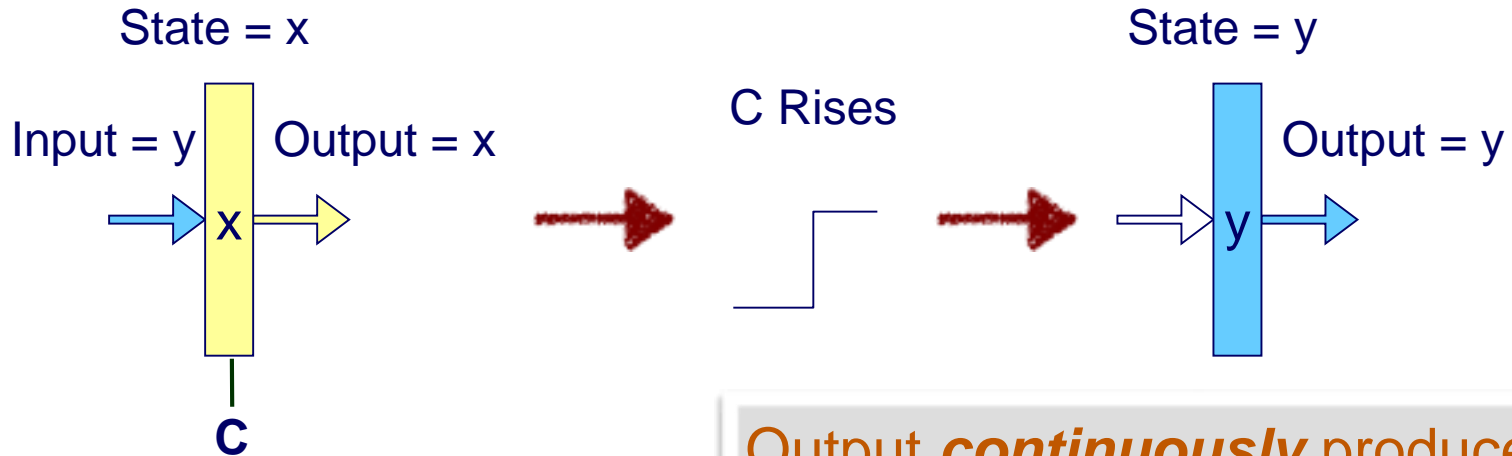


Output **continuously** produces  $y$  after the rising edge unless you cut off power.

- Stores data bits
- For most of time acts as barrier between input and output
- As  $C$  rises, loads input
- So you'd better compute the input before the  $C$  signal rises if you want to store the input data to the register

# Clock Signal

 


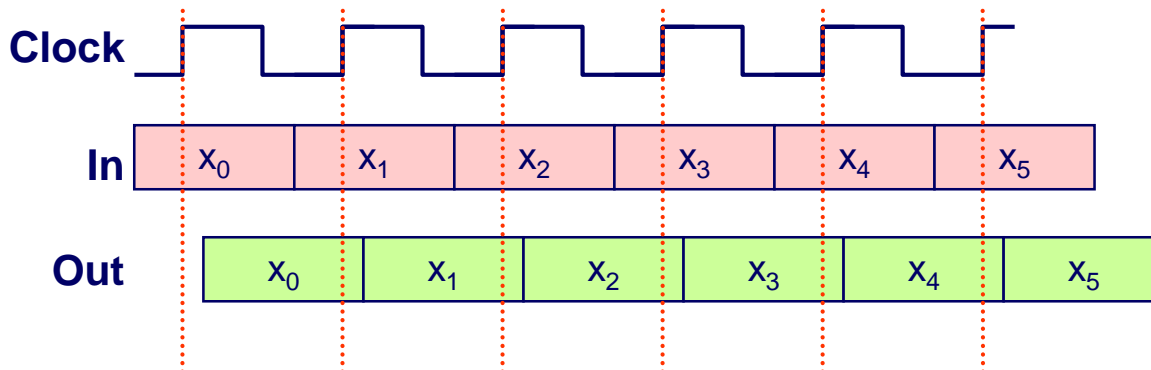- A special C: periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer


 
# Clock Signal


- Cycle time of a clock signal: the time duration between two rising edges.
- Frequency of a clock signal: how many rising (falling) edges in 1 second.
- 1 GHz CPU means the clock frequency is 1 GHz
  - The cycle time is  $1/10^9 = 1 \text{ ns}$



# Register File


- A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out
- To write: give a register file ID, a new value, overwrite the old value
- How do we build a register file out of individual registers??

## Register File

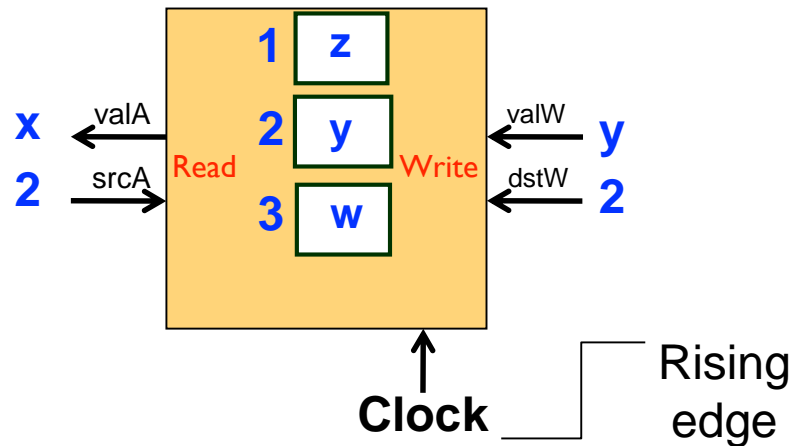

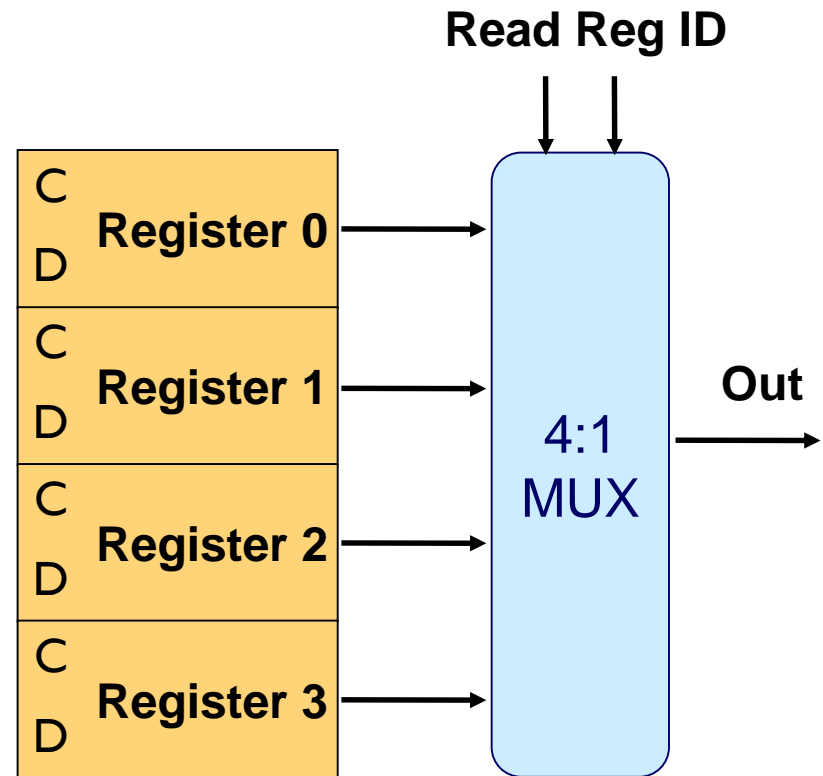
# Register File Read

- Continuously read a register independent of the clock signal


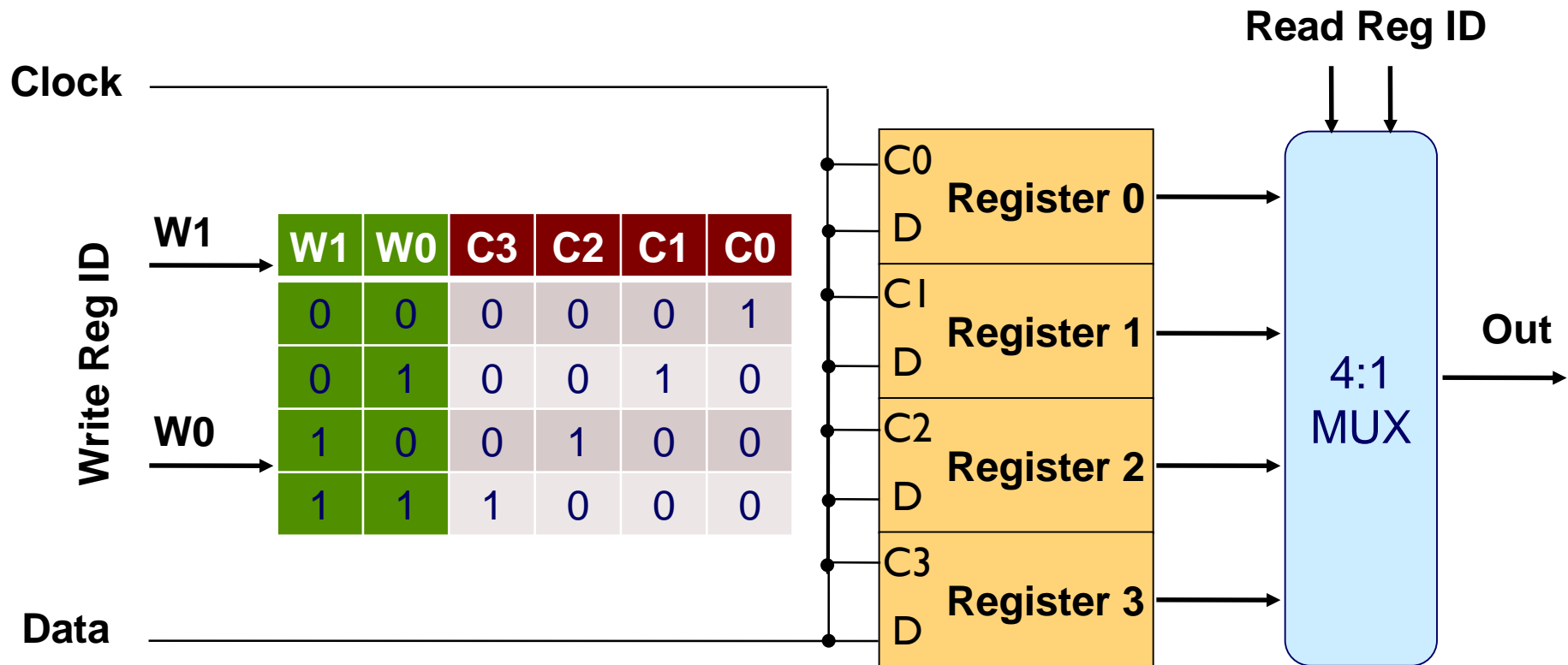
# Register File Write

- Only write to a specific register when the clock rises. How??



# Decoder

W1	W0	C3	C2	C1	C0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

W0 \_

W1 \_

\_C0

\_C1

\_C2

\_C3

$$C0 = !W1 \ \& \ !W0$$


$$C1 = !W1 \ \& \ W0$$

$$C2 = W1 \ \& \ !W0$$

$$C3 = W1 \ \& \ W0$$




# Register File Write

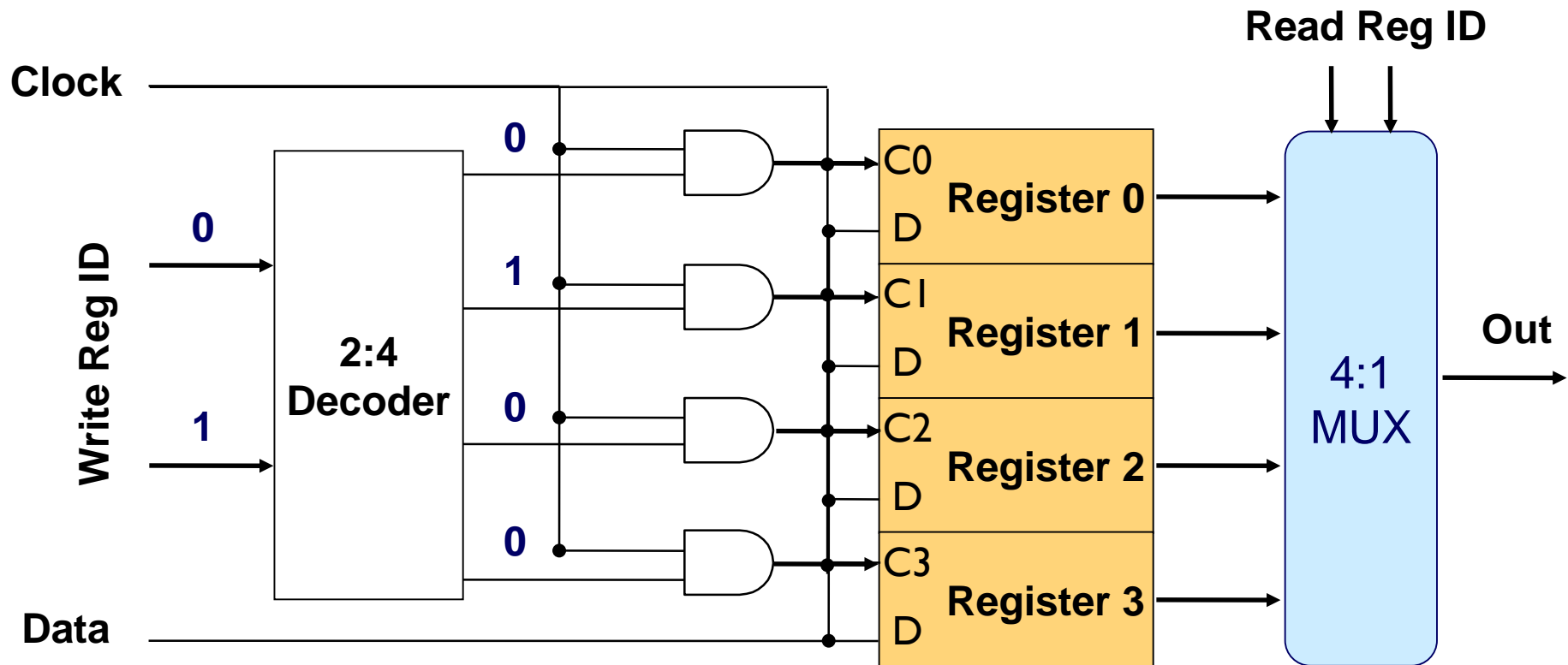

- This implementation can read 1 register and write 1 register at the same time: 1 read port and 1 write port
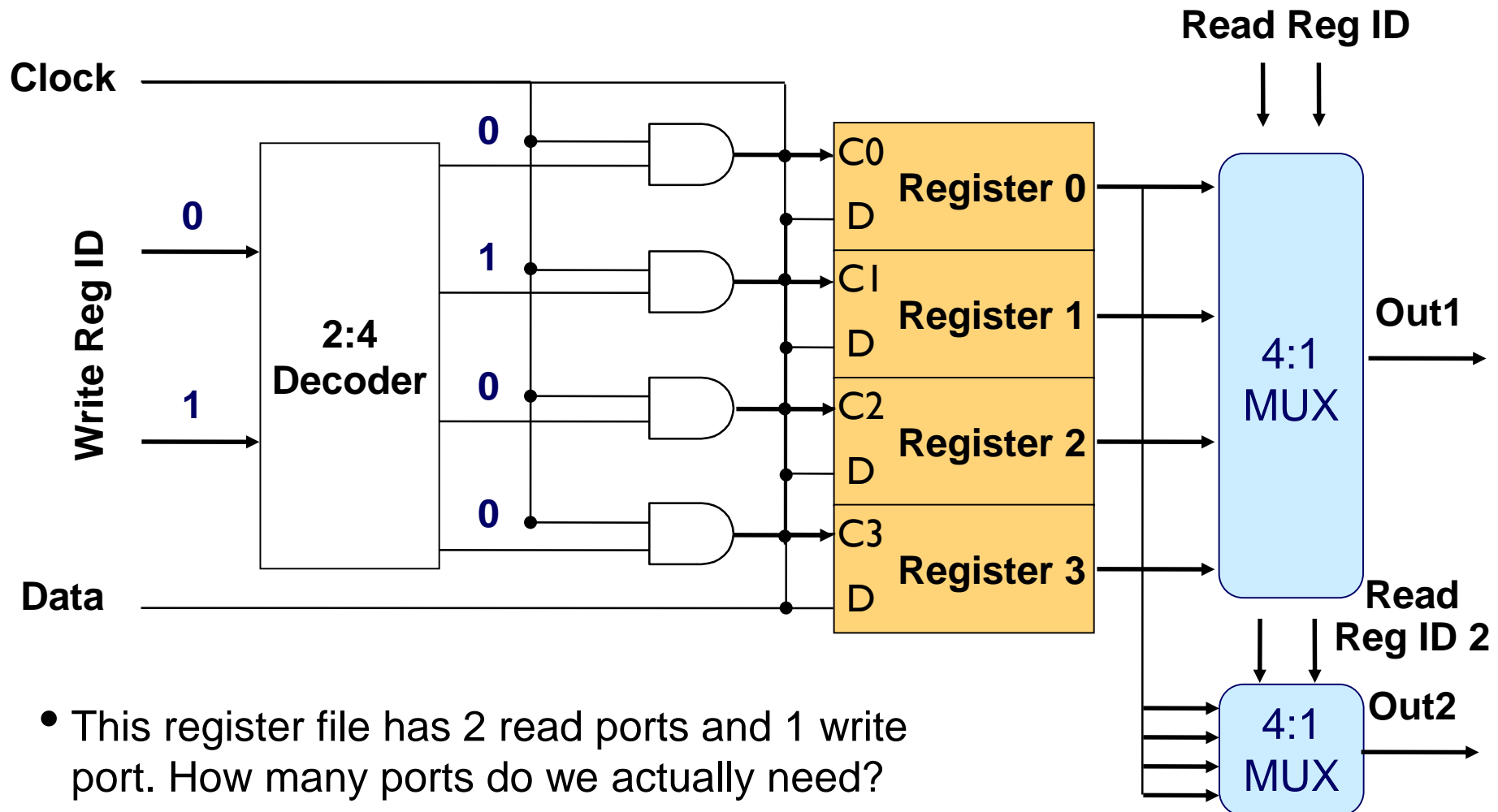
# Multi-Port Register File


- What if we want to read multiple registers at the same time?




- This register file has 2 read ports and 1 write port. How many ports do we actually need?
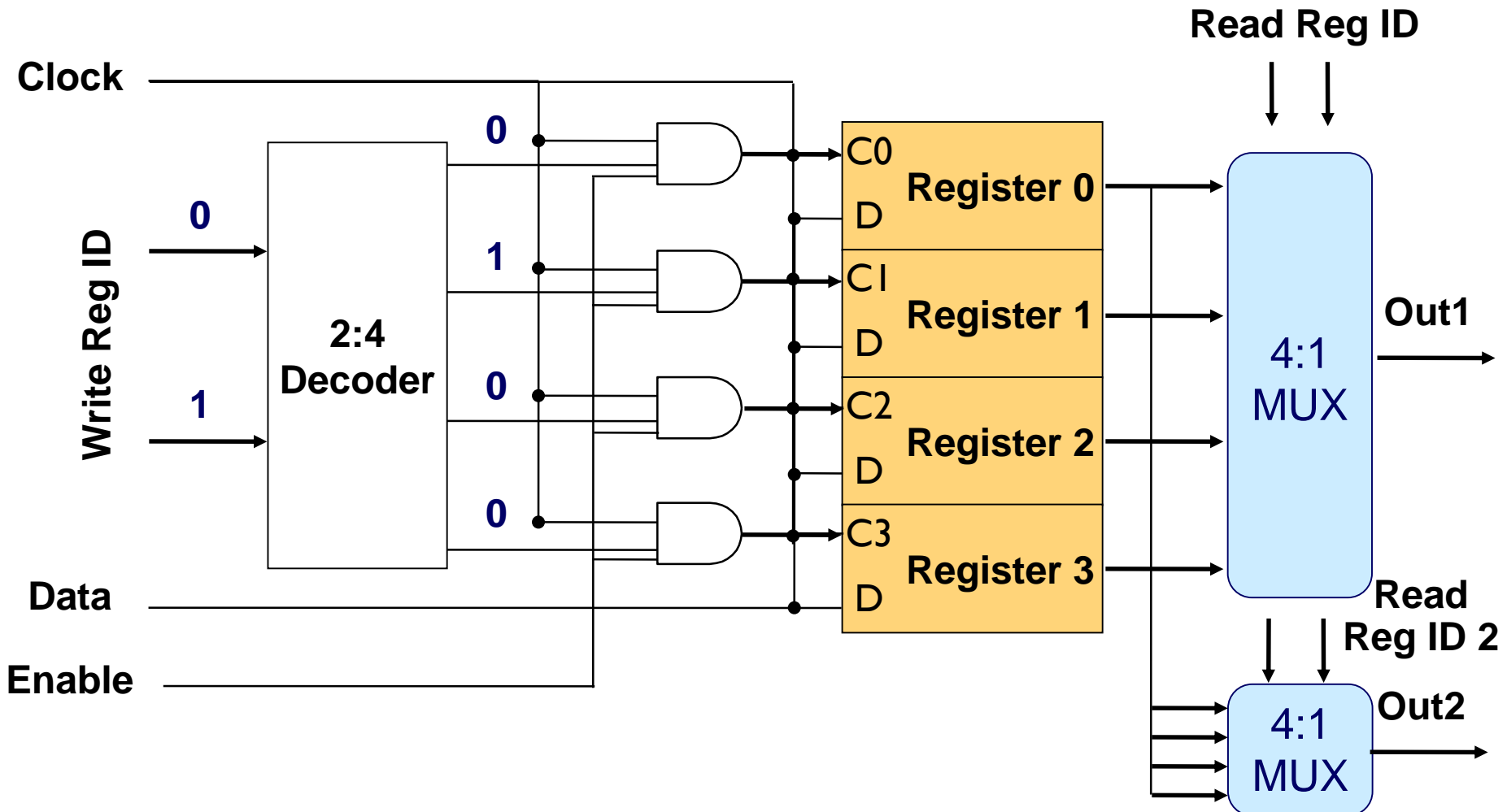
# Multi-Port Register File

- Is this correct? What if we don't want to write anything?




# Register File

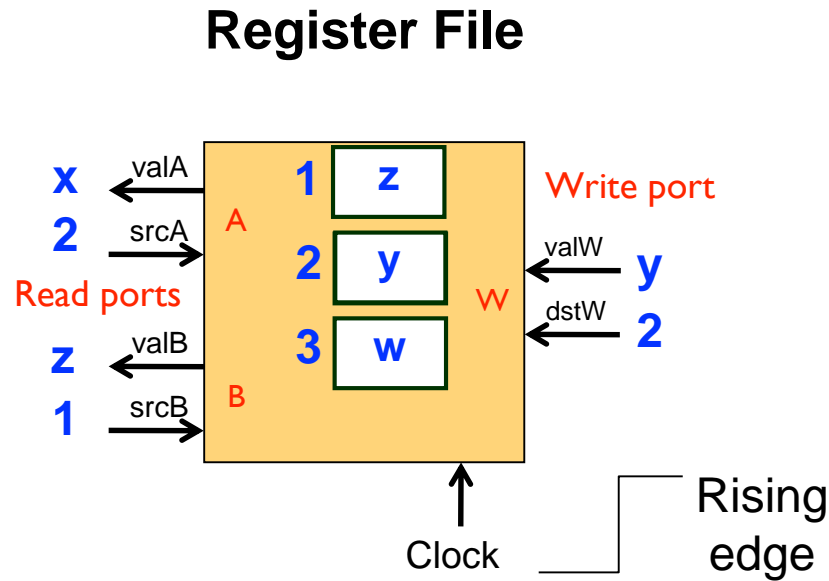


- Stores multiple registers of data
  - Address input specifies which register to read or write
- Register file is a form of **Random-Access Memory (RAM)**
- Multiple Ports: Can read and/or write multiple words in one cycle. Each port has separate address and data input/output

# State Machine Example

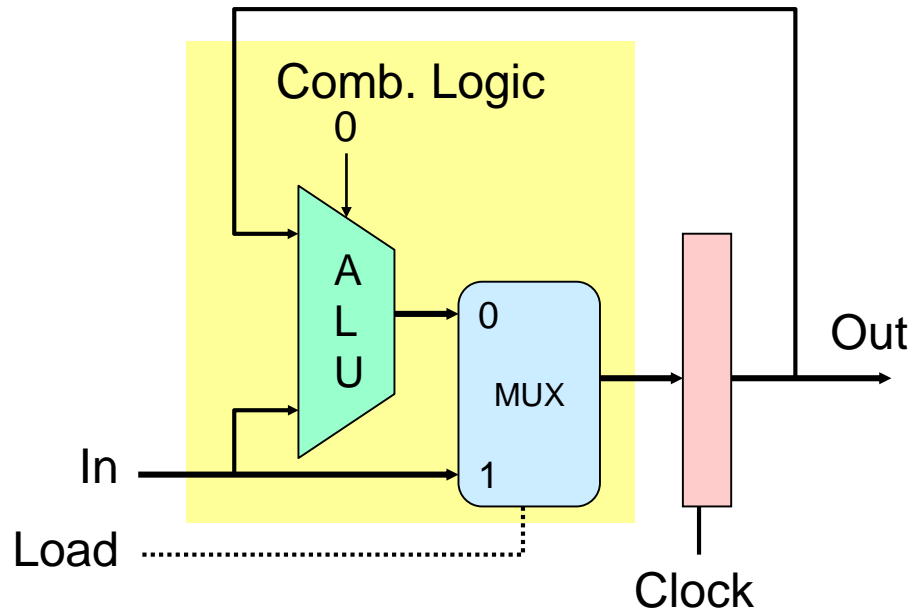


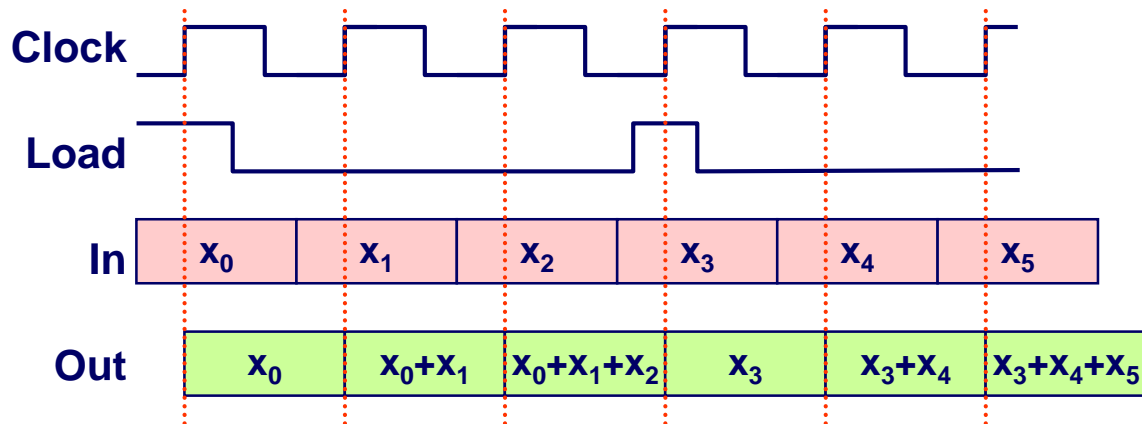- Accumulator circuit
- Load or accumulate on each cycle


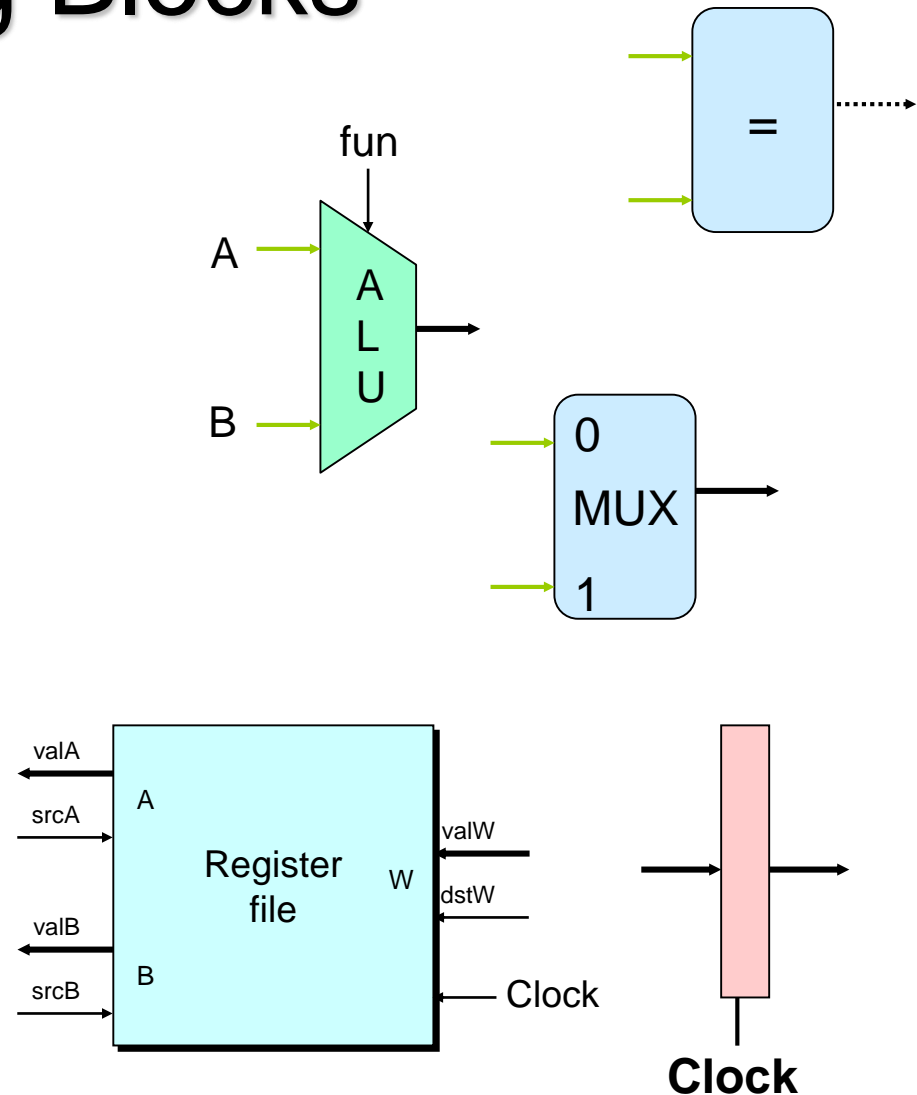
# Building Blocks

- Combinational Logic
  - Compute Boolean functions of inputs
  - Continuously respond to input changes
  - Operate on data and implement control
- Storage Elements
  - Store bits
  - Addressable memories
  - Non-addressable registers
  - Loaded only as clock rises



# Arithmetic and Logical Operations

Instruction Code

Function Code


Add

`addq rA, rB`




Subtract (rA from rB)

`subq rA, rB`

 


And

`andq rA, rB`

 

Exclusive-Or


`xorq rA, rB`

 

- Refer to generically as “OPq”
- Encodings differ only by “function code”
  - Low-order 4 bits in first instruction word
- Set condition codes as side effect
 
# Executing an ADD instruction

- How does the processor execute `addq %rax,%rsi`
- The binary encoding is `60 06`






# Executing an ADD instruction

- How does the processor execute `addq %rax,%rsi`
- The binary encoding is `60 06`

**Instruction Code**  
**Add**


**Function Code**

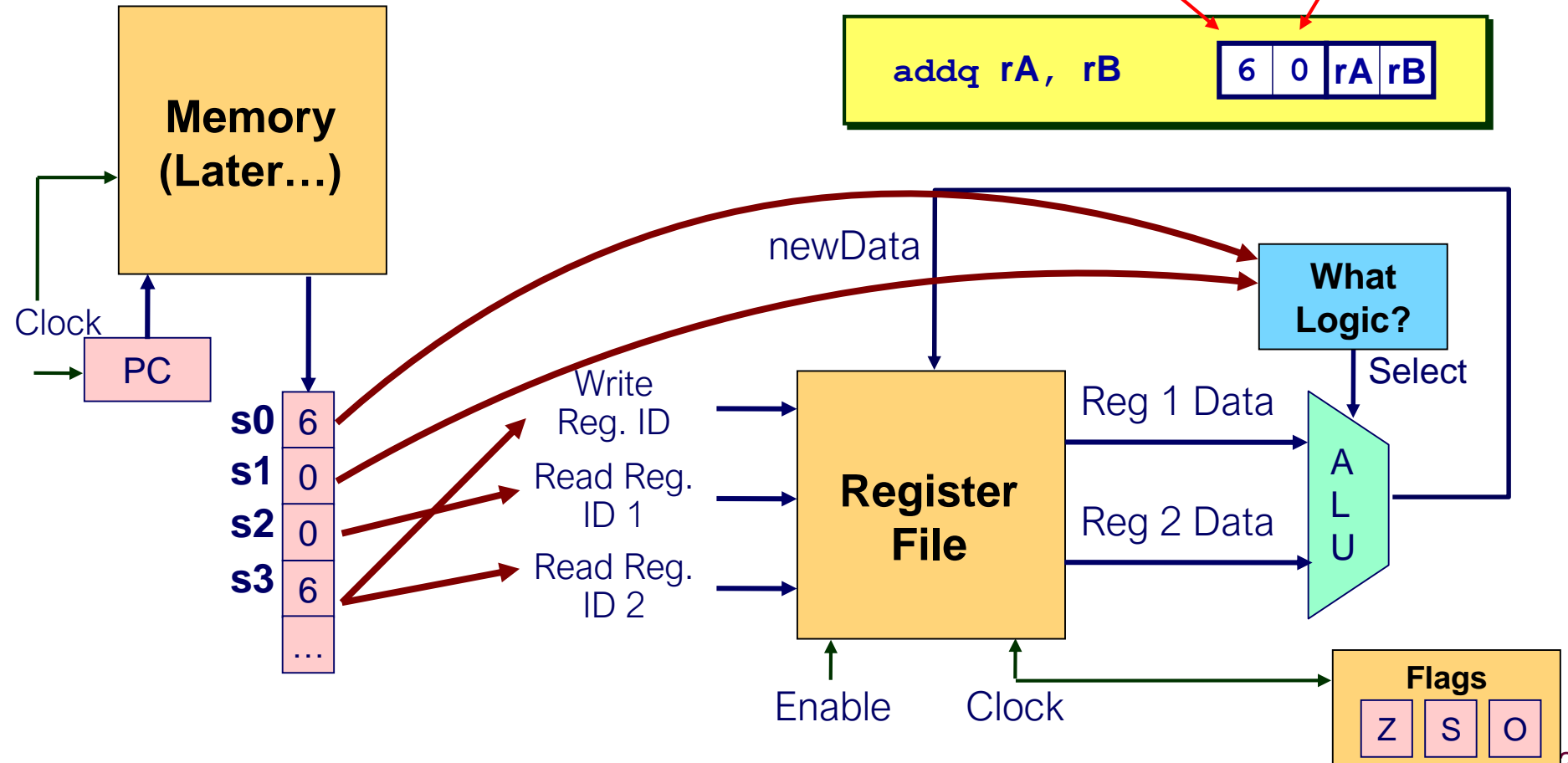

# Executing an ADD instruction


- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;
- Logic 3: if (s0 == 6) nPC = oPC + 2;
- How about Logic 4?

How do these logics get implemented?

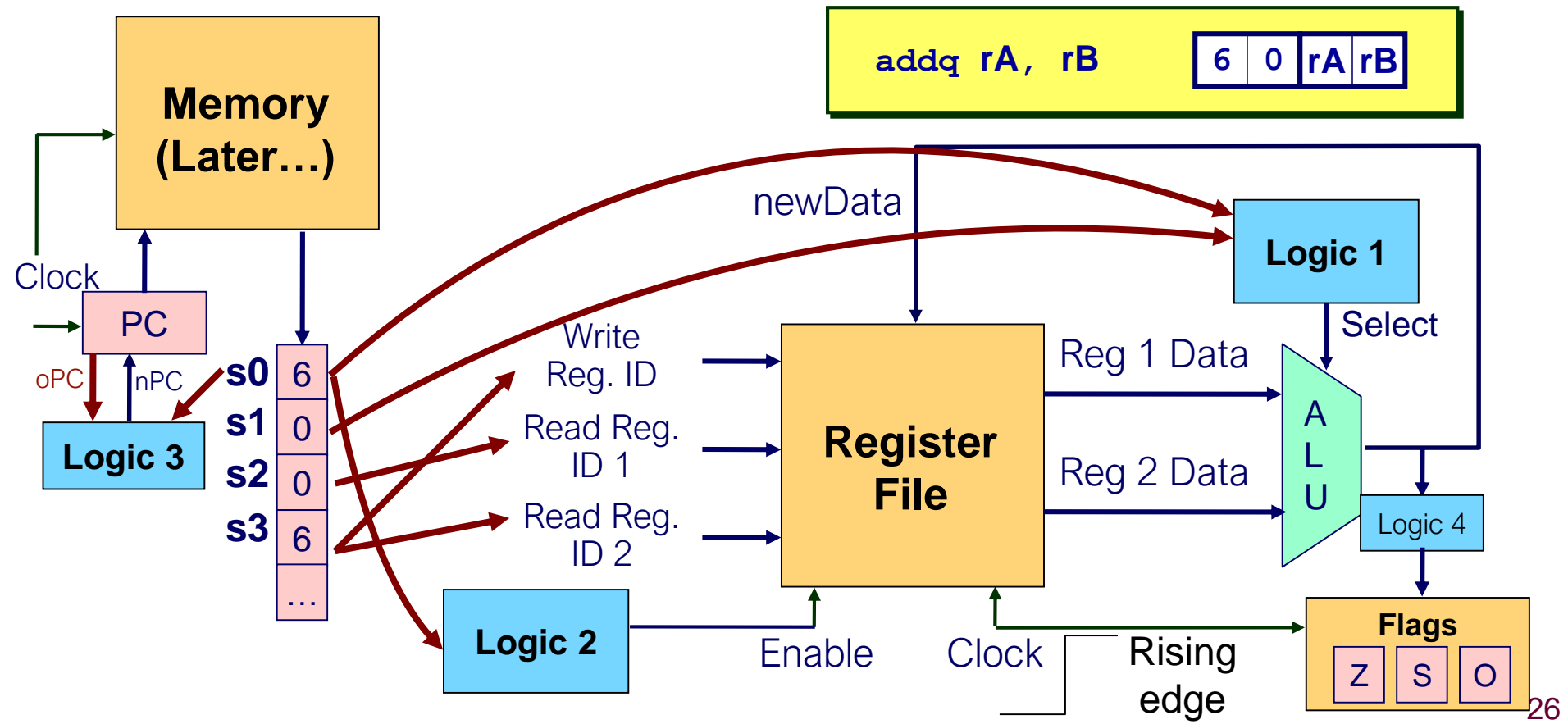

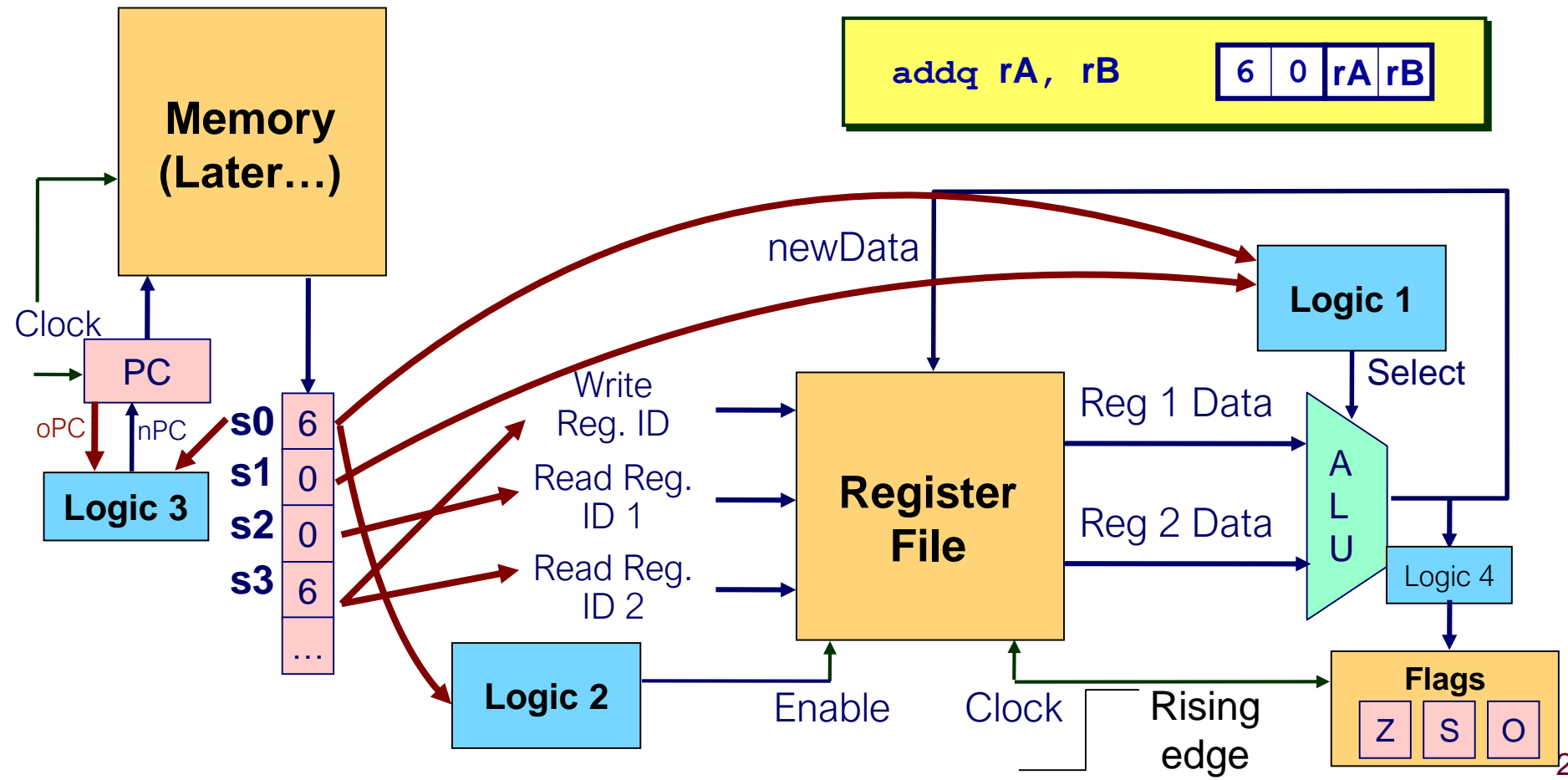
# Executing an ADD instruction

- When the rising edge of the clock arrives, the RF/PC/Flags will be written.
- So the following has to be ready: newData, nPC, which means Logic1, Logic2, Logic3, and Logic4 has to finish.



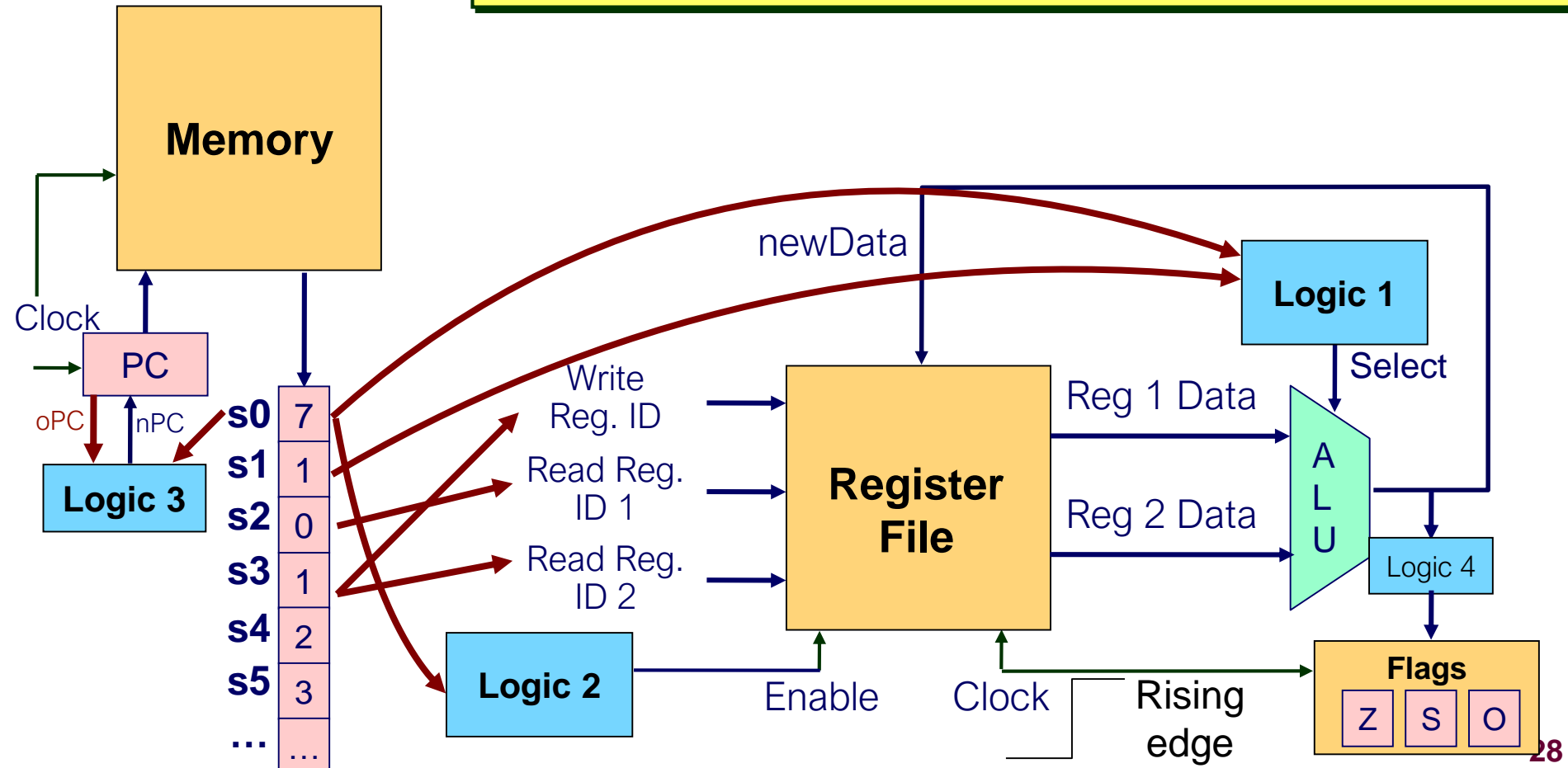
# Executing a JLE instruction

- Let's say the binary encoding for `jle .L0` is `71 0123000000000000`
- What are the logics now?


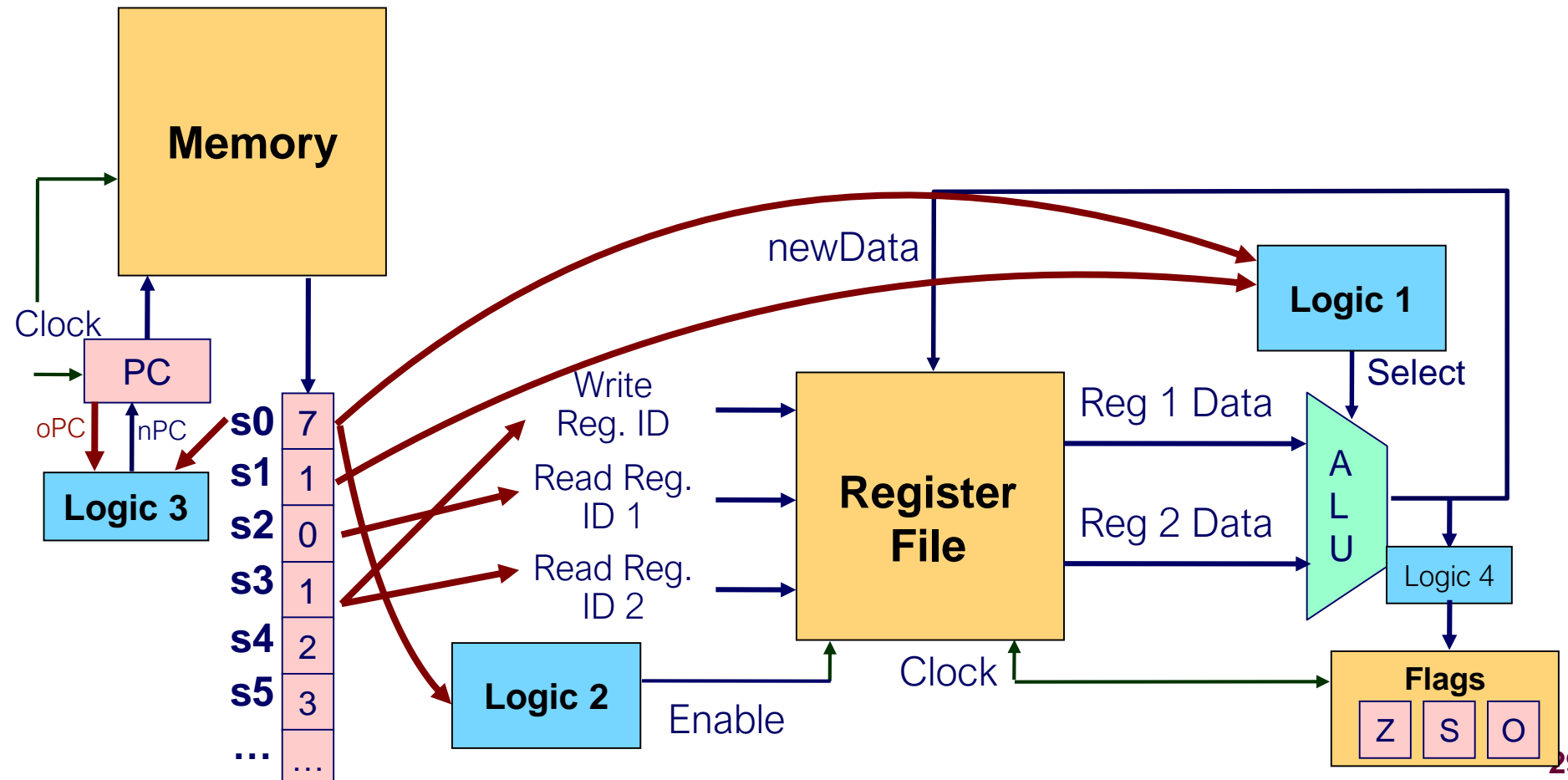
# Executing a JLE instruction

- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;



jle Dest

7


1

Dest

# Executing a JLE instruction


## ■ Logic 3??

```
if (s0 == 6) nPC = oPC + 2;  
else if (s0 == 7) {  
  if (s1 == 1) { // jLE  
    if (Z || (S ^ O)) nPC = Dest; // jump  
    else nPC = oPC + 9; // don't jump, but add 9 (why??)  
  } else if (s1 == ...) {...}  
}}
```

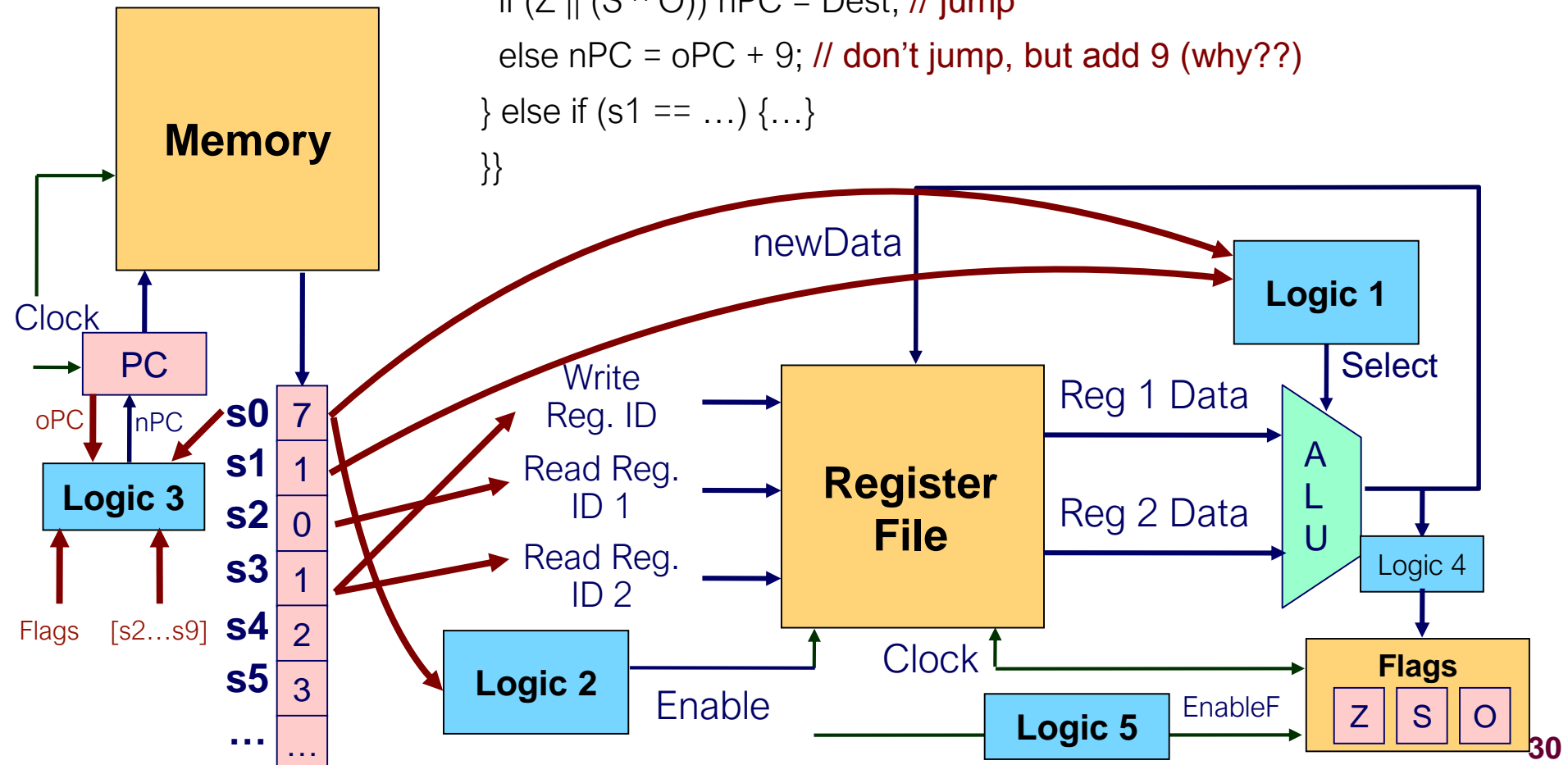

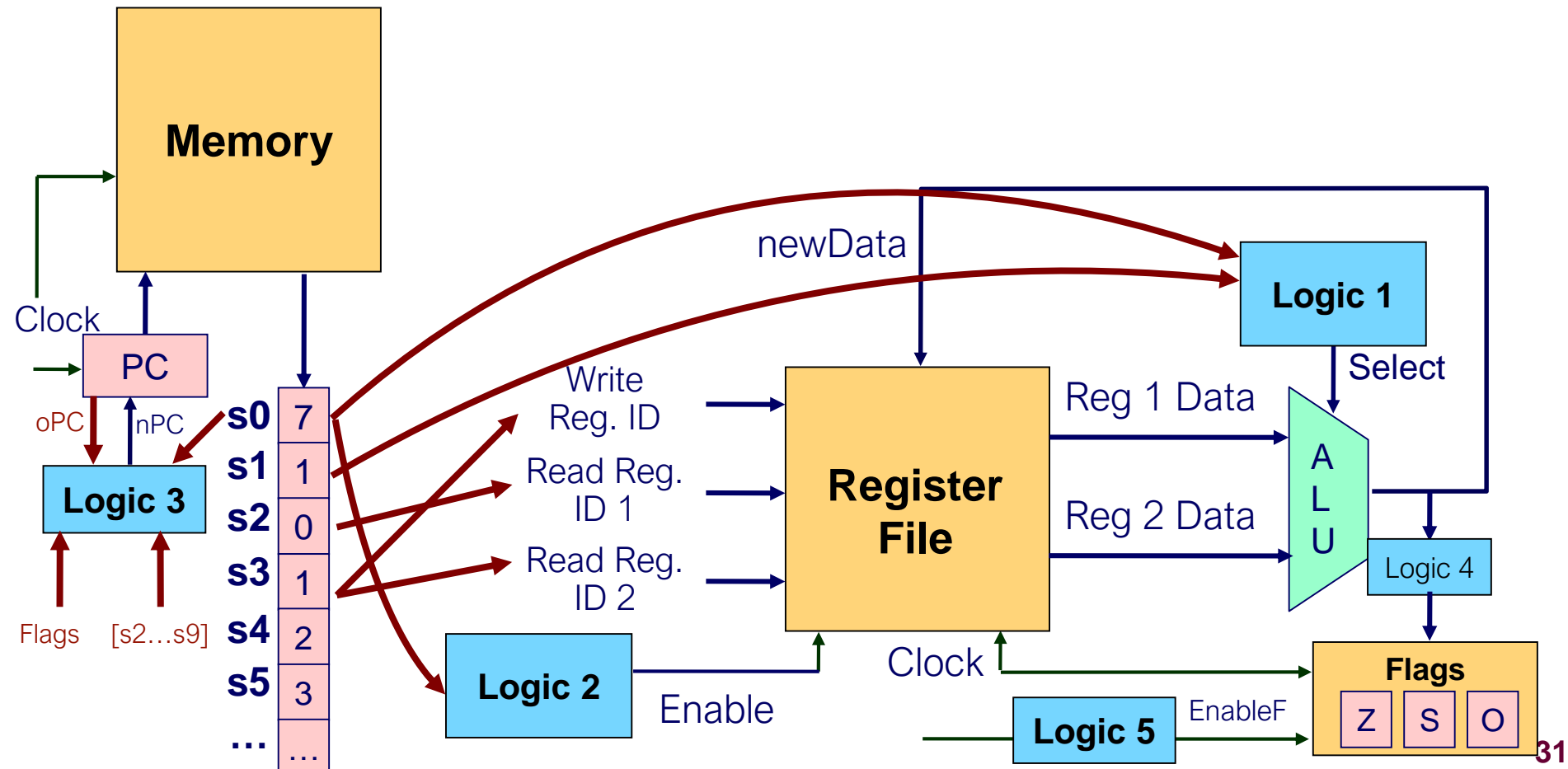
# Executing a JLE instruction

- Logic 4? Does JLE write flags?
- Need another piece of logic.
- Logic 5: if (s0 == 7) EnableF = 0; else if (s0 == 6) EnableF = 1;



# Microarchitecture (So far)

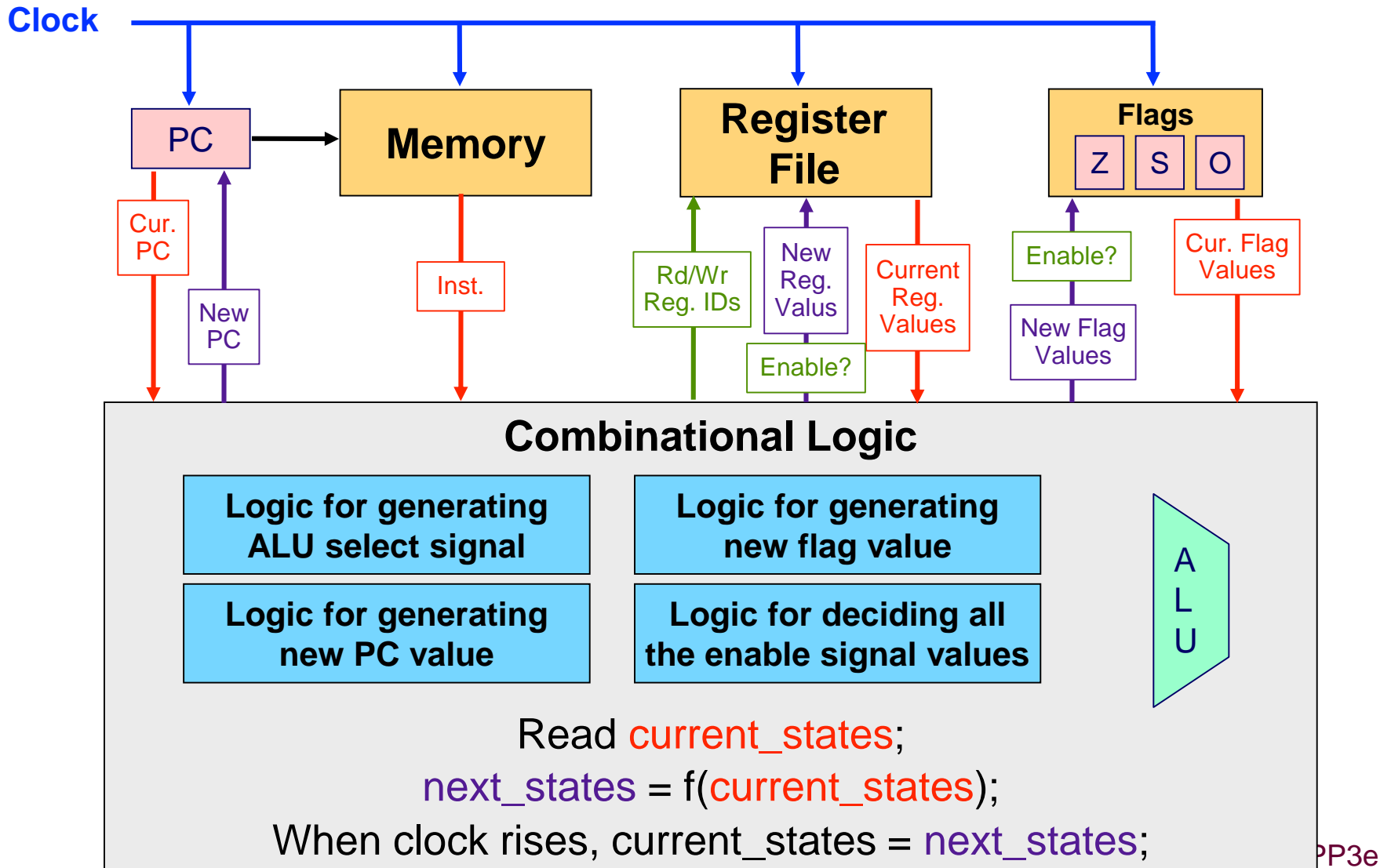




# Executing a MOV instruction


- How do we modify the hardware to execute a move instruction?

rmmovq rA, D(rB)

 

move rA to the memory address rB + D

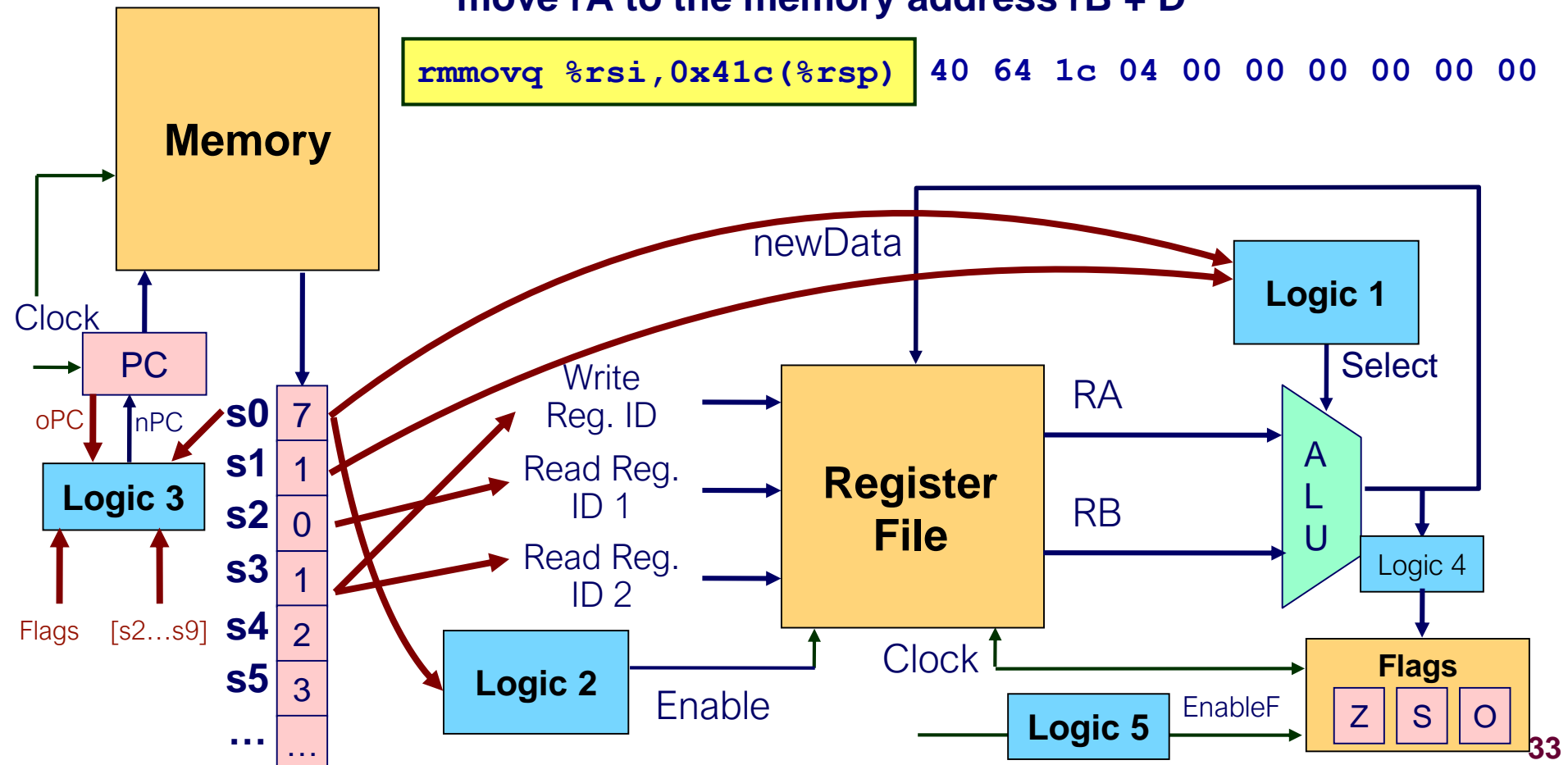rmmovq %rsi,0x41c(%rsp) 40 64 1c 04 00 00 00 00 00 00 00




move rA to the memory address rB + D

rmmovq rA, D(rB)



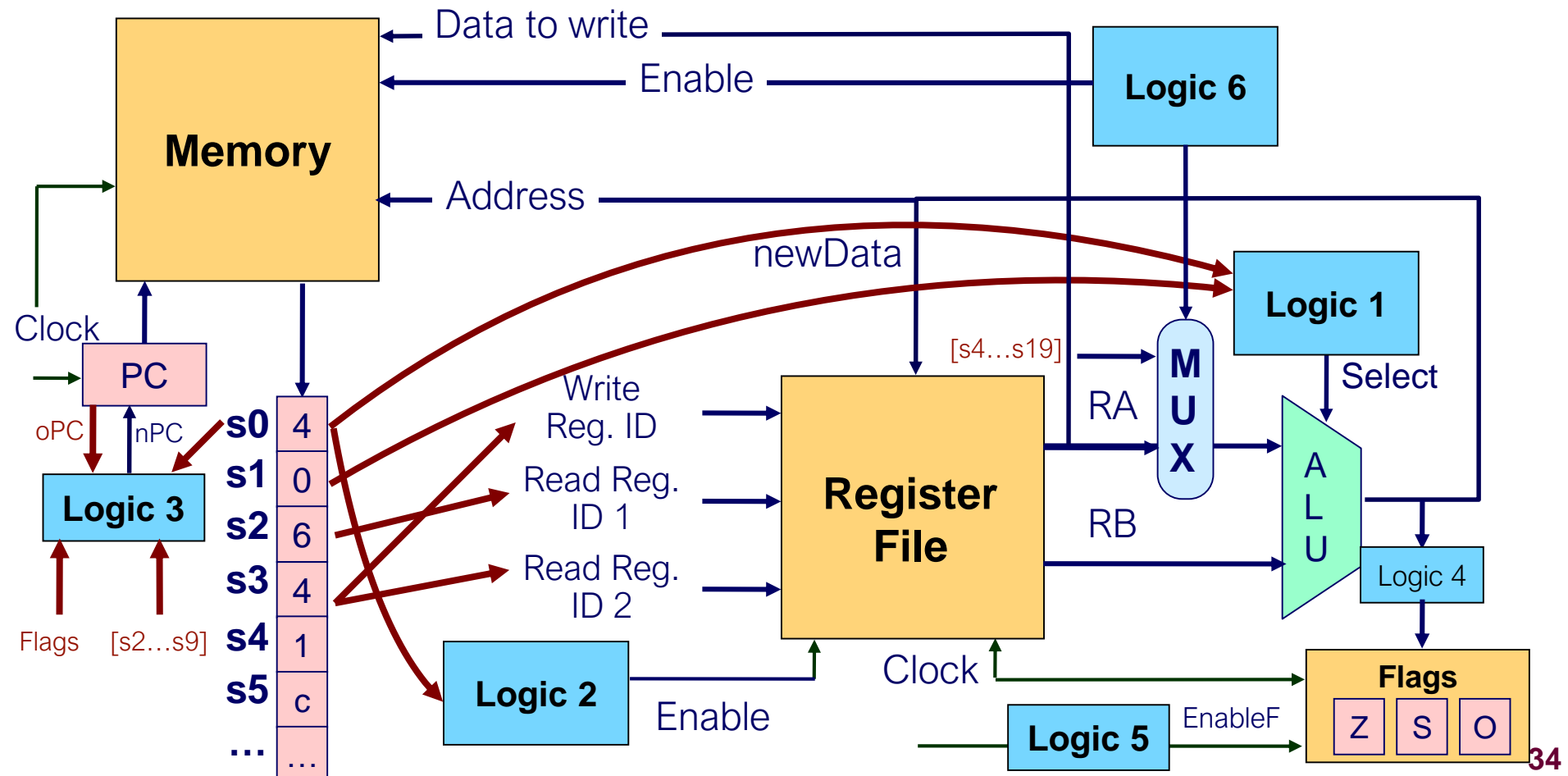
- Need new logic (Logic 6) to select the input to the ALU for Enable.
- How about other logics?



# How About Memory to Register MOV?

move data at memory address  $rB + D$  to  $rA$


`mrmovq D(rB), rA`

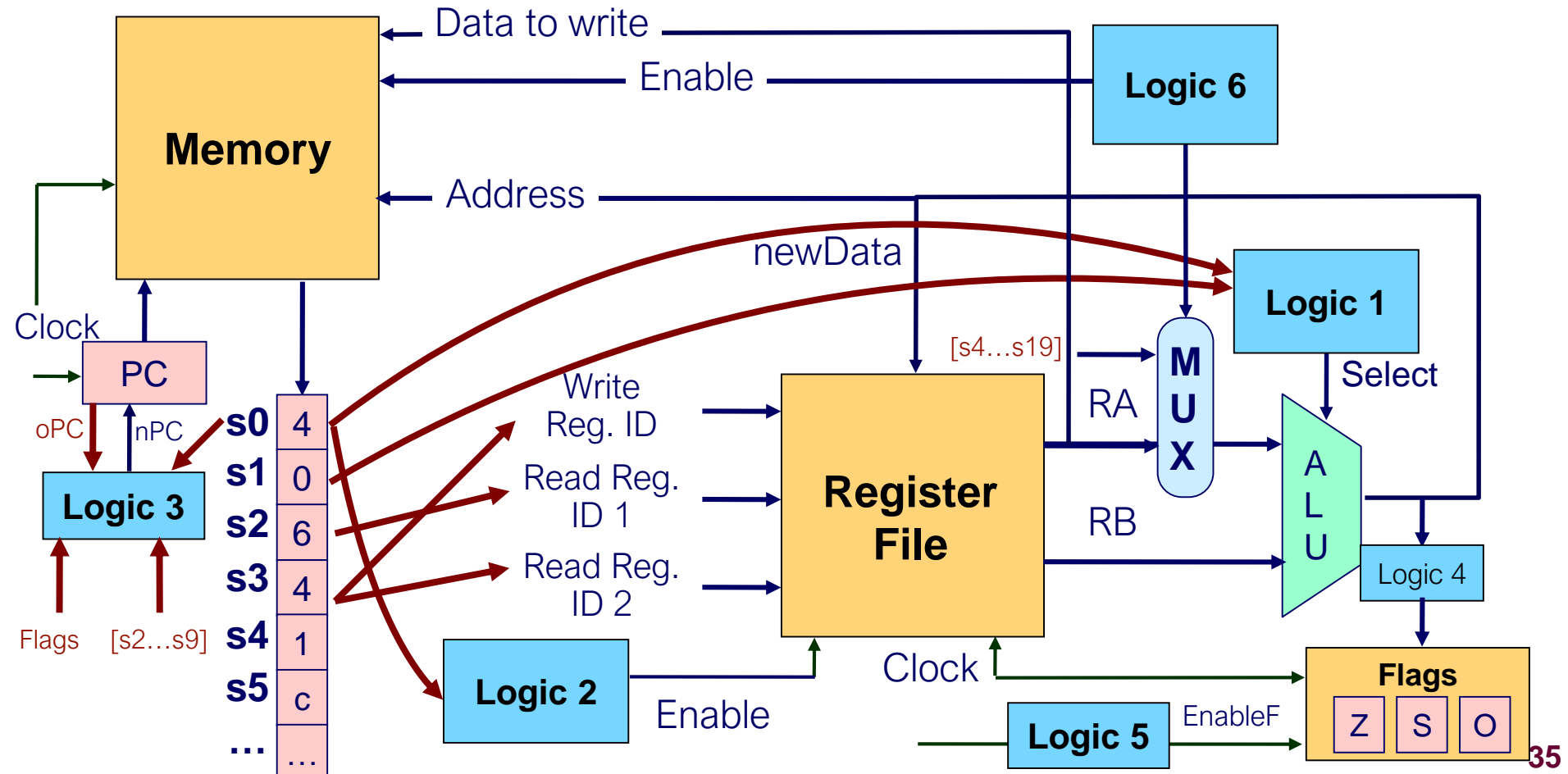


# How About Memory to Register MOV?

move data at memory address  $rB + D$  to  $rA$

`mrmovq D(rB), rA`

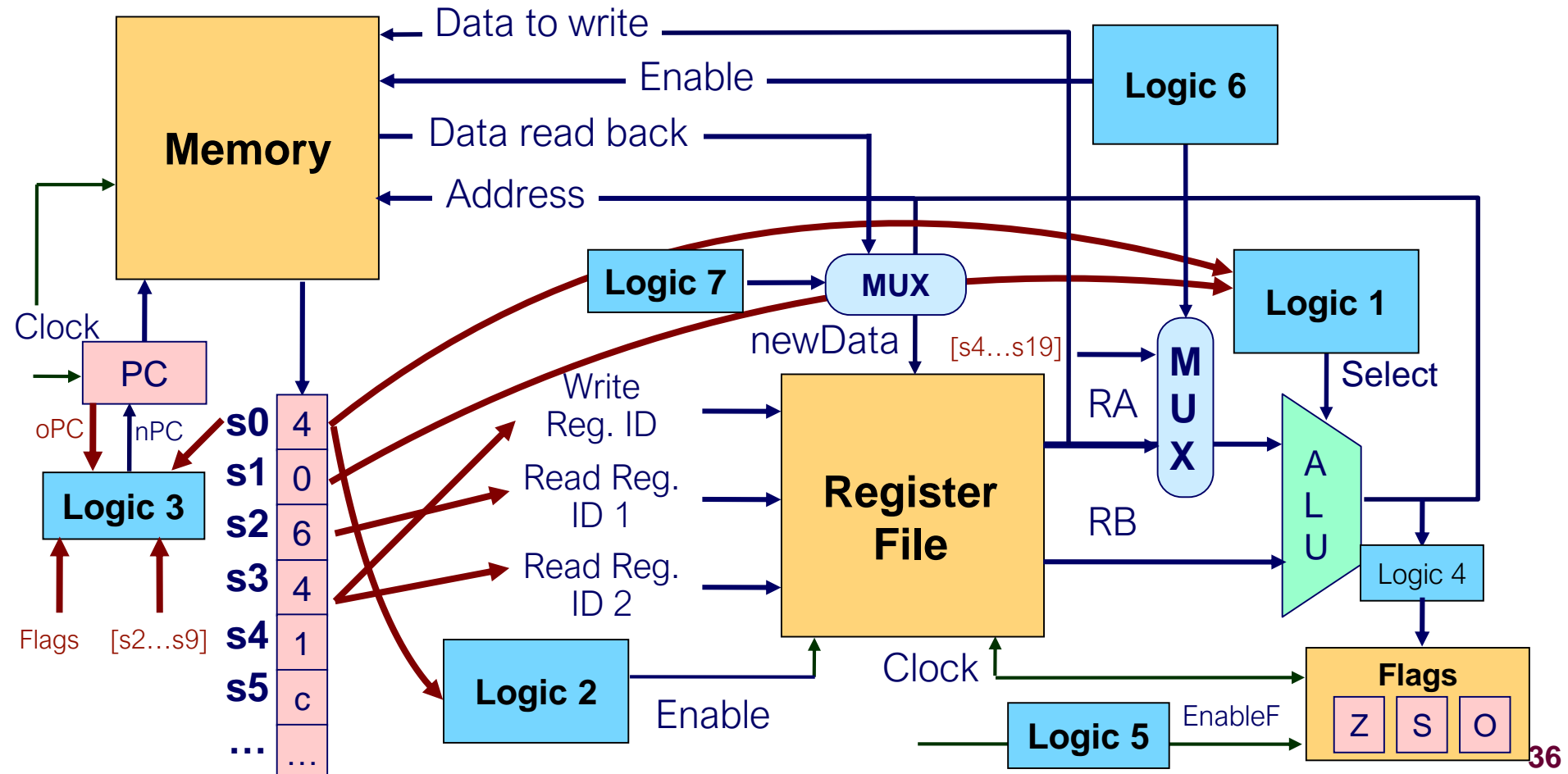

# Microarchitecture (with MOV)

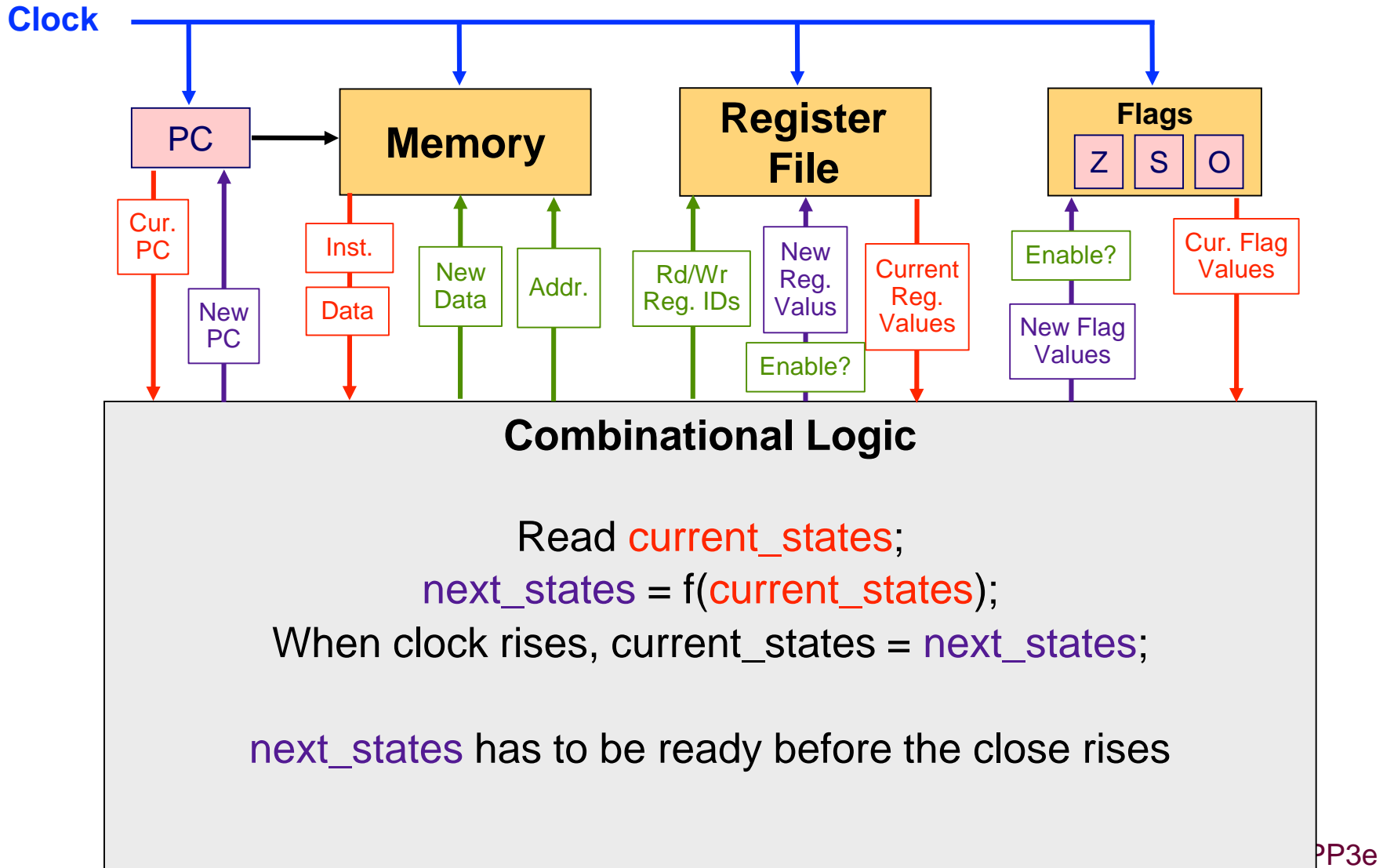


# Microarchitecture Overview


Think of it as a state machine

Every cycle, one instruction gets executed. At the end of the cycle, architecture states get modified.


States (All updated as clock rises)

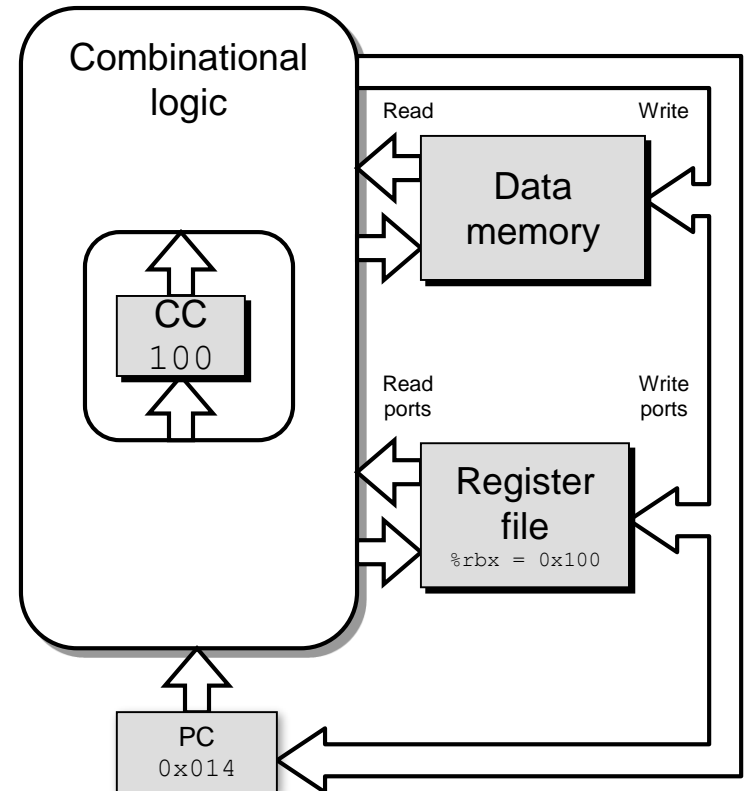- PC register
- Cond. Code register
- Data memory
- Register file




 


Cycle 1:	0x000:	<code>irmovq \$0x100,%rbx</code>	# %rbx <-- 0x100
Cycle 2:	0x00a:	<code>irmovq \$0x200,%rdx</code>	# %rdx <-- 0x200
Cycle 3:	0x014:	<code>addq %rdx,%rbx</code>	# %rbx <-- 0x300 CC <-- 000
Cycle 4:	0x016:	<code>je dest</code>	# Not taken
Cycle 5:	0x01f:	<code>rmmovq %rbx,0(%rdx)</code>	# M[0x200] <-- 0x300

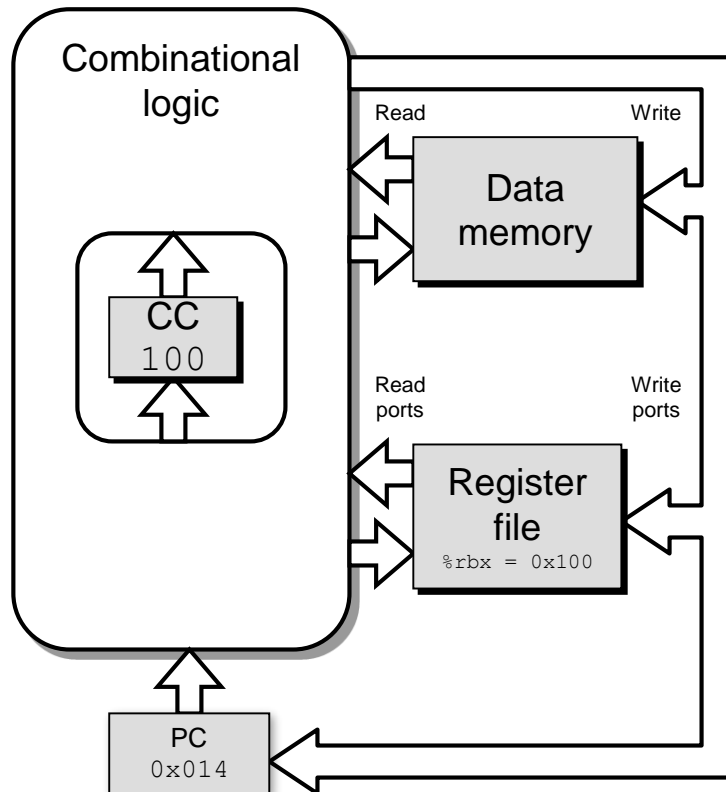

 state set according to second  
`irmovq` instruction  
combinational logic starting to  
react to state changes



Cycle 1:	0x000:	<code>irmovq \$0x100,%rbx</code>	# %rbx <-- 0x100
Cycle 2:	0x00a:	<code>irmovq \$0x200,%rdx</code>	# %rdx <-- 0x200
Cycle 3:	0x014:	<code>addq %rdx,%rbx</code>	# %rbx <-- 0x300 CC <-- 000
Cycle 4:	0x016:	<code>je dest</code>	# Not taken
Cycle 5:	0x01f:	<code>rmmovq %rbx,0(%rdx)</code>	# M[0x200] <-- 0x300

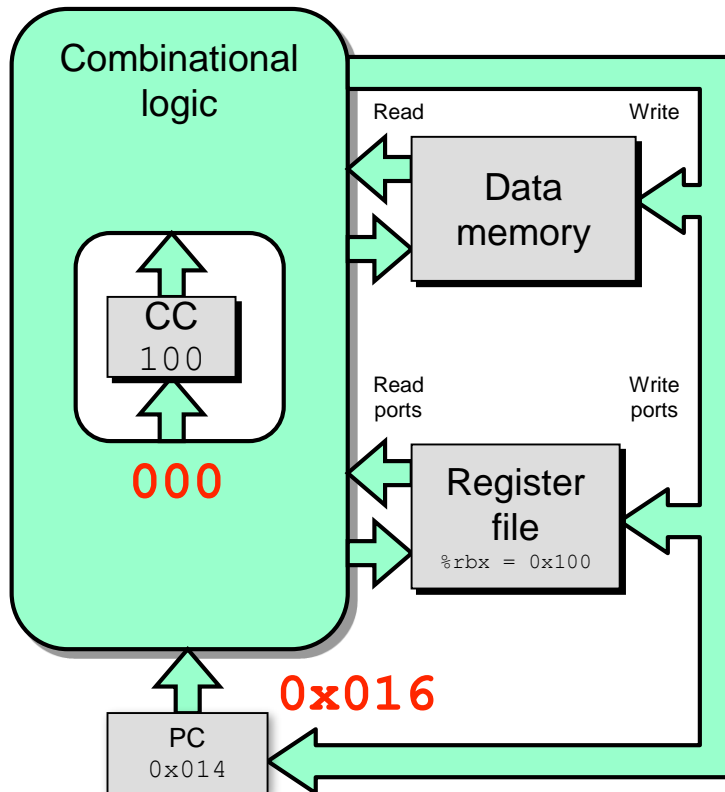


state set according to second `irmovq` instruction


combinational logic generates results for `addq` instruction

%rbx  
<--  
0x300



 


Cycle 1:	0x000:	irmovq \$0x100,%rbx	# %rbx <-- 0x100
Cycle 2:	0x00a:	irmovq \$0x200,%rdx	# %rdx <-- 0x200
Cycle 3:	0x014:	addq %rdx,%rbx	# %rbx <-- 0x300 CC <-- 000
Cycle 4:	0x016:	je dest	# Not taken
Cycle 5:	0x01f:	rmmovq %rbx,0(%rdx)	# M[0x200] <-- 0x300

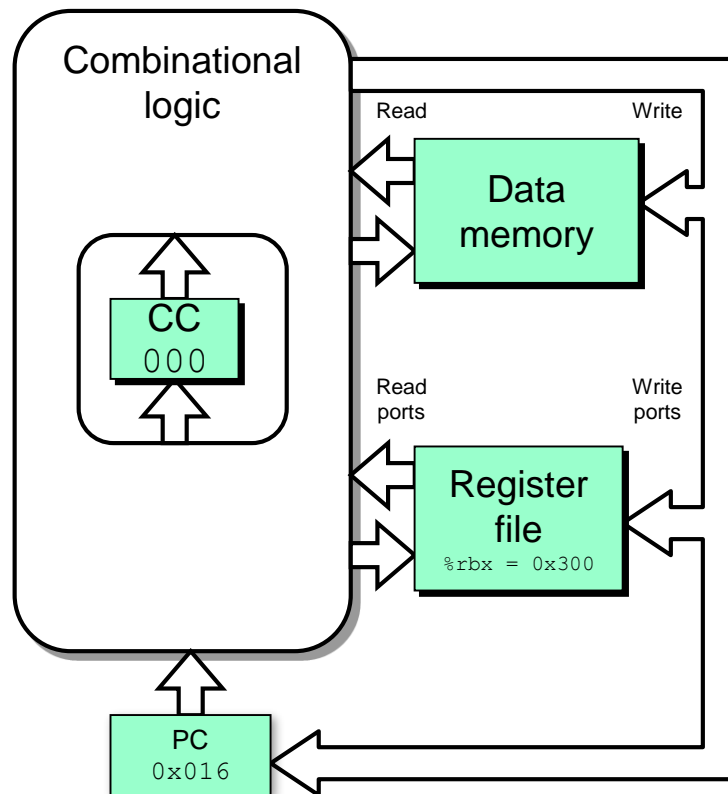


state set according to **addq** instruction

 combinational logic starting to react to state changes



Cycle 1:	0x000:	irmovq \$0x100,%rbx	# %rbx <-- 0x100
Cycle 2:	0x00a:	irmovq \$0x200,%rdx	# %rdx <-- 0x200
Cycle 3:	0x014:	addq %rdx,%rbx	# %rbx <-- 0x300 CC <-- 000
Cycle 4:	0x016:	je dest	# Not taken
Cycle 5:	0x01f:	rmmovq %rbx,0(%rdx)	# M[0x200] <-- 0x300

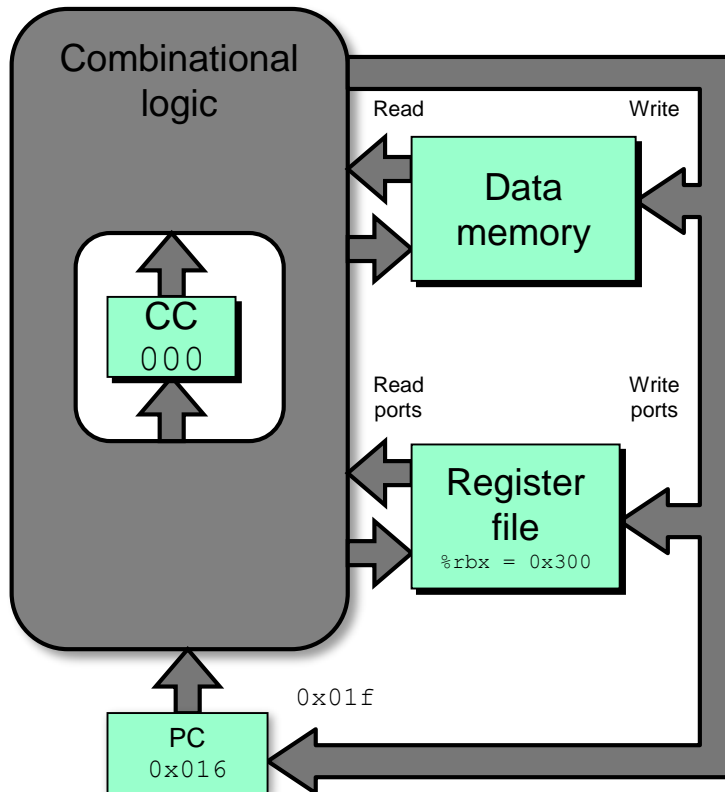

state set according to **addq** instruction

combinational logic generates results for **je** instruction