

# **CSC 252: Computer Organization**


## **Spring 2023: Lecture 13**

Instructor: Yuhao Zhu

Department of Computer Science  
University of Rochester


# Building on top of R-S Latch

D Latch

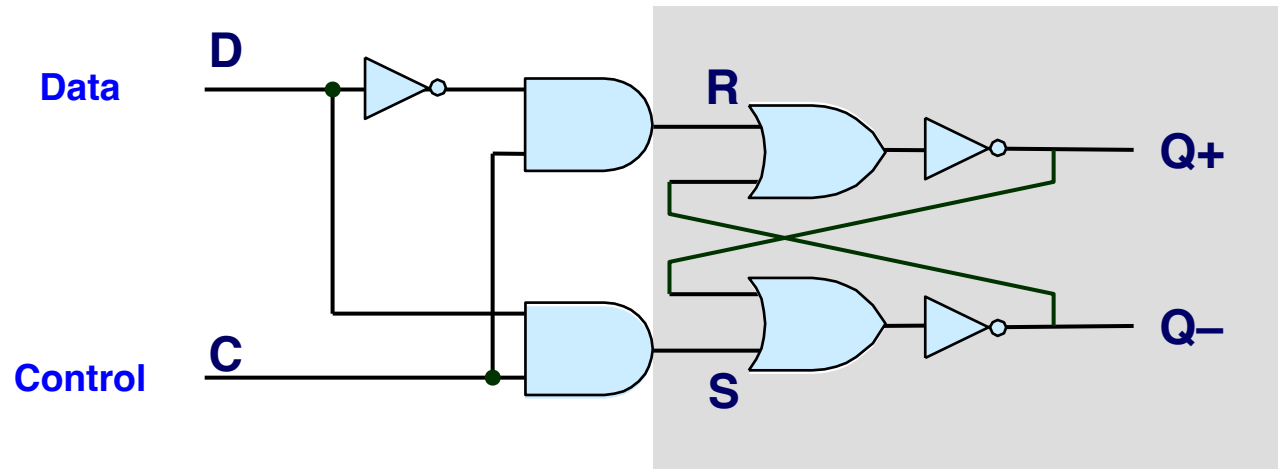


If R and S are different, Q+ is the same as S

Storing Data (Latching)

 

Q+ will continuously change as d changes


Holding Data

 


Q+ doesn't change with d

# D-Latch is “Transparent”

## Latching


 


## Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**
- There is a propagation delay of the combinational circuit from **D** to **Q+**. So hold C for a while until the signal is fully propagated
- Then set **C** to 0. Value latched depends on value of **D** as **C** goes to 0
- D-latch is *transparent* when **C** is 1
- D-latch is “*level-triggered*” b/c **Q** changes as the *voltage level* of **C** rises.

# Edge-Triggered Latch (Flip-Flop)

  


- Flip-flop: Only latches data for a brief period
- Value latched depends on data as C **rises** (i.e., 0→1); usually called at the **rising edge** of C
- Output remains stable at all other times


# Why Use a Flip-Flop?

 

 - Because the data we want to store might be temporarily changing before it settles down (due to glitch). We want to capture only the final value.
- If we had a transparent D latch, the latched value would change with F, i.e., temporal glitches will be temporarily stored as well.
- With a flip flop, we can store data only when its value settles: raise the control signal of the flop when F settles.




# Registers

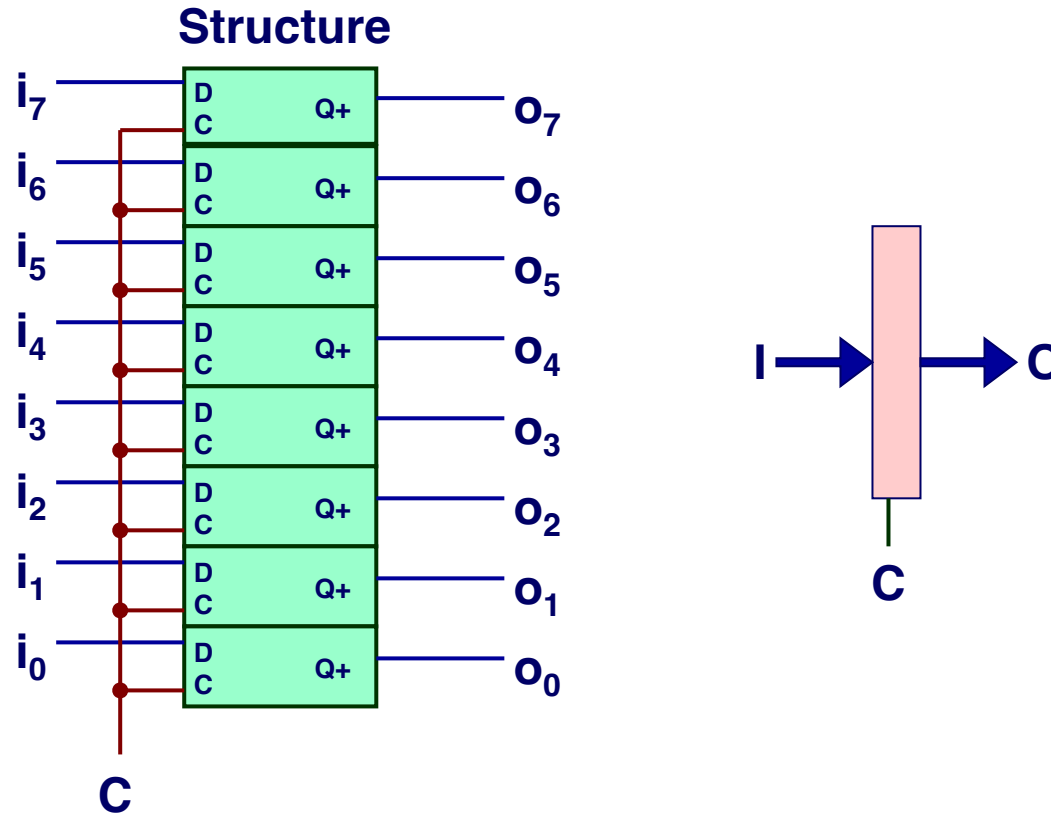

- Stores several bits of data
- Collection of edge-triggered latches (D Flip-flops)
- Loads input on rising edge of the C signal


# Register Operation

 


Output ***continuously*** produces y after the rising edge unless you cut off power.

- Stores data bits
- For most of time acts as barrier between input and output
- As C rises, loads input
- So you'd better compute the input before the C signal rises if you want to store the input data to the register

# Clock Signal

 

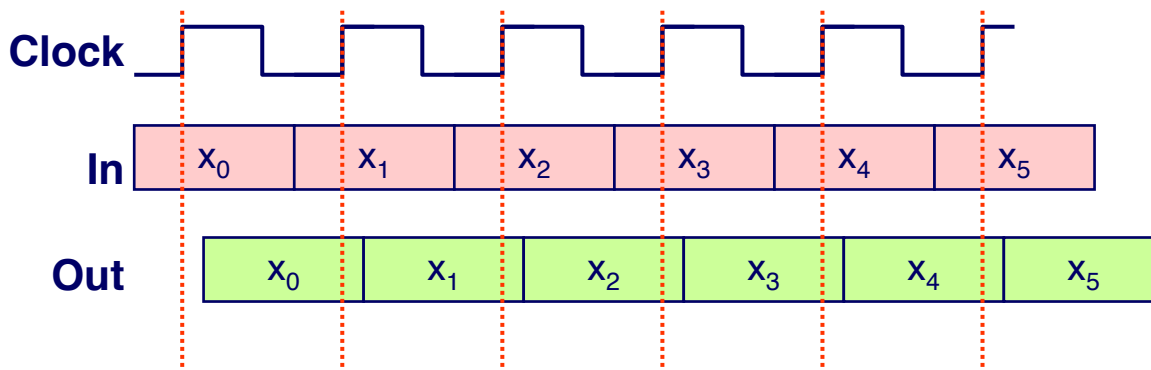
- A special C: periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer.




 
# Clock Signal


- Cycle time of a clock signal: the time duration between two rising edges.
- Frequency of a clock signal: how many rising (falling) edges in 1 second.
- 1 GHz CPU means the clock frequency is 1 GHz
  - The cycle time is  $1/10^9 = 1 \text{ ns}$



# Register File


- A register file consists of a set of registers that you can individually read from and write to.
- To read: give a register file ID, and read the stored value out
- To write: give a register file ID, a new value, overwrite the old value
- How do we build a register file out of individual registers??

## Register File

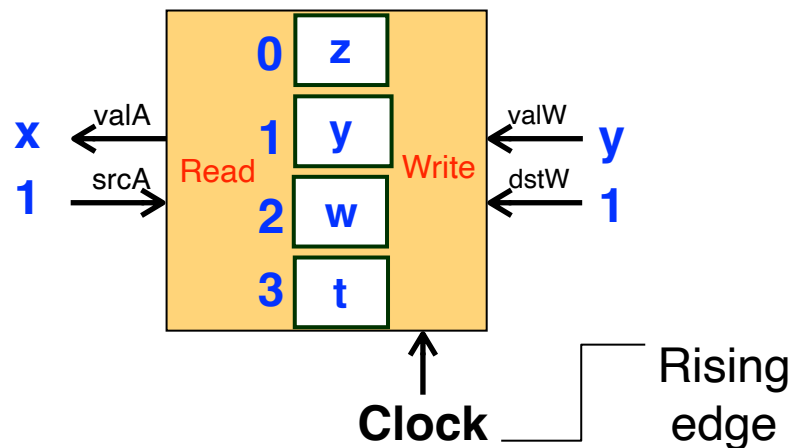

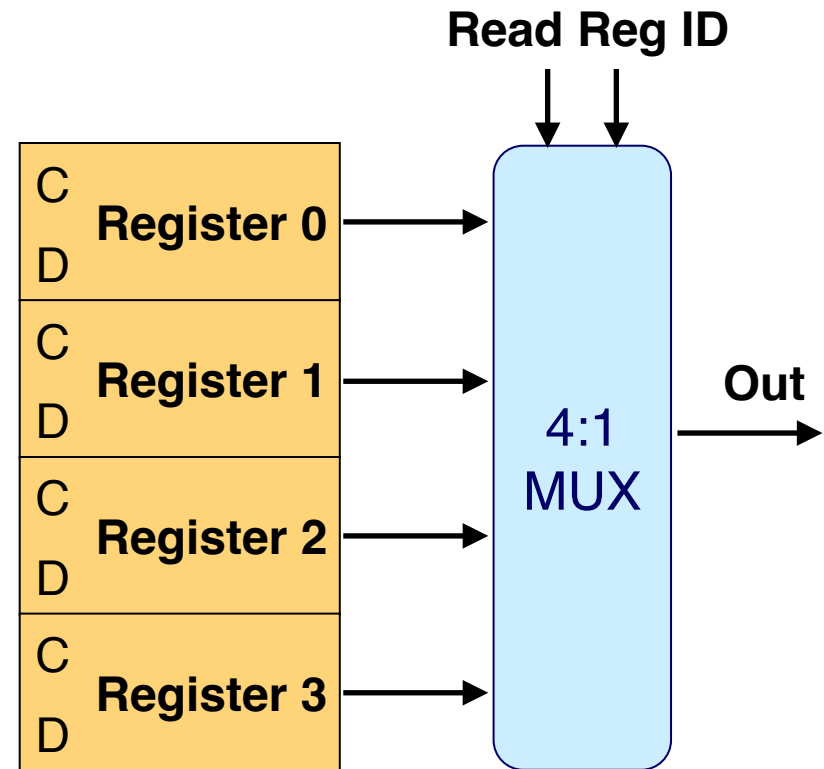
# Register File Read

- Continuously read a register independent of the clock signal


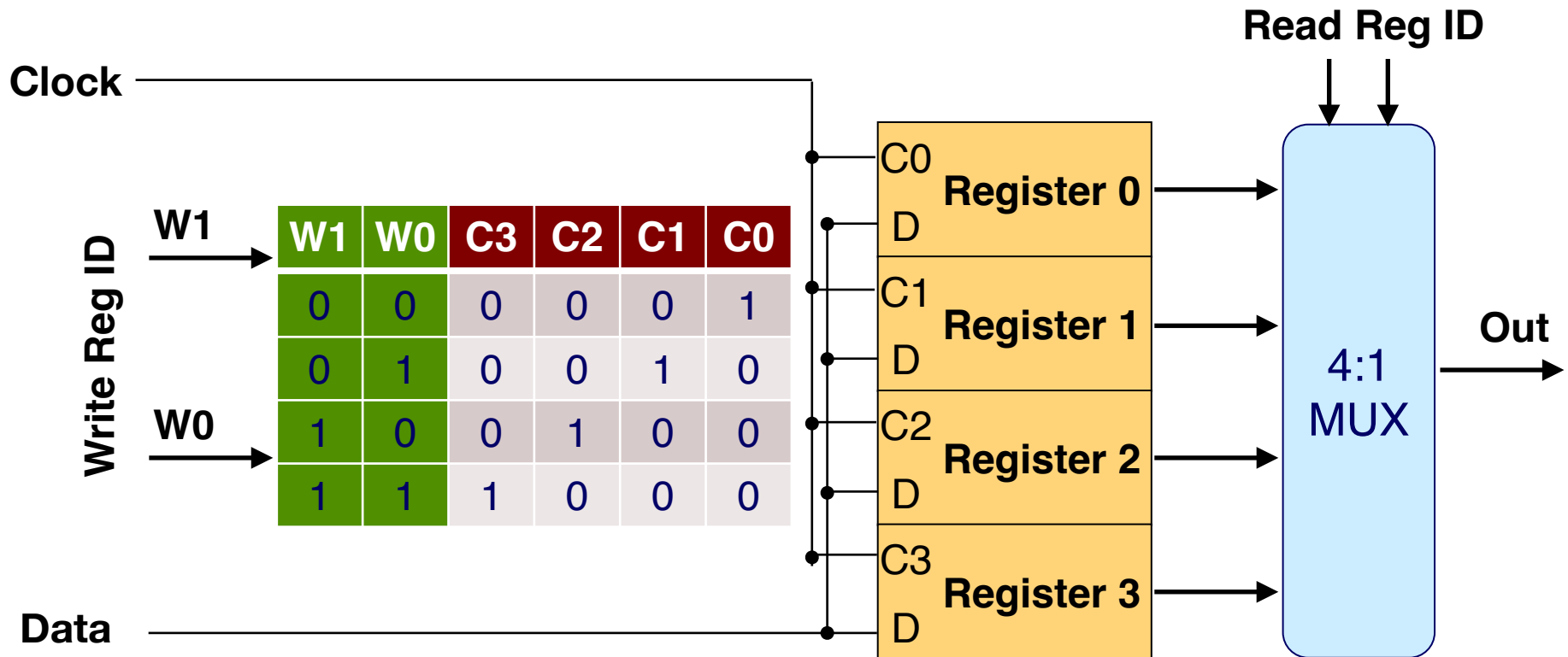
# Register File Write

- Only write to a specific register when the clock rises. How??



# Decoder

W1	W0	C3	C2	C1	C0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

W0 \_

W1 \_

\_C0

\_C1

\_C2

\_C3


$$C0 = !W1 \ \& \ !W0$$

$$C1 = !W1 \ \& \ W0$$

$$C2 = W1 \ \& \ !W0$$

$$C3 = W1 \ \& \ W0$$


# Register File Write

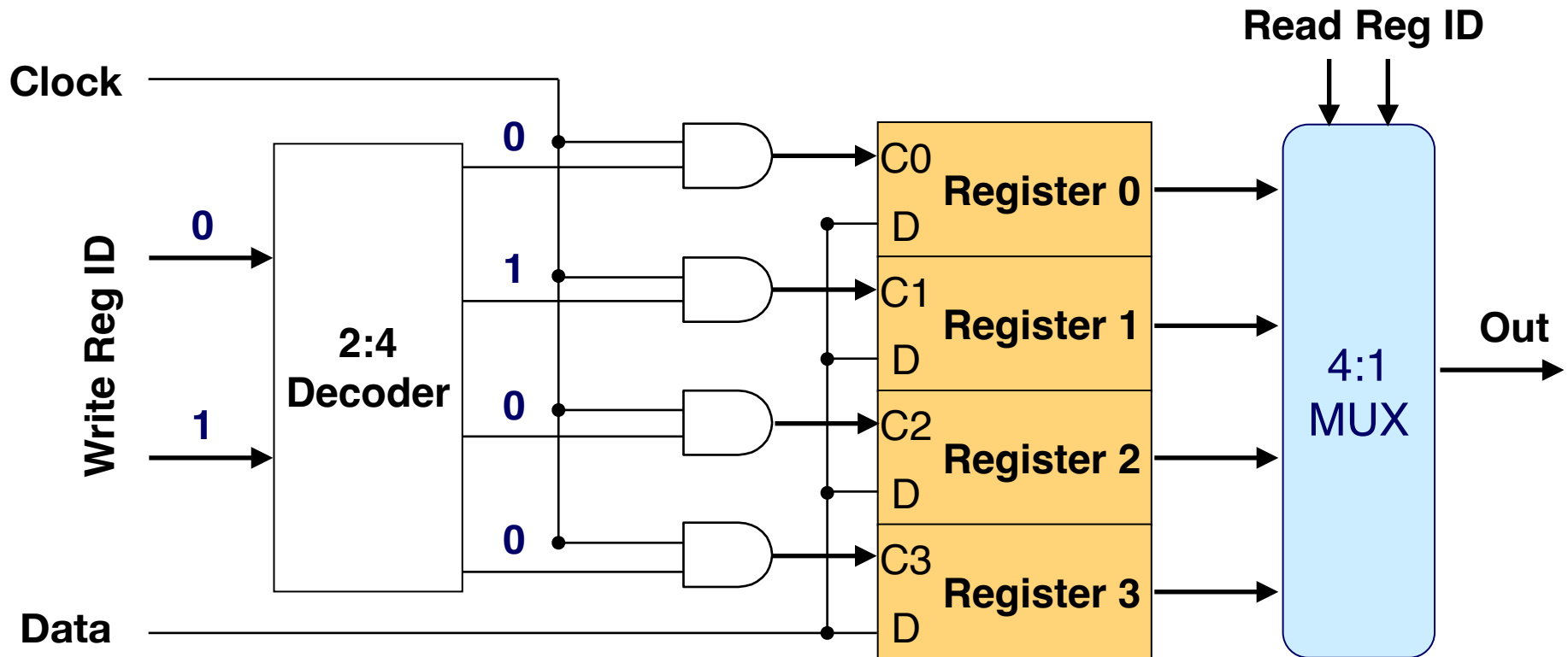

- This implementation can read 1 register and write 1 register at the same time: 1 read port and 1 write port

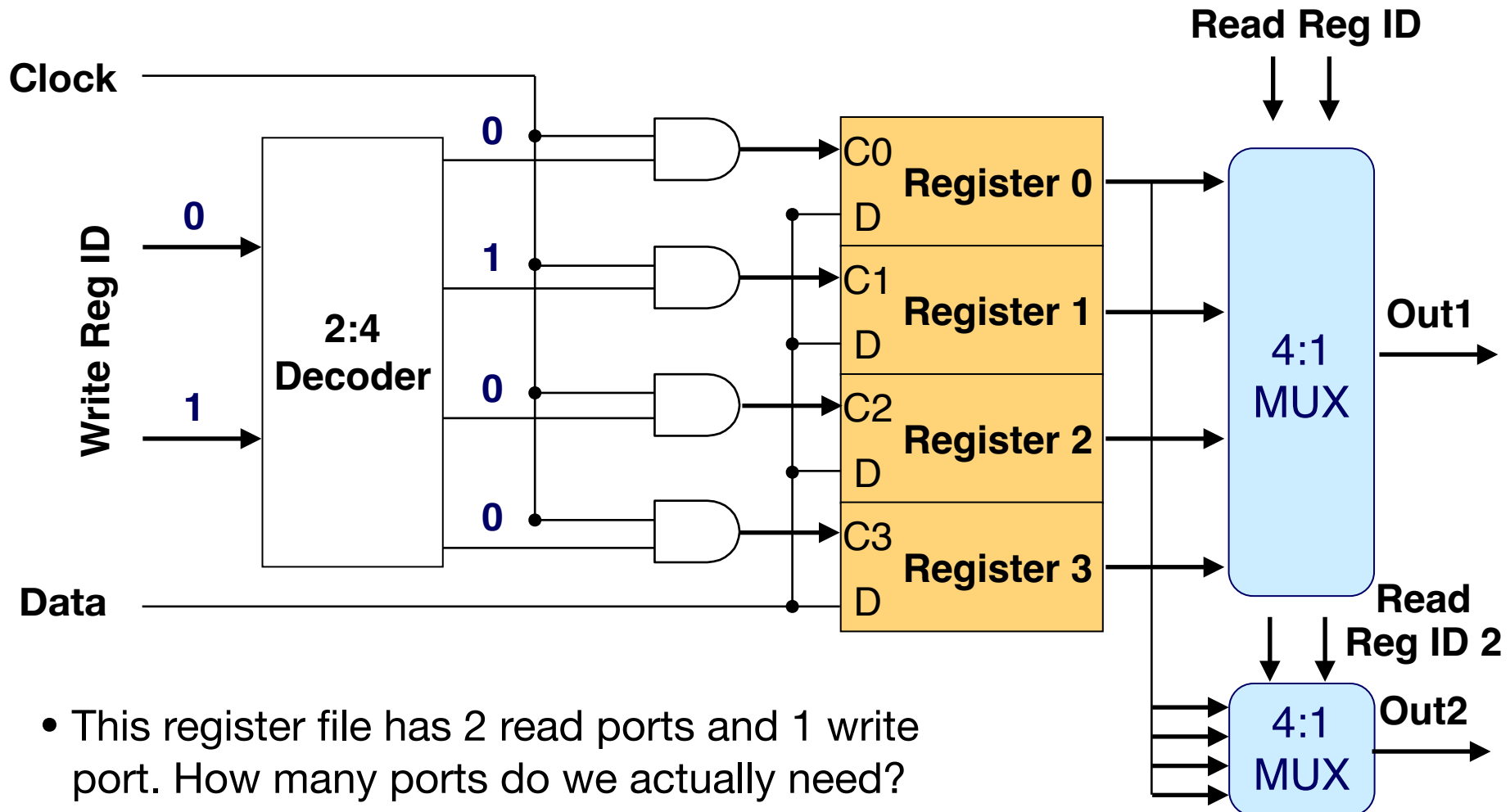
# Multi-Port Register File

- What if we want to read multiple registers at the same time?


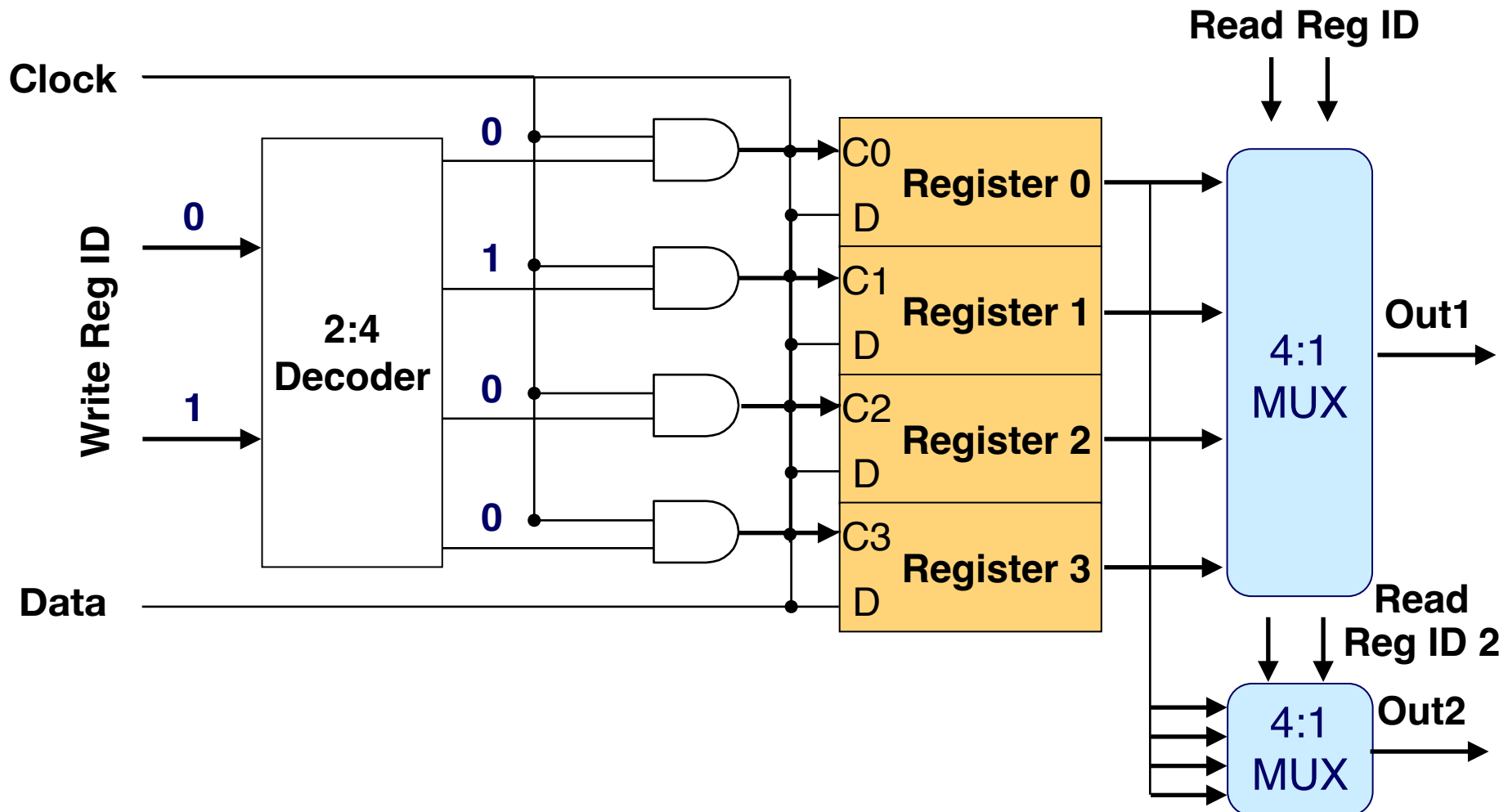
# Multi-Port Register File


- Is this correct? What if we don't want to write anything?




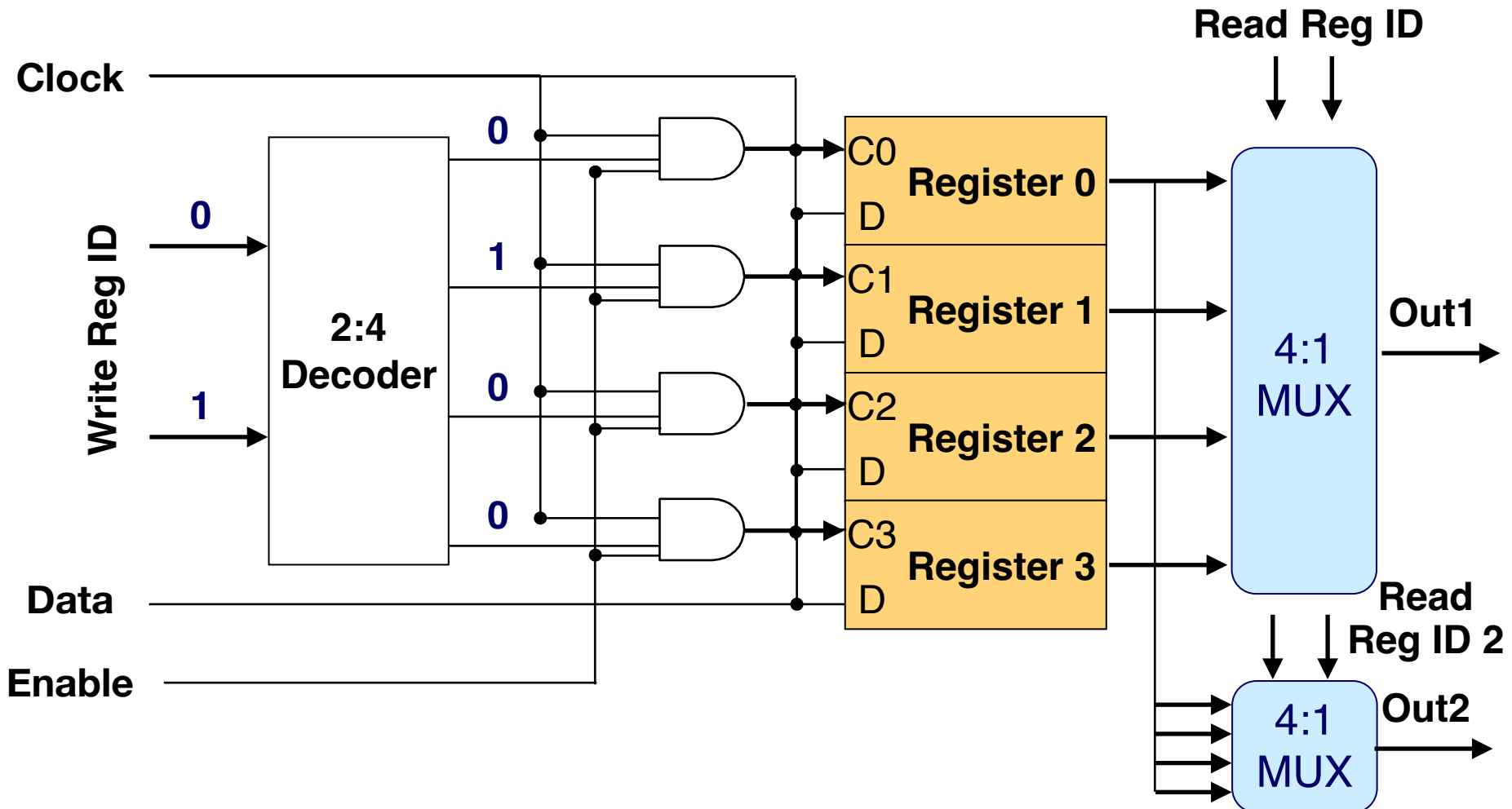
# Multi-Port Register File

- Is this correct? What if we don't want to write anything?




# Processor Microarchitecture

- Sequential, single-cycle microarchitecture implementation
  - Basic idea
  - Hardware implementation
- Pipelined microarchitecture implementation
  - Basic Principles
  - Difficulties: Control Dependency
  - Difficulties: Data Dependency

 
# Executing an ADD instruction

- How does the processor execute `addq %rax,%rsi`
- The binary encoding is `60 06`


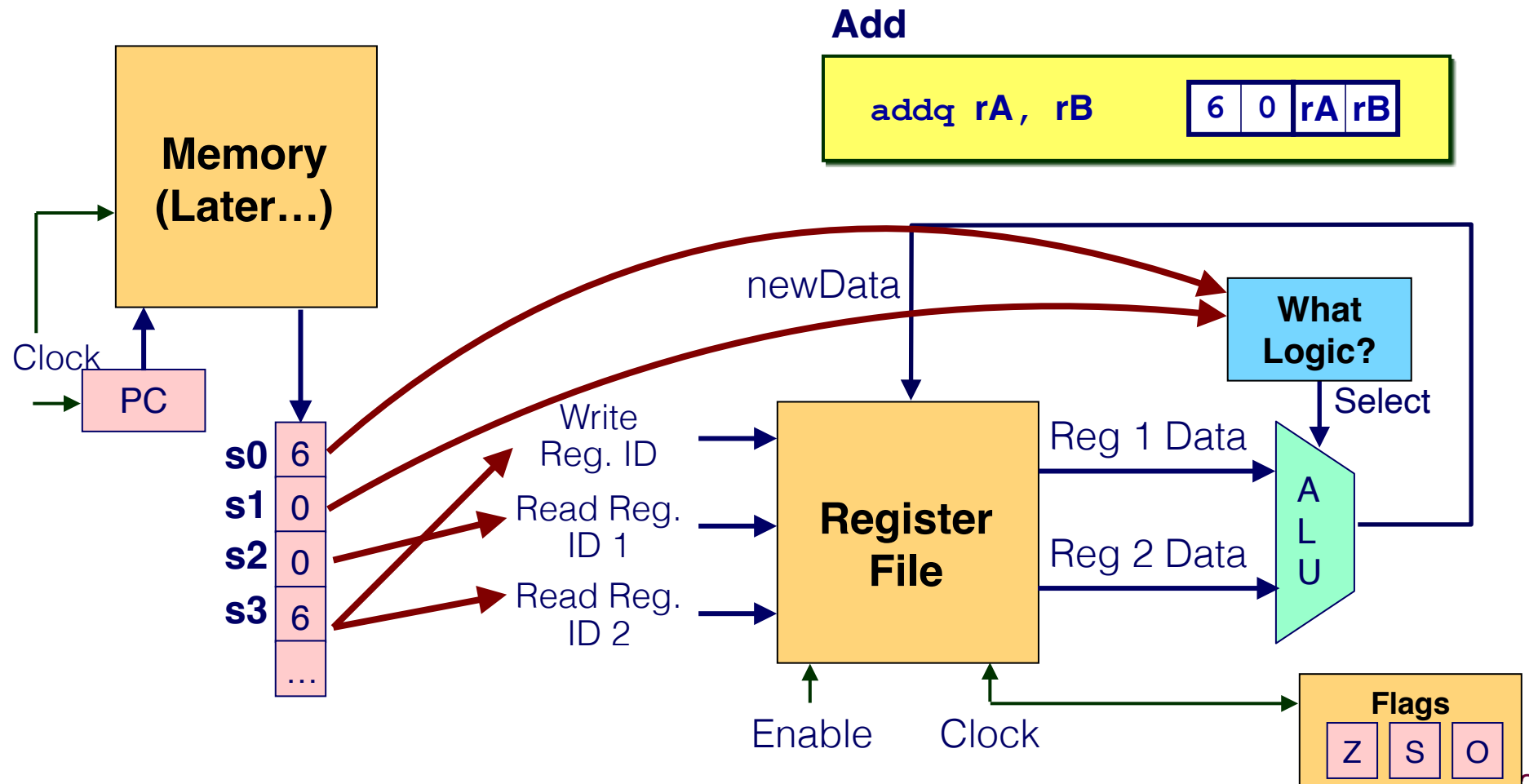
# Executing an ADD instruction


- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`



# Executing an ADD instruction


- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;
- Logic 3: if (s0 == 6) nPC = oPC + 2;
- How about Logic 4?

How do these logics get implemented?

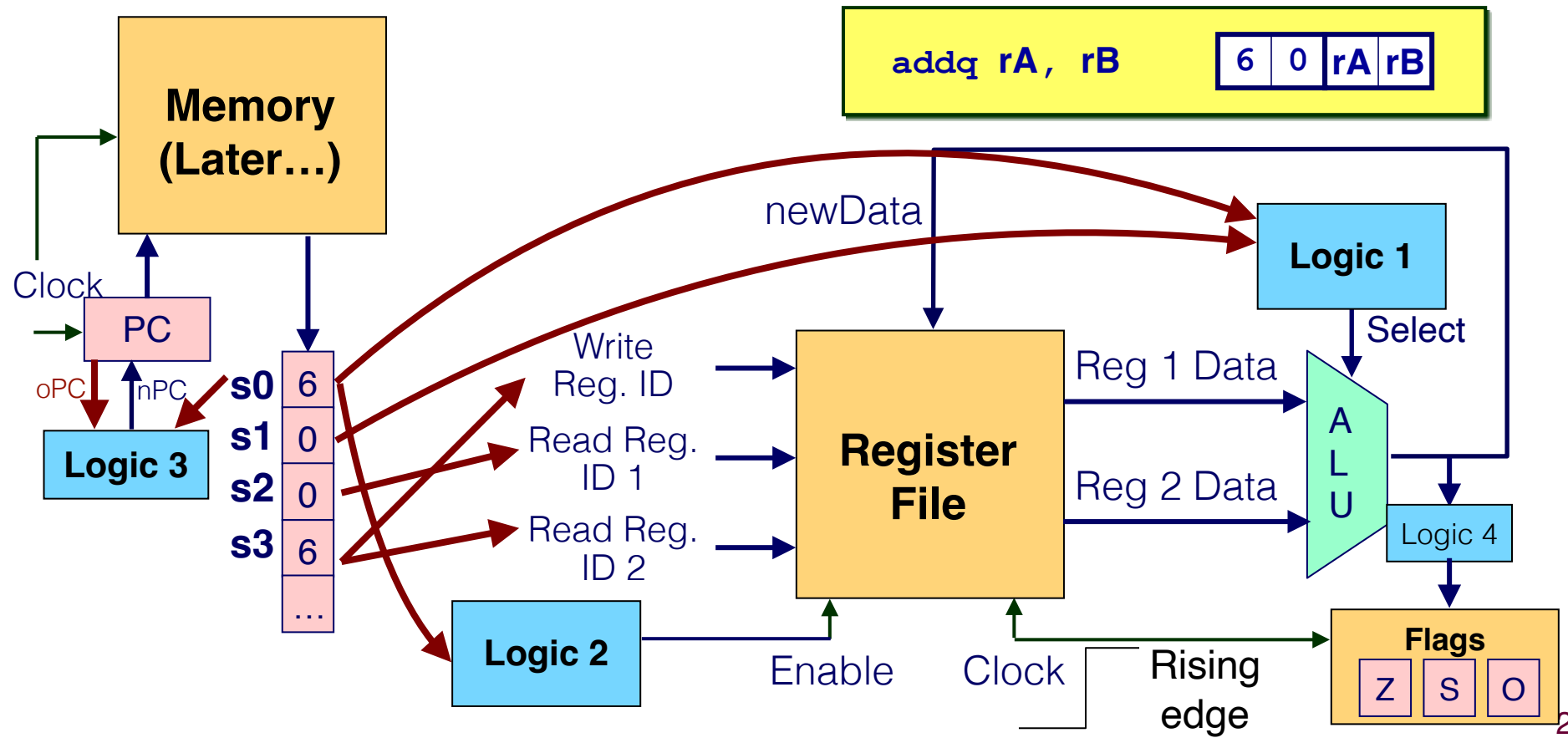

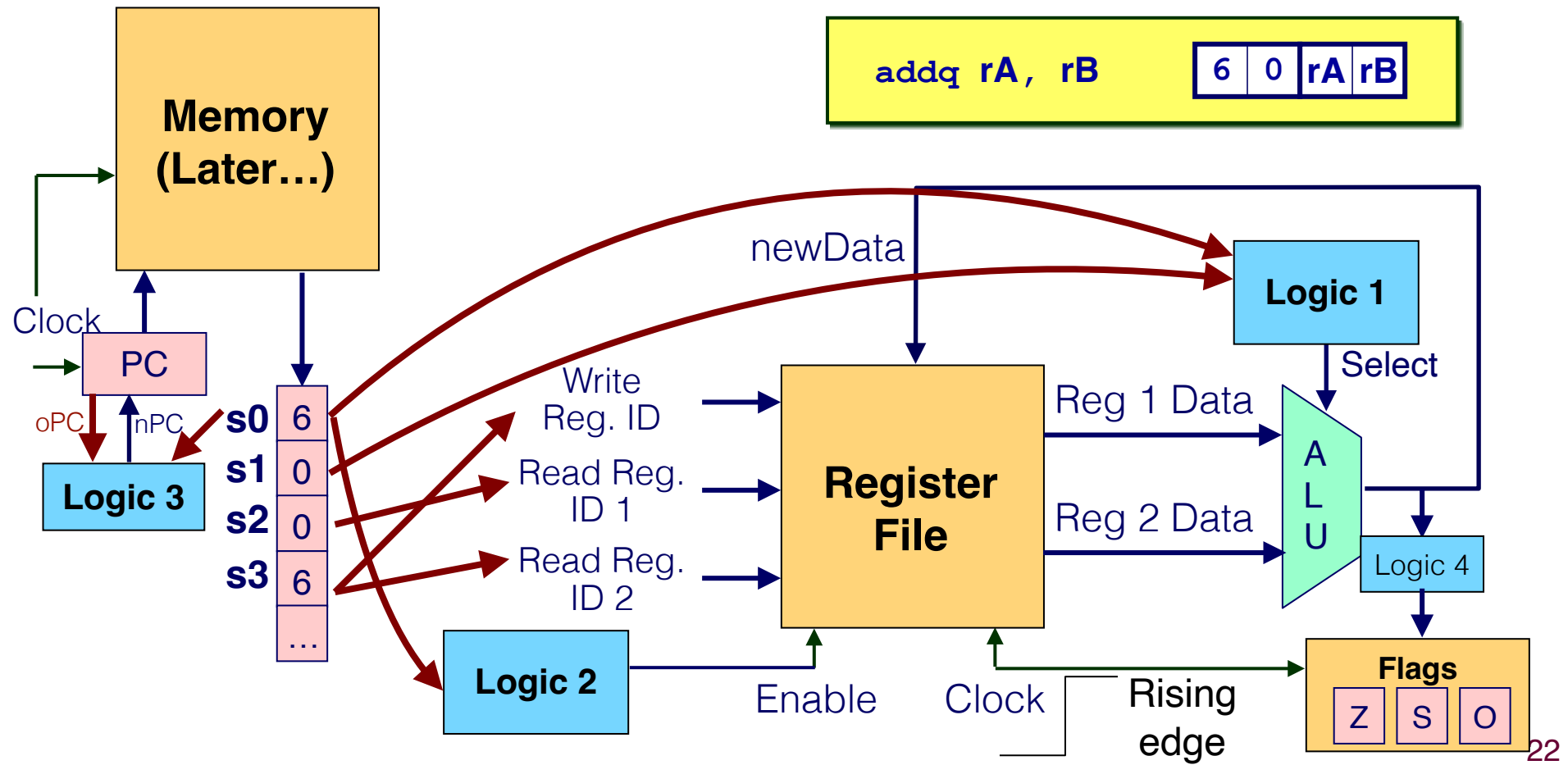
# Executing an ADD instruction

- When the rising edge of the clock arrives, the RF/PC/Flags will be written.
- So the following has to be ready: newData, nPC, which means Logic1, Logic2, Logic3, and Logic4 has to finish.



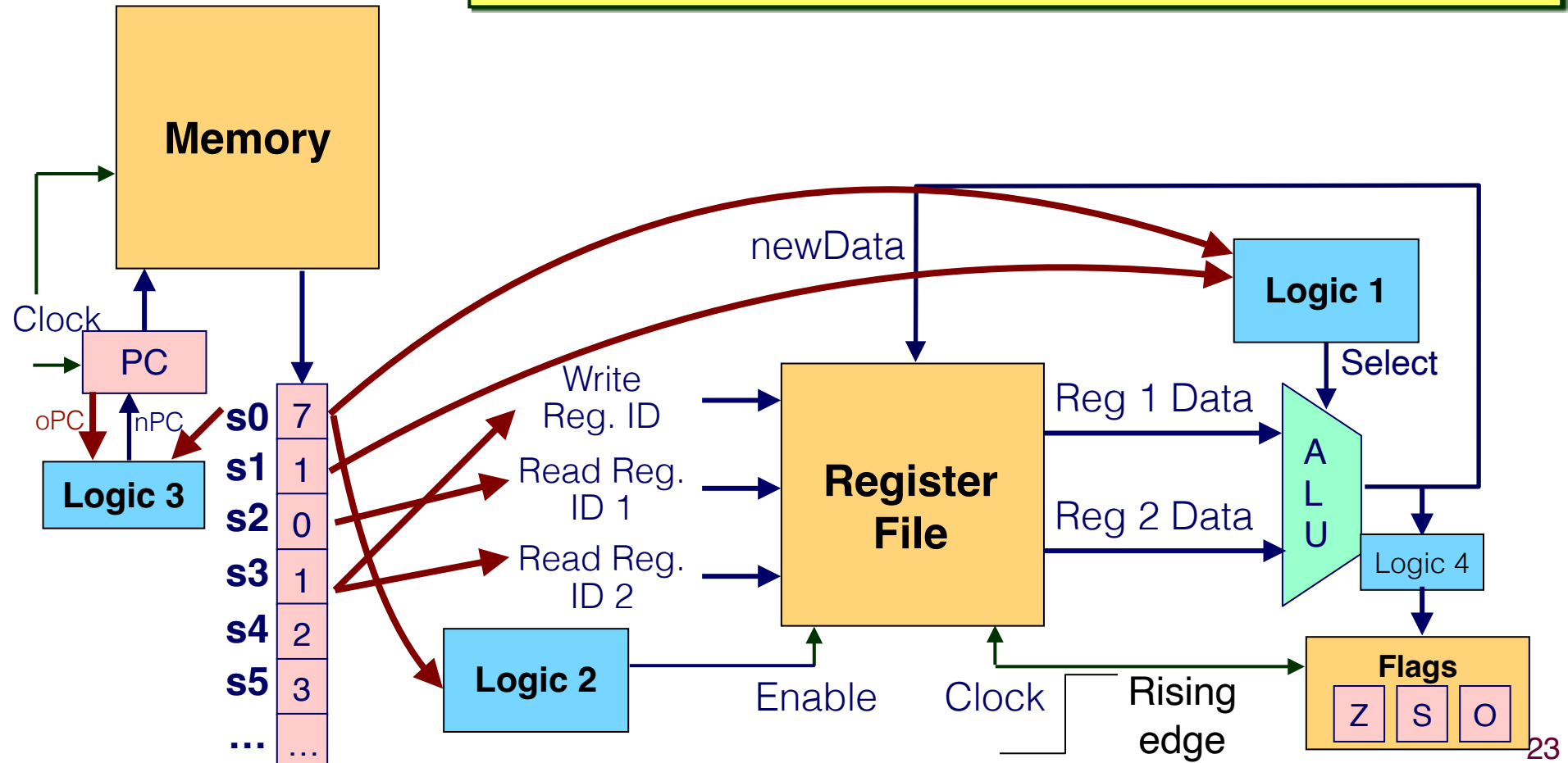
# Executing a JLE instruction

- Let's say the binary encoding for `jle .L0` is `71 0123000000000000`
- What are the logics now?


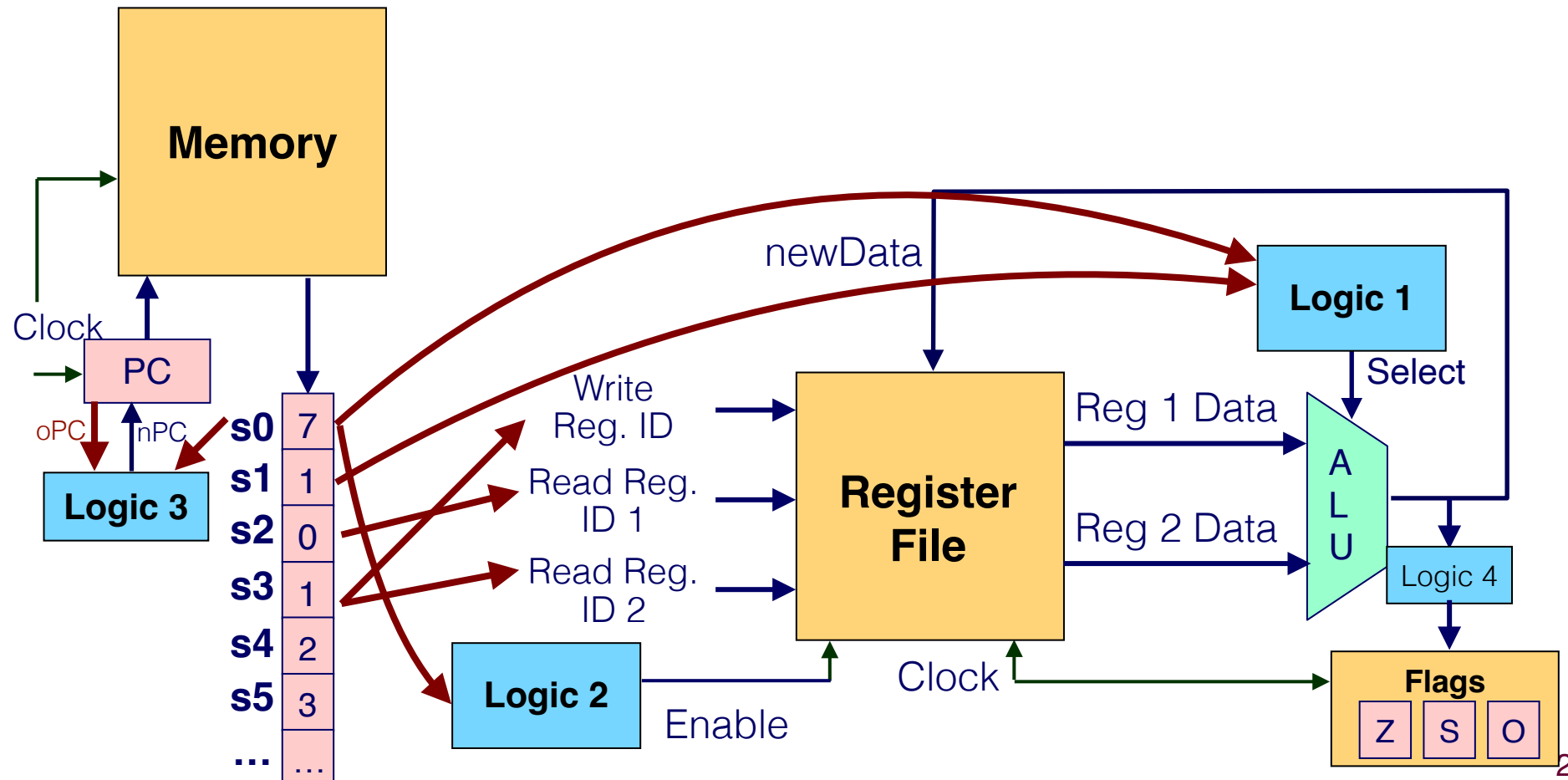
# Executing a JLE instruction

- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;





jle Dest

7


1

Dest

# Executing a JLE instruction

- Logic 3??

if (s0 == 6) nPC = oPC + 2;

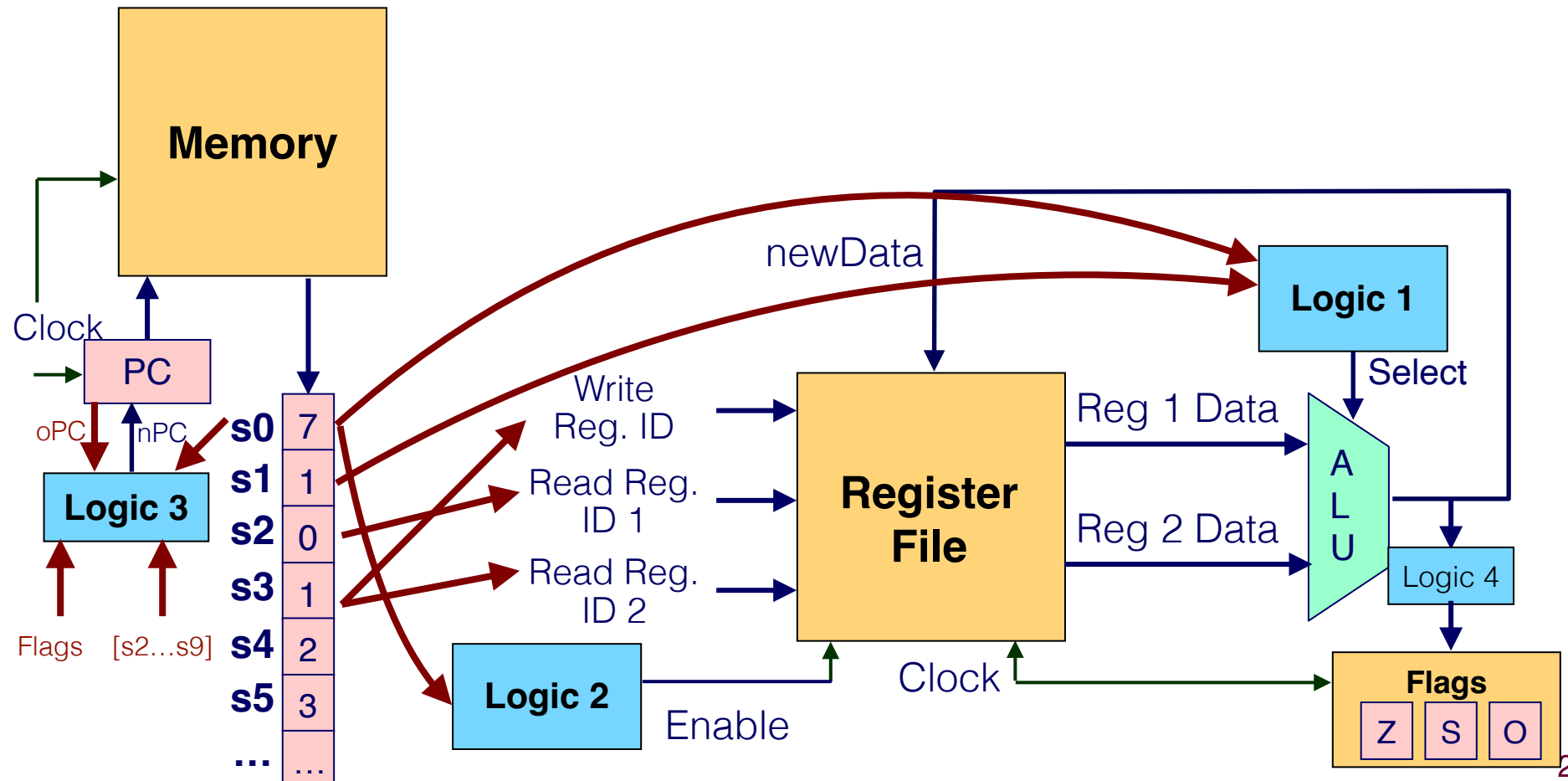

jle Dest


7 1

Dest

# Executing a JLE instruction


- Logic 3??

```
if (s0 == 6) nPC = oPC + 2;  
else if (s0 == 7) {  
  if (s1 == 1) { // jLE  
    if (Z || (S ^ O)) nPC = Dest; // jump  
    else nPC = oPC + 10; // don't jump, but add 10 (why??)  
  } else if (s1 == ...) {...}  
}
```

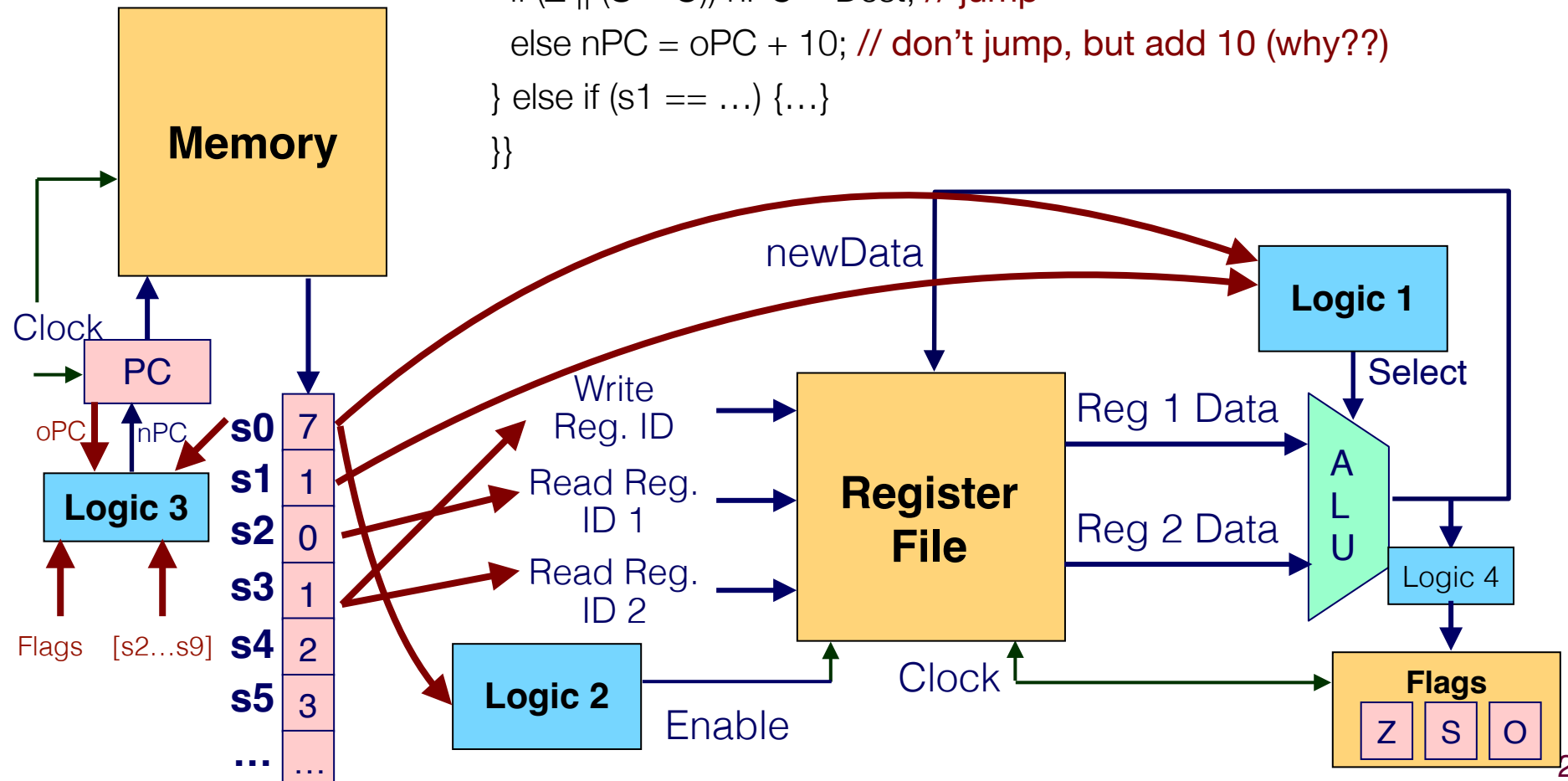
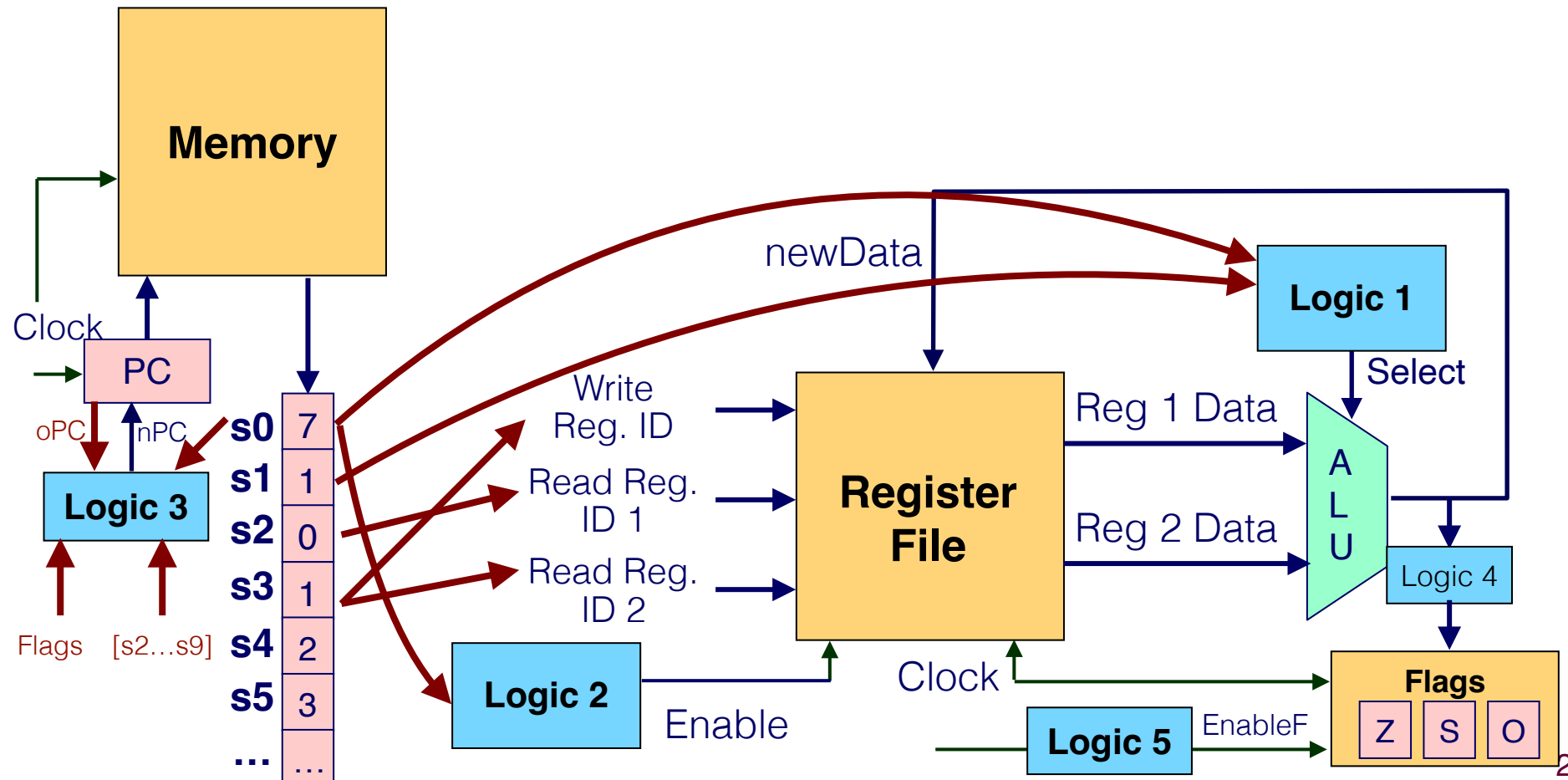
# Executing a JLE instruction

- Logic 4? Does JLE write flags?
- Need another piece of logic.
- Logic 5: if (s0 == 7) EnableF = 0; else if (s0 == 6) EnableF = 1;



# Microarchitecture (So far)

