

CSC 252: Computer Organization

Spring 2018: Lecture 10

Instructor: Yuhao Zhu

Department of Computer Science
University of Rochester

Action Items:


- **Trivia 3 was just due**
- **Assignment 3 is due March 2, midnight**

Announcement


- Programming Assignment 3 is out
 - Due on **March 2, midnight**

18	19	20	21	22	23	24
25	26	27	28	Mar 1	2	3


due



So far in 252...

 


So far in 252...

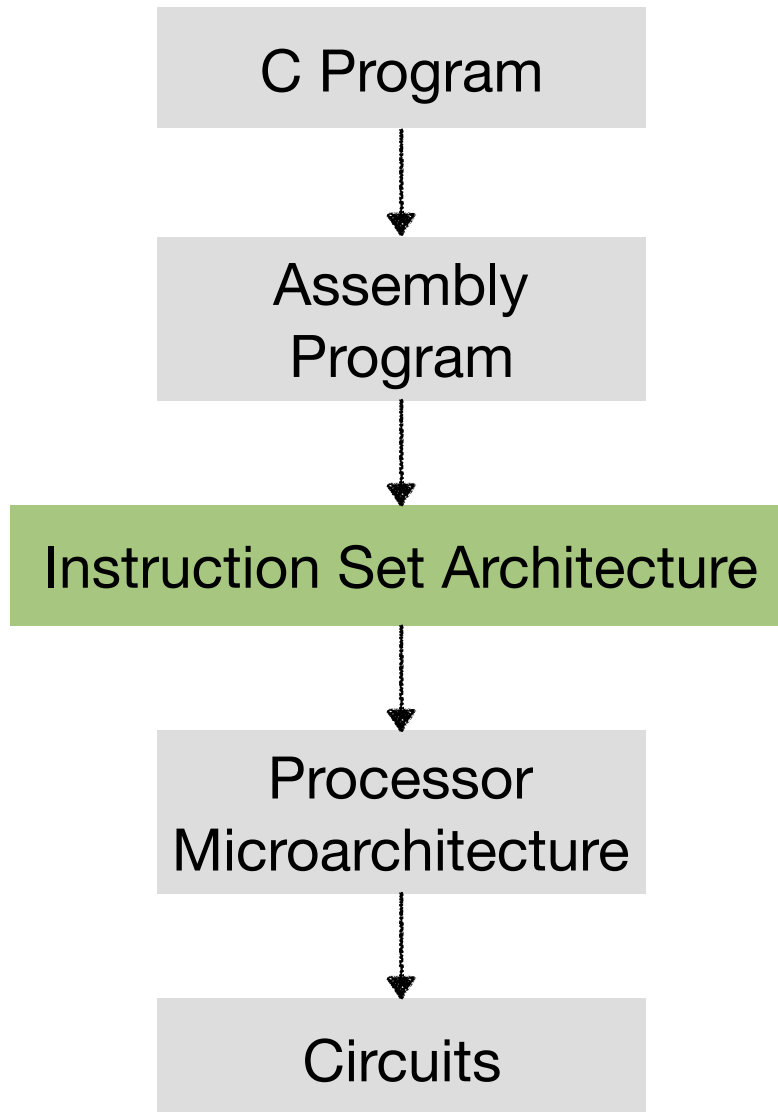

```
ret, call  
movq, addq  
jmp, jne
```


So far in 252...

 

```
movq    %rsi, %rax
imulq   %rdx, %rax
jmp     .done
```

```
ret, call
movq, addq
jmp, jne
```

So far in 252...

 


```
int, float  
if, else  
+, -, >>
```

```
movq    %rsi, %rax  
imulq   %rdx, %rax  
jmp     .done
```

```
ret, call  
movq, addq  
jmp, jne
```

So far in 252...

 

int, float
if, else
+, -, >>


```
movq    %rsi, %rax  
imulq   %rdx, %rax  
jmp     .done
```

```
ret, call  
movq, addq  
jmp, jne
```

???

???

So far in 252...

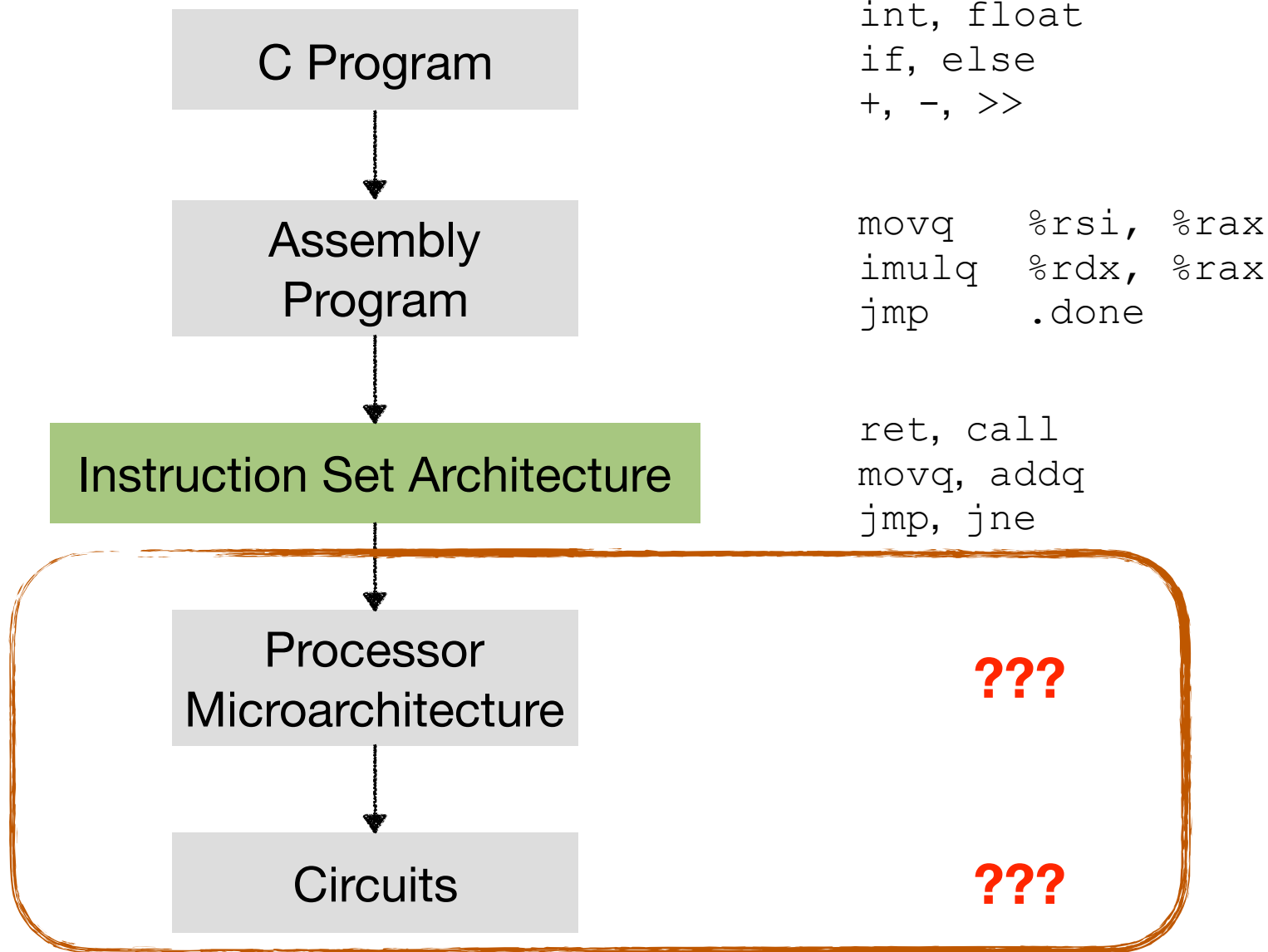


Today: Circuits Basics

- Transistors
- Circuits for computations
- Circuits for storing data

Overview of Circuit-Level Design

- Fundamental Hardware Requirements
 - Communication: How to get values from one place to another. Mainly three electrical **wires**.
 - Computation: **transistors**. Combinational logic.
 - Storage: **transistors**. Sequential logic.
- Bits are Our Friends: Everything expressed in 0s and 1s
 - Communication: Low or high voltage on wire
 - Computation: Compute Boolean functions
 - Storage: Store bits of information
- Circuit design is often abstracted as **logic design**

Digital Signals

 

- Extract discrete values from continuous voltage signal
- Simplest version: 1-bit signal
 - Either high range (1) or low range (0)
 - With guard range between them
- Not strongly affected by noise or low quality circuit elements
 - Can make circuits simple, small, and fast

Basic Building Block: Transistors

Basic Building Block: Transistors

MOS = Metal Oxide Semiconductor


- two types: n-type and p-type

Basic Building Block: Transistors

MOS = Metal Oxide Semiconductor

- two types: n-type and p-type

n-type (NMOS)

 

Terminal #2 must be connected to GND (0V).


Basic Building Block: Transistors

MOS = Metal Oxide Semiconductor

- two types: n-type and p-type

n-type (NMOS)

 - when Gate has positive voltage, short circuit between #1 and #2 (switch closed)



Terminal #2 must be connected to GND (0V).


Basic Building Block: Transistors

MOS = Metal Oxide Semiconductor

- two types: n-type and p-type

n-type (NMOS)

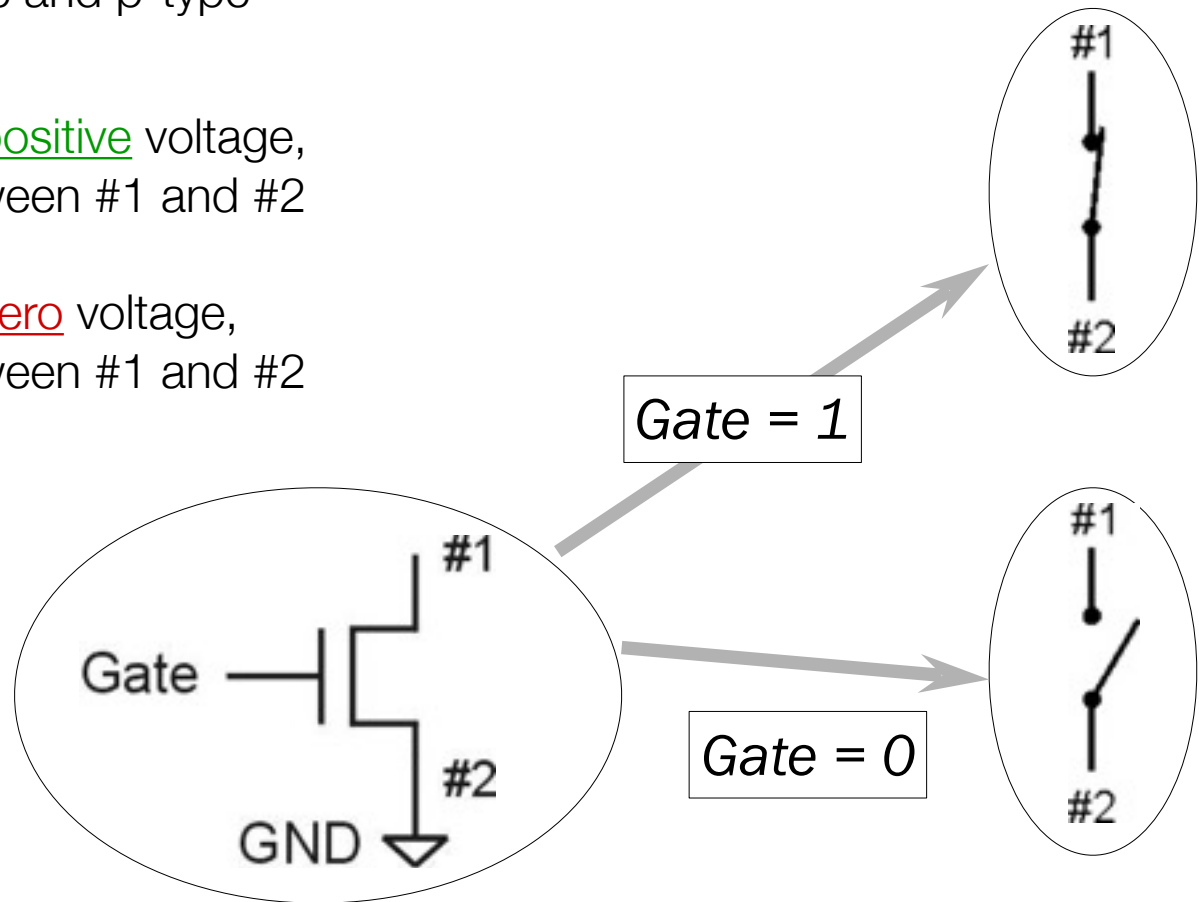- when Gate has positive voltage, short circuit between #1 and #2 (switch closed)
- when Gate has zero voltage, open circuit between #1 and #2 (switch open)




Terminal #2 must be connected to GND (0V).

Basic Building Block: Transistors

p-type is *complementary* to n-type (**PMOS**)

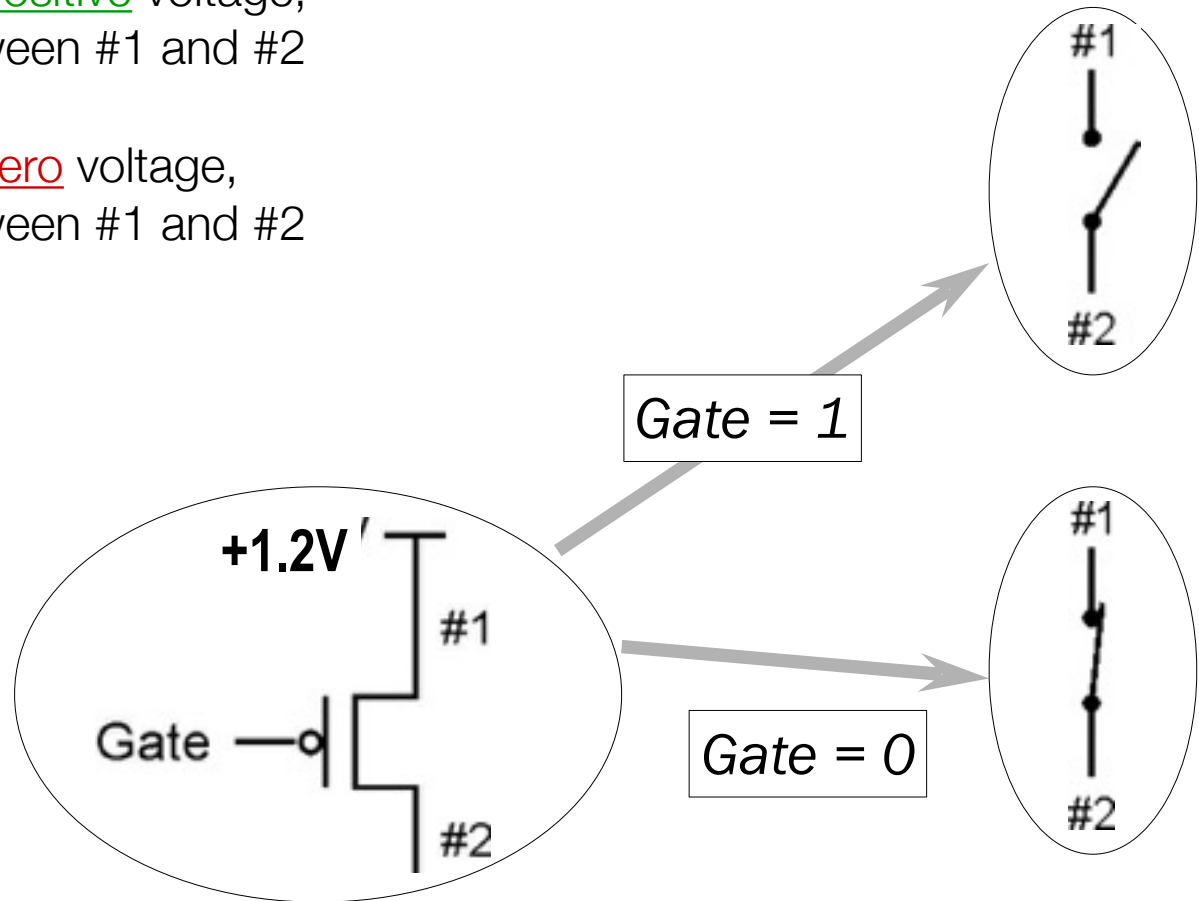- when Gate has positive voltage, open circuit between #1 and #2 (switch open)
- when Gate has zero voltage, short circuit between #1 and #2 (switch closed)




Terminal #1 must be connected to +1.2V


CMOS Circuit

- Complementary MOS
- Uses both n-type and p-type MOS transistors
 - p-type
 - Attached to + voltage
 - Pulls output voltage UP when input is zero
 - n-type
 - Attached to GND
 - Pulls output voltage DOWN when input is one


Inverter (NOT Gate)

 



Inverter (NOT Gate)

 




Inverter (NOT Gate)

 


Inverter (NOT Gate)

  



Inverter (NOT Gate)

   



Inverter (NOT Gate)

 

In	Out
0	1
1	0

  


NOR Gate (NOT + OR)

  


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Note: Serial structure on top, parallel on bottom.


Basic Logic Gates

 


NOT

 


OR

 

NOR

 

AND

 


NAND

Today: Circuits Basics

- Transistors
- Circuits for computations
- Circuits for storing data


Computing with Logic Gates

And

 


$$\text{out} = a \ \&\& \ b$$

Or

 


$$\text{out} = a \ || \ b$$

Not

 


$$\text{out} = !a$$

 
- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs with some small delay




Computing with Logic Gates

 

 
- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs with some small delay




Computing with Logic Gates

 

 
- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs with some small delay




Computing with Logic Gates

 

 - Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs with some small delay



Combinational Circuits

 

- A Network of Logic Gates


- Continuously responds to changes on primary inputs
- Primary outputs become (after some delay) Boolean functions of primary inputs

Bit Equality

```
bool eq = (a&&b) || (!a&&!b)
```


Bit Equality

```
bool eq = (a&&b) || (!a&&!b)
```

 


Bit Equality

```
bool eq = (a&&b) || (!a&&!b)
```

 


Bit Equality

```
bool eq = (a&&b) || (!a&&!b)
```

 


Bit Equality

```
bool eq = (a&&b) || (!a&&!b)
```

 


Bit Equality

```
bool eq = (a&&b) || (!a&&!b)
```

 


Bit Equality

```
bool eq = (a&&b) || (!a&&!b)
```

 


Bit Equality

```
bool eq = (a&&b) || (!a&&!b)
```

 

Bit Equality


```
bool eq = (a&&b) || (!a&&!b)
```

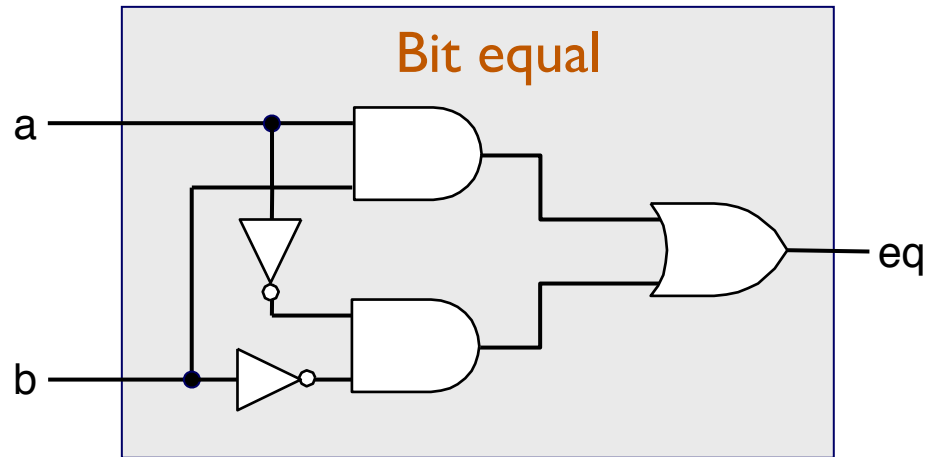

Bit Equality


HCL Expression

```
bool eq = (a&&b) || (!a&&!b)
```

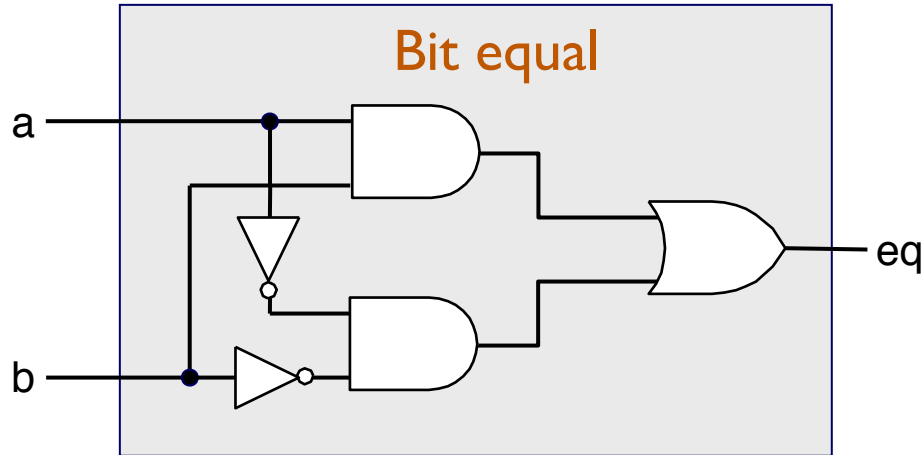


- Hardware Control Language (HCL)
 - Very simple hardware description language
 - Boolean operations have syntax similar to C logical operations
 - We'll use it to describe control logic for processors

Word Equality

 

Word-Level Representation

 

HCL Representation

```
bool Eq = (A == B)
```

Bit-Level Multiplexor (MUX)

- Control signal s
- Data signals a and b
- Output a when $s=1$, b when $s=0$

Bit-Level Multiplexor (MUX)

- Control signal s
- Data signals a and b
- Output a when $s=1$, b when $s=0$

HCL Expression


```
bool out = (s&&a) || (!s&&b)
```

Bit-Level Multiplexor (MUX)


- Control signal s
- Data signals a and b
- Output a when $s=1$, b when $s=0$

HCL Expression


```
bool out = (s&&a) || (!s&&b)
```

 

Word Multiplexor

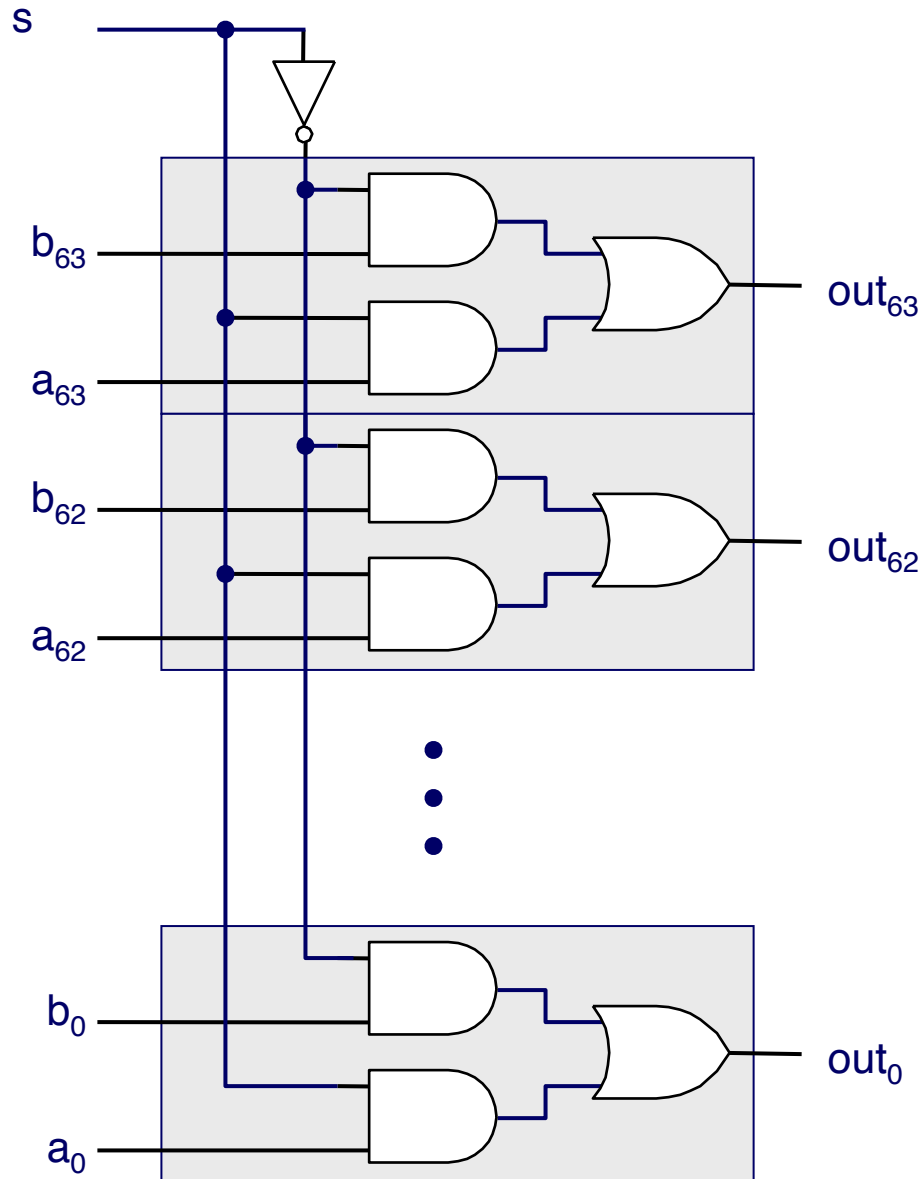

Word-Level Representation

 

HCL Representation

```
int Out = [  
    s : A;  
    1 : B;  
];
```

- Select input word A or B depending on control signal s
- HCL representation
 - Case expression
 - Series of test : value pairs
 - Output value for first successful test

Full (1-bit) Adder

Add two bits and carry-in,
produce one-bit sum and carry-out.

A	B	C_{in}	S C_{ou} t	
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full (1-bit) Adder

Add two bits and carry-in,
produce one-bit sum and carry-out.

$$S = (\sim A \ \& \ \sim B \ \& \ C_{in})$$

A	B	C _{in}	S	C _{ou}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full (1-bit) Adder

Add two bits and carry-in,
produce one-bit sum and carry-out.

$$S = (\sim A \& \sim B \& C_{in}) \\ | (\sim A \& B \& \sim C_{in})$$

A	B	C _{in}	S	C _{ou}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full (1-bit) Adder

Add two bits and carry-in,
produce one-bit sum and carry-out.

$$\begin{aligned} S = & (\sim A \ \& \ \sim B \ \& \ C_{in}) \\ & | (\sim A \ \& \ B \ \& \ \sim C_{in}) \\ & | (A \ \& \ \sim B \ \& \ \sim C_{in}) \end{aligned}$$

A	B	C _{in}	S	C _{ou}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full (1-bit) Adder

Add two bits and carry-in,
produce one-bit sum and carry-out.

$$\begin{aligned} S = & (\sim A \ \& \ \sim B \ \& \ C_{in}) \\ & | (\sim A \ \& \ B \ \& \ \sim C_{in}) \\ & | (A \ \& \ \sim B \ \& \ \sim C_{in}) \\ & | (A \ \& \ B \ \& \ C_{in}) \end{aligned}$$

A	B	C _{in}	S	C _{ou} t
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full (1-bit) Adder

Add two bits and carry-in,
produce one-bit sum and carry-out.

$$\begin{aligned} S = & (\sim A \ \& \ \sim B \ \& \ C_{in}) \\ & | (\sim A \ \& \ B \ \& \ \sim C_{in}) \\ & | (A \ \& \ \sim B \ \& \ \sim C_{in}) \\ & | (A \ \& \ B \ \& \ C_{in}) \end{aligned}$$

$$\begin{aligned} C_{ou} = & (\sim A \ \& \ B \ \& \ C_{in}) \\ & | (A \ \& \ \sim B \ \& \ C_{in}) \\ & | (A \ \& \ B \ \& \ \sim C_{in}) \\ & | (A \ \& \ B \ \& \ C_{in}) \end{aligned}$$

A	B	C _{in}	S	C _{ou}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full (1-bit) Adder

Add two bits and carry-in,
produce one-bit sum and carry-out.

$$\begin{aligned} C_{ou} = & (\sim A \& B \& C_{in}) \\ & | (A \& \sim B \& C_{in}) \\ & | (A \& B \& \sim C_{in}) \\ & | (A \& B \& C_{in}) \end{aligned}$$

Full (1-bit) Adder


$$C_{ou} = (\sim A \& B \& C_{in})$$

$$| (A \& \sim B \& C_{in})$$

$$| (A \& B \& \sim C_{in})$$

$$| (A \& B \& C_{in})$$

 
Add two bits and carry-in,
produce one-bit sum and carry-out.




Full (1-bit) Adder

$$C_{ou} = (\sim A \& B \& C_{in}) \mid (A \& \sim B \& C_{in}) \mid (A \& B \& \sim C_{in}) \mid (A \& B \& C_{in})$$

 Add two bits and carry-in,
produce one-bit sum and carry-out.




Four-bit Adder

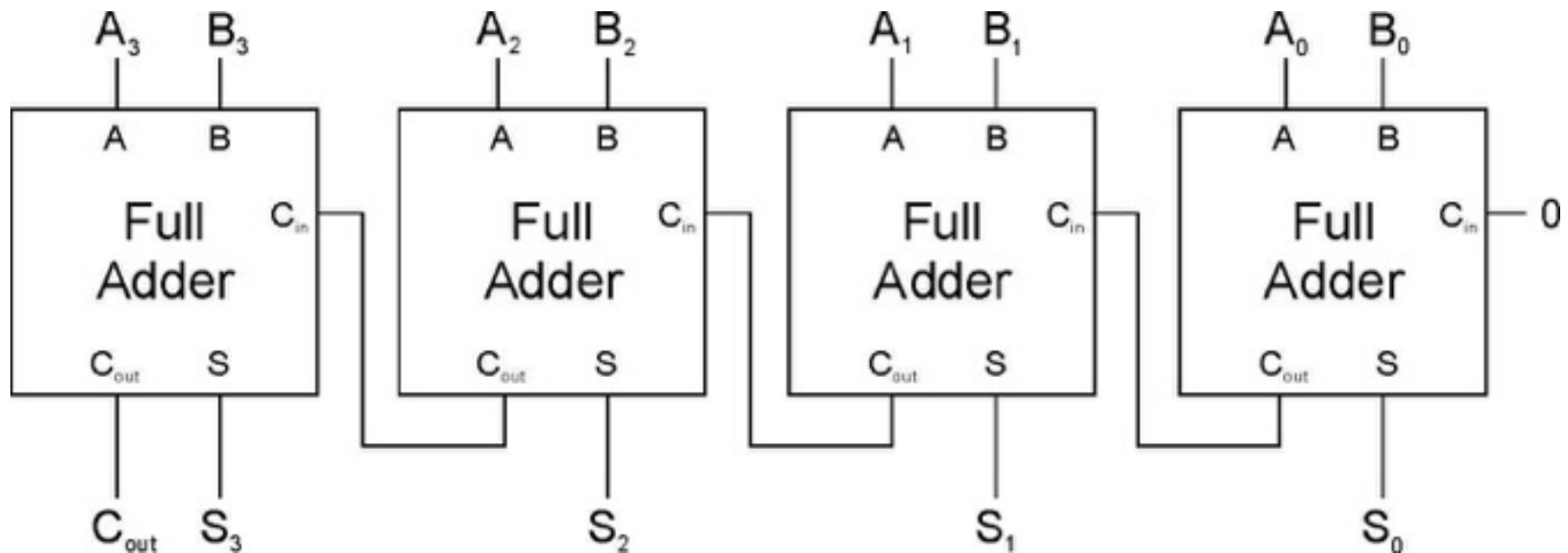


Four-bit Adder

 - Ripple-carry Adder
 - Simple, but performance linear to bit width




Four-bit Adder

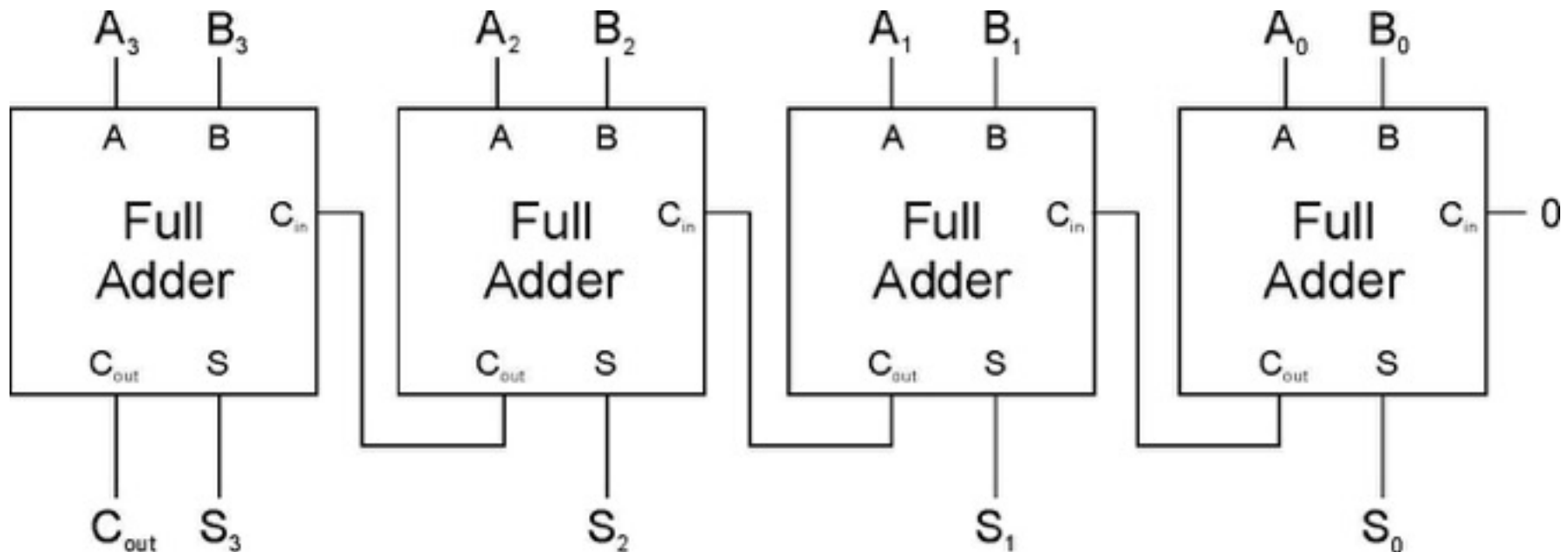- Ripple-carry Adder
 - Simple, but performance linear to bit width
- Carry look-ahead adder (CLA)
 - Generate all carriers simultaneously







Arithmetic Logic Unit

 

- Combinational logic
 - Continuously responding to inputs
- Control signal selects function computed
 - add, subtract, and, or
- Also computes values for condition codes

Arithmetic Logic Unit

Questions?

    


- Combinational logic
 - Continuously responding to inputs
- Control signal selects function computed
 - add, subtract, and, or
- Also computes values for condition codes


Today: Circuits Basics

- Transistors
- Circuits for computations
- Circuits for storing data


Storing 1 Bit

 


Storing 1 Bit

 

Storing 1 Bit

 


Bistable Element

 

Storing and Accessing 1 Bit


Bistable Element

 


$q = 0 \text{ or } 1$

Storing and Accessing 1 Bit

Bistable Element

 


R-S Latch

 


Storing and Accessing 1 Bit


Bistable Element

 

R-S Latch

 


Setting

 


Storing and Accessing 1 Bit


Bistable Element

 


R-S Latch

 

Setting

 


Resetting

 


Storing and Accessing 1 Bit

Bistable Element

 


$q = 0 \text{ or } 1$


R-S Latch

 


Setting

 

Resetting

 


Storing

 


1-Bit D Latch

D Latch

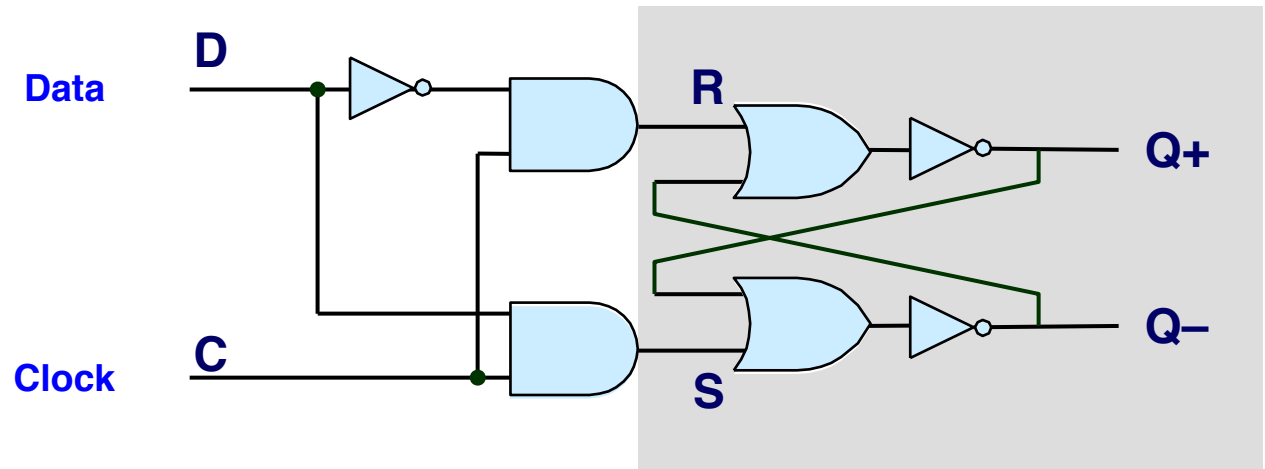


1-Bit D Latch

D Latch

 


Latching

 


1-Bit D Latch


D Latch

 

Latching

 


Storing

 


D-Latch is Transparent (Level-Triggered)

Latching

 


Changing D

 


- When in latching mode, combinational propagation from D to Q+ and Q-
- Value latched depends on value of D as C falls


Edge-Triggered Latch (Flip-Flop)

 


Edge-Triggered Latch (Flip-Flop)

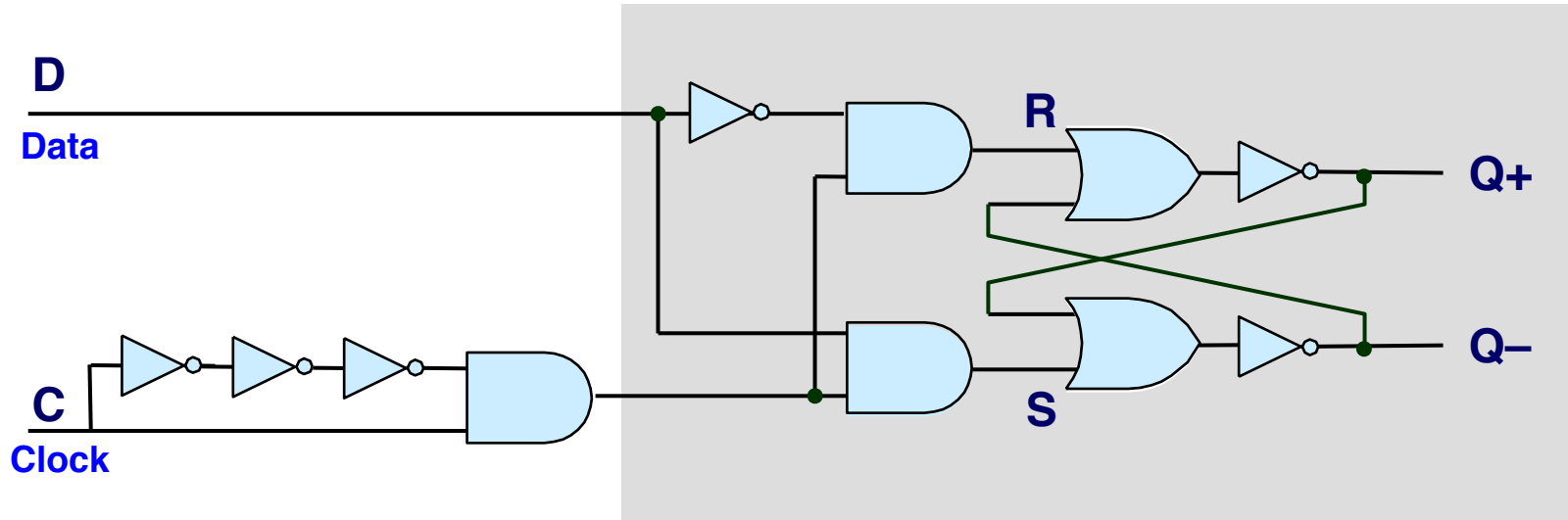


Edge-Triggered Latch (Flip-Flop)

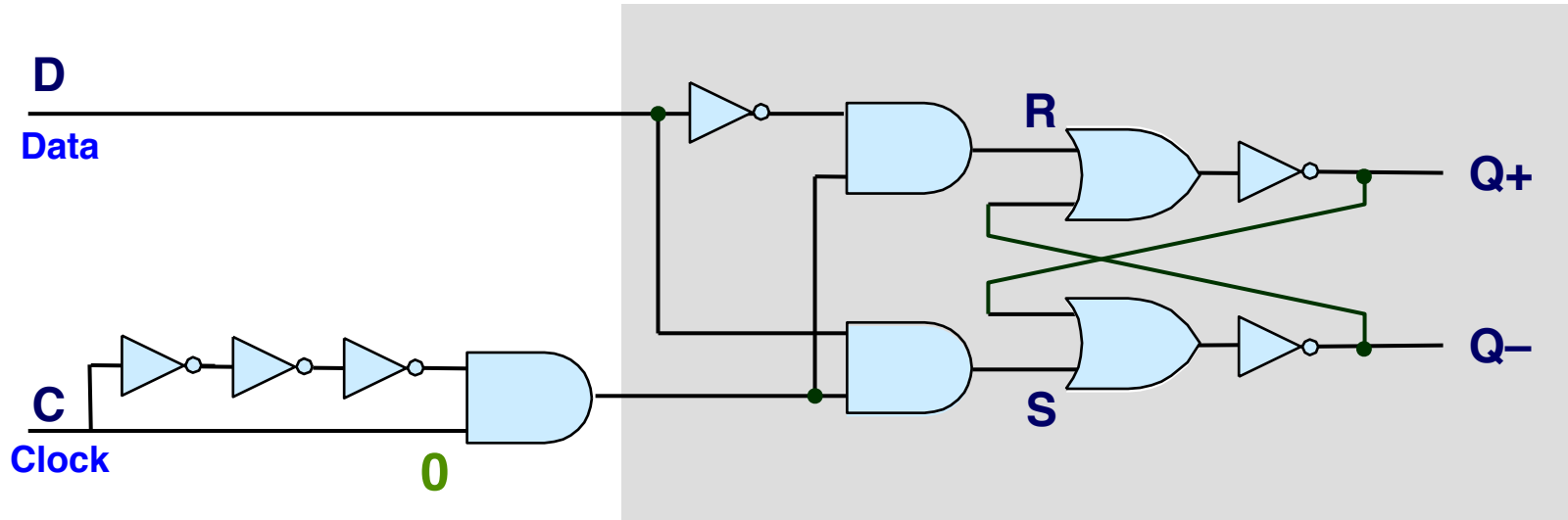


Edge-Triggered Latch (Flip-Flop)

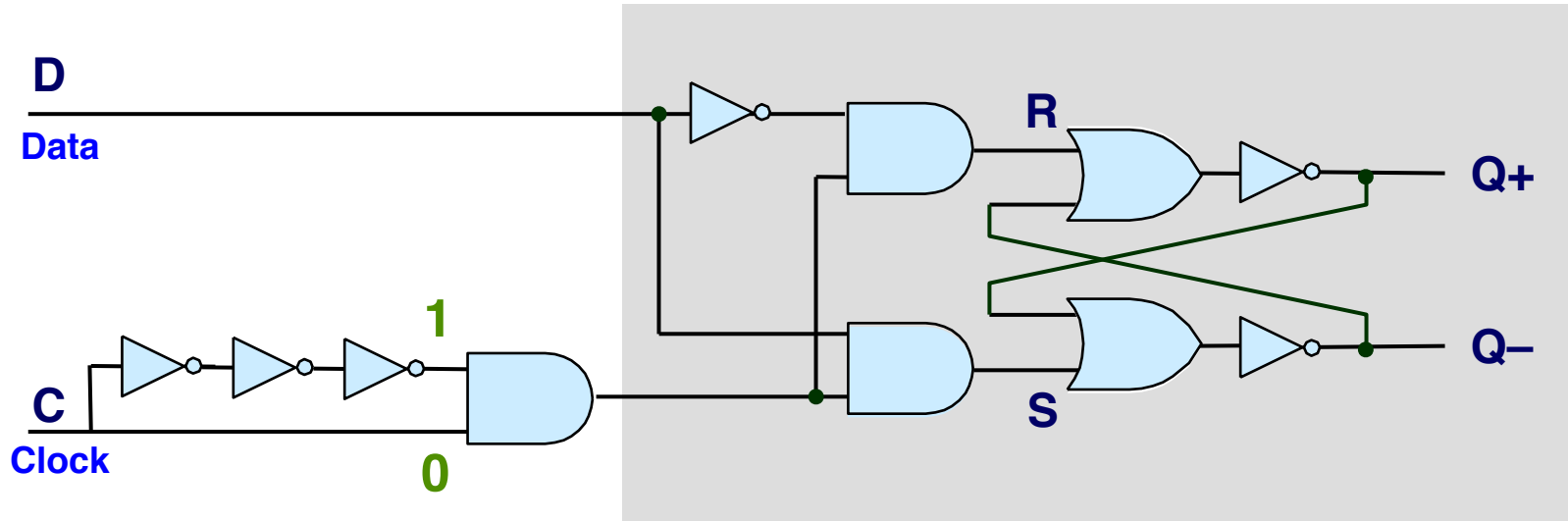


Edge-Triggered Latch (Flip-Flop)

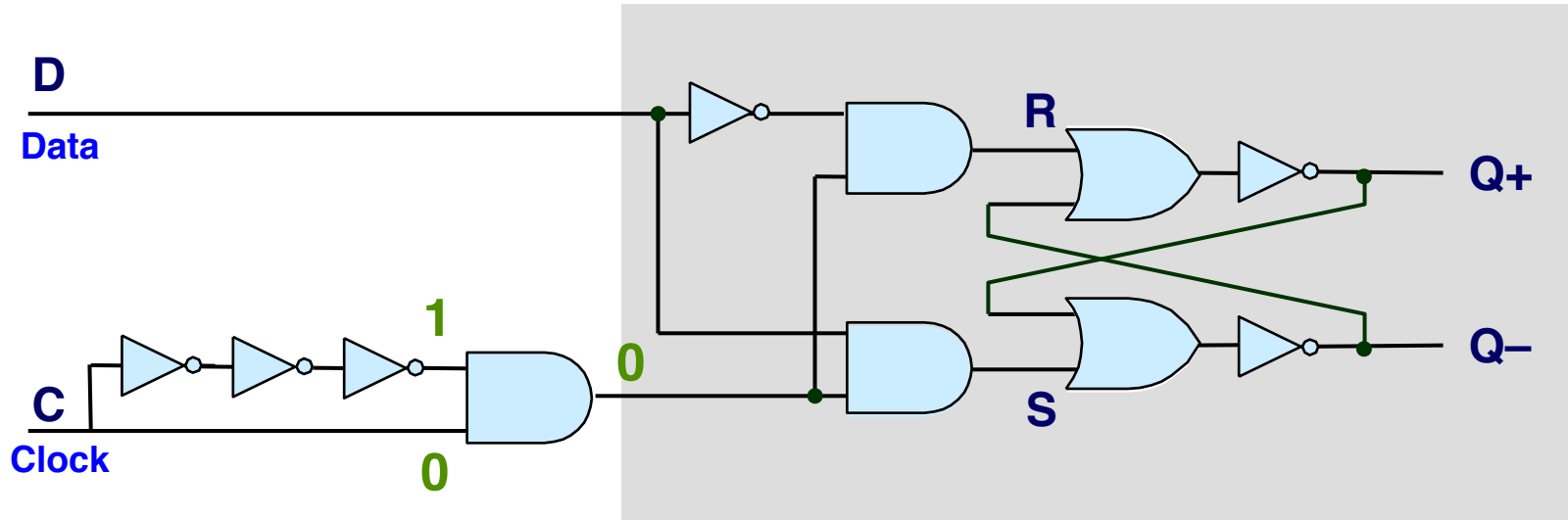


Edge-Triggered Latch (Flip-Flop)

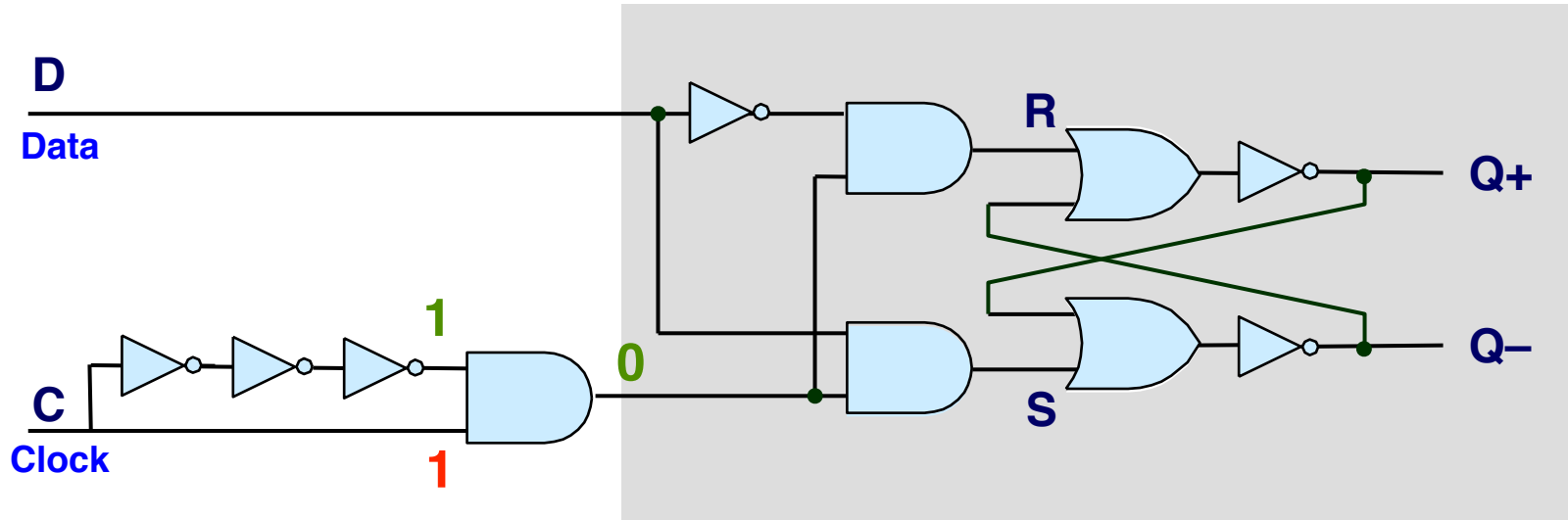


Edge-Triggered Latch (Flip-Flop)

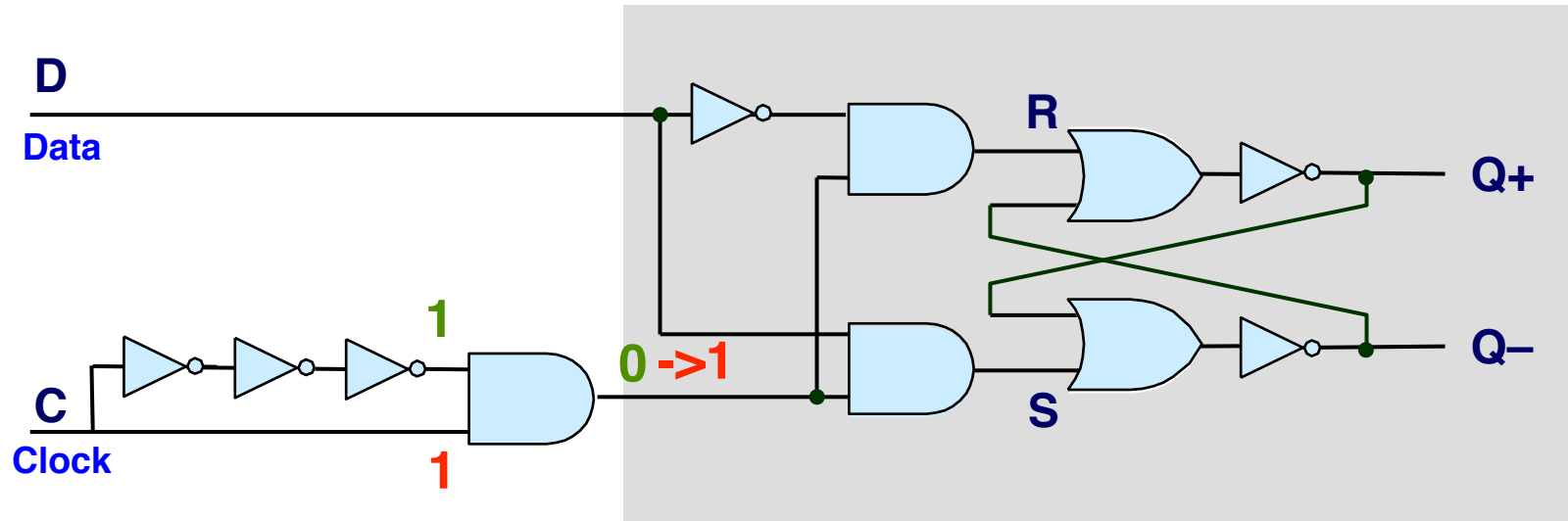



Edge-Triggered Latch (Flip-Flop)

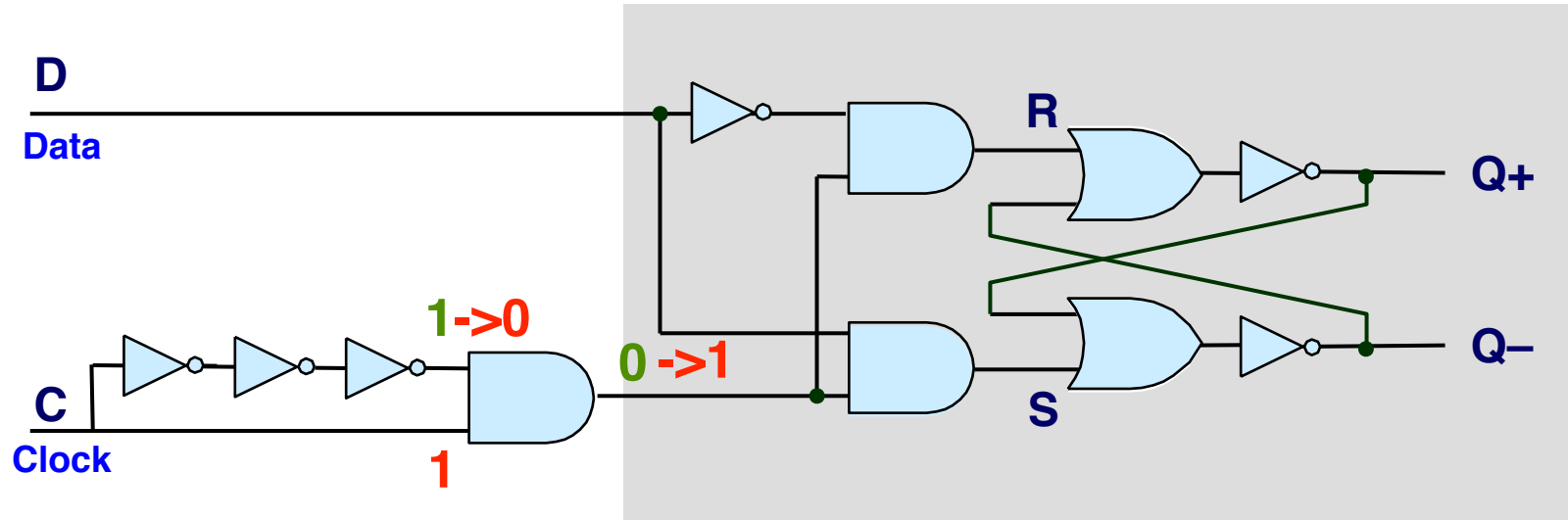



Edge-Triggered Latch (Flip-Flop)

 

Edge-Triggered Latch (Flip-Flop)

 
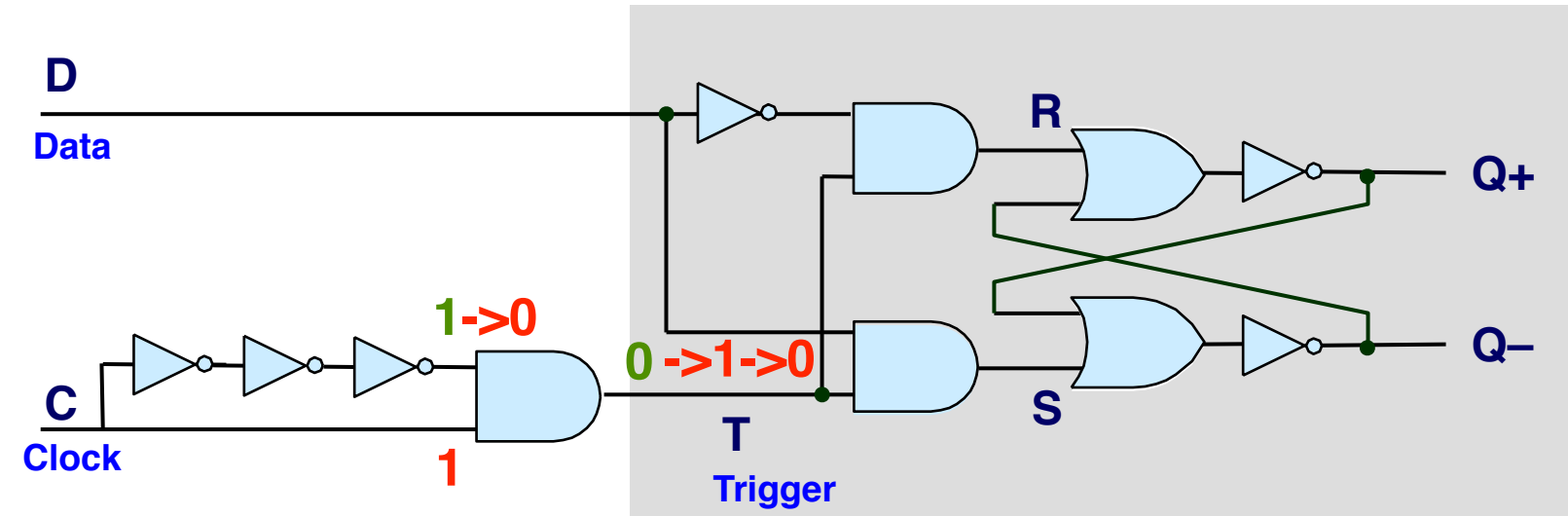


Edge-Triggered Latch (Flip-Flop)

 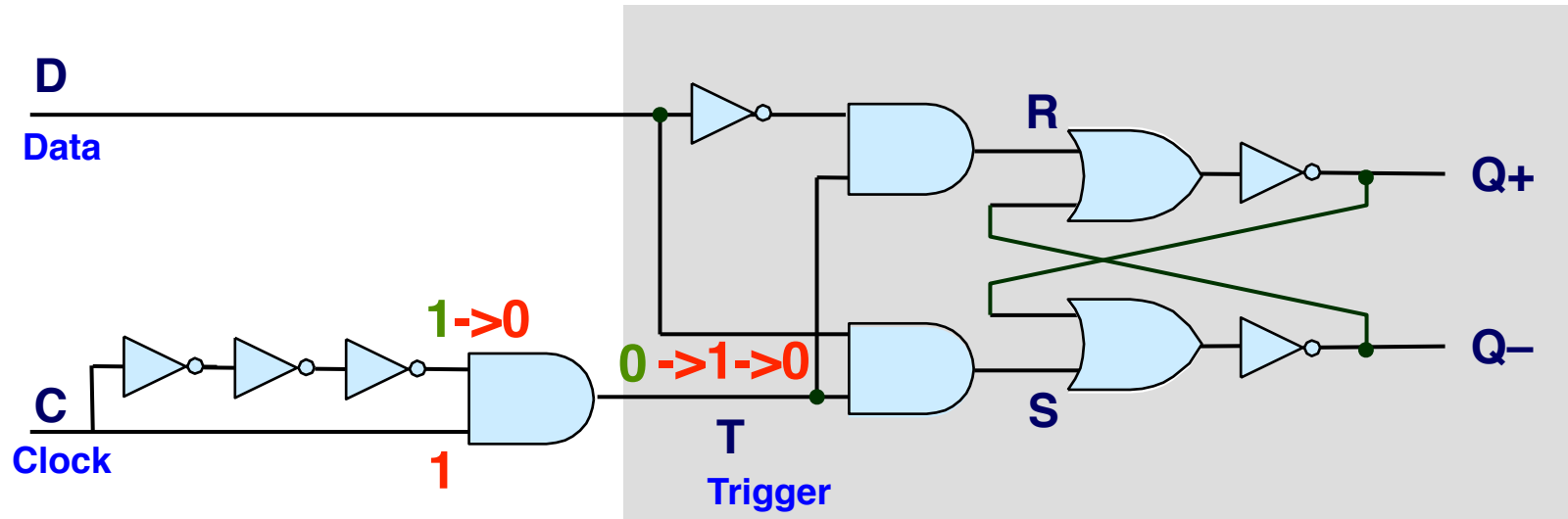


- Flip-flop: Only in latching mode for brief period
- Value latched depends on data as clock rises
- Output remains stable at all other times

Registers

 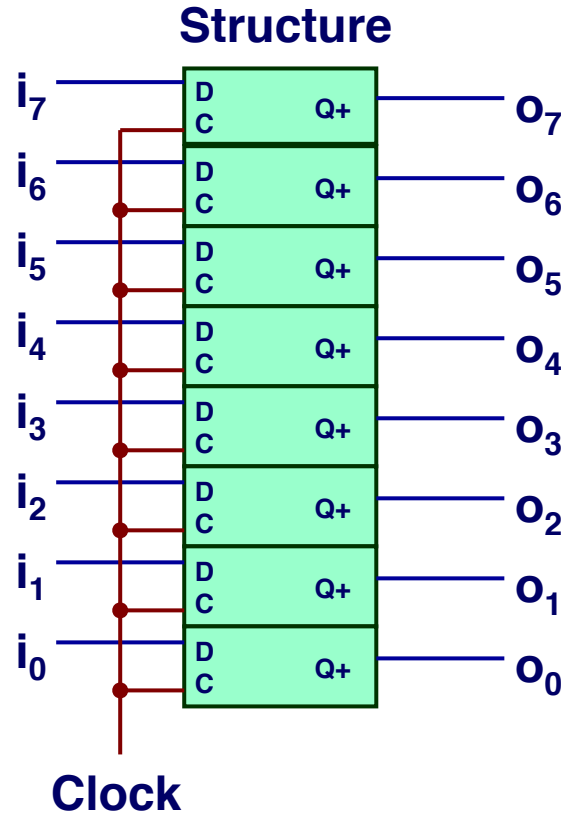


- Stores word of data
- Collection of edge-triggered latches (D Flip-flops)
- Loads input on rising edge of clock


Register Operation

 


Register Operation

 

Register Operation

 

Register Operation

 

- Stores data bits
- For most of time acts as barrier between input and output
- As clock rises, loads input

Decoder

A1	A0	D3	D2	D1	D0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$D0 = \neg A1 \ \& \ \neg A0$$

$$D1 = \neg A1 \ \& \ A0$$

$$D2 = A1 \ \& \ \neg A0$$

$$D3 = A1 \ \& \ A0$$

Decoder


A1	A0	D3	D2	D1	D0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$D0 = \neg A1 \ \& \ \neg A0$$

$$D1 = \neg A1 \ \& \ A0$$


$$D2 = A1 \ \& \ \neg A0$$

$$D3 = A1 \ \& \ A0$$

 

Register File


Register File

 

↑
Clock


Register File

Register File

 


- Stores multiple registers of data
 - Address input specifies which register to read or write

Register File

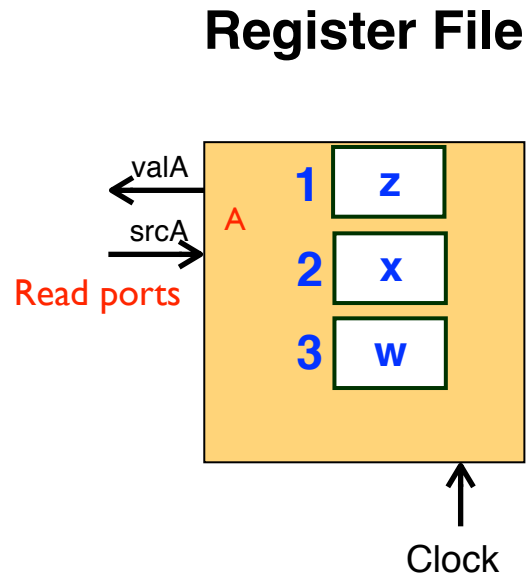


- Stores multiple registers of data
 - Address input specifies which register to read or write

Register File

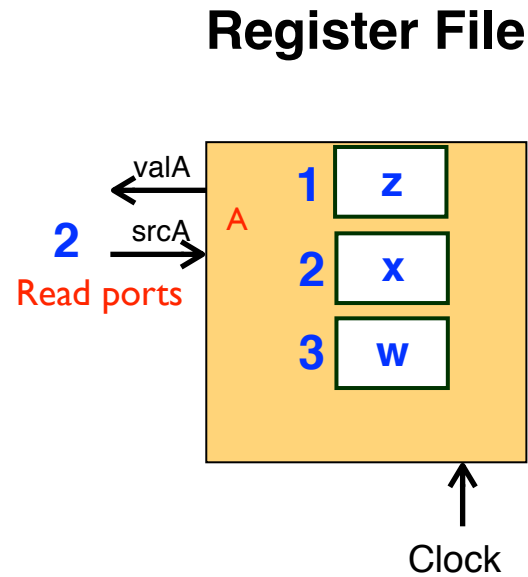


- Stores multiple registers of data
 - Address input specifies which register to read or write

Register File

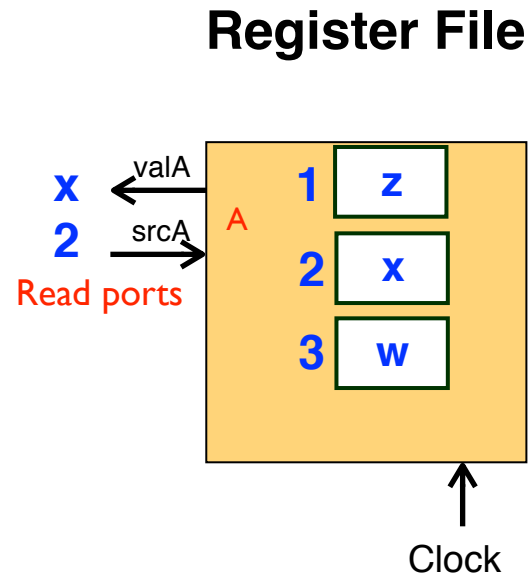


- Stores multiple registers of data
 - Address input specifies which register to read or write

Register File

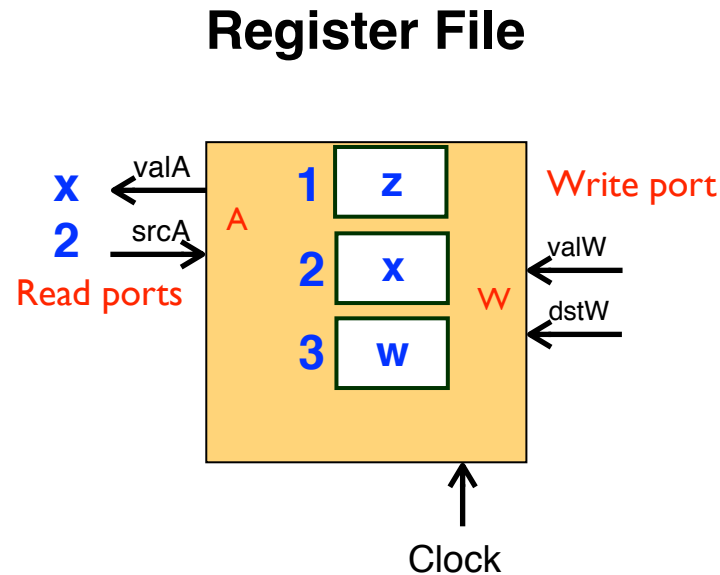


- Stores multiple registers of data
 - Address input specifies which register to read or write

Register File

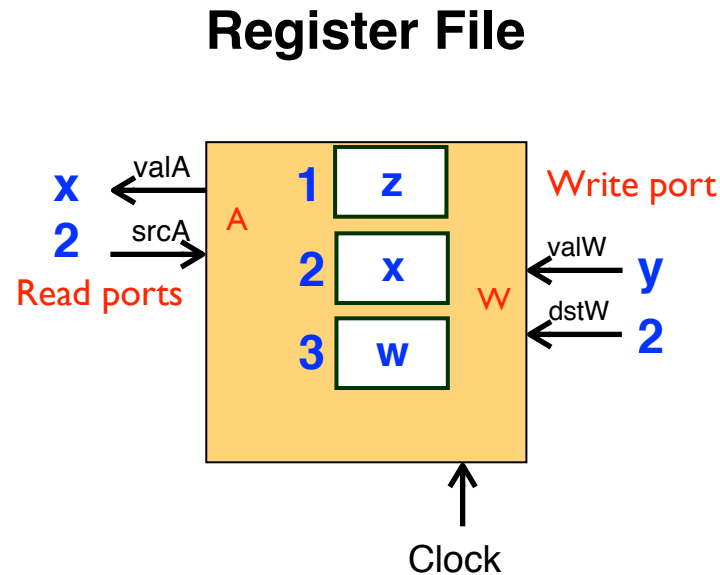


- Stores multiple registers of data
 - Address input specifies which register to read or write

Register File

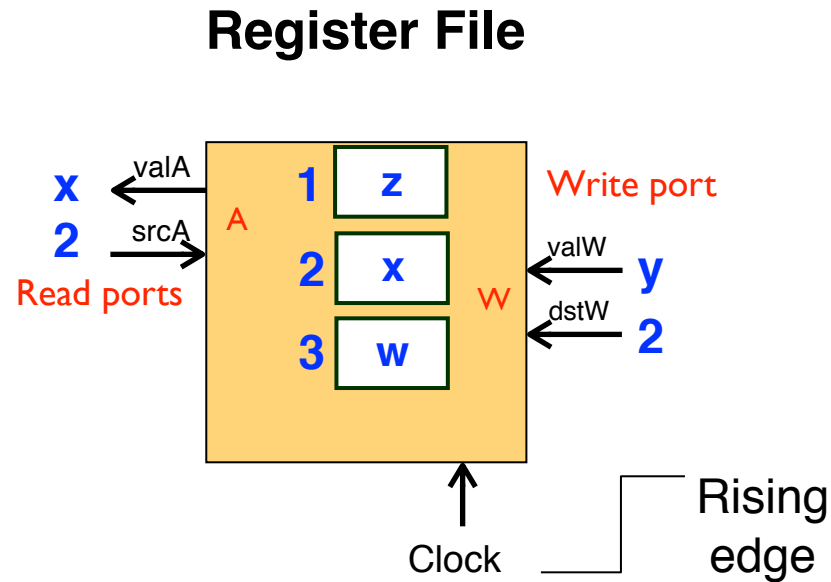


- Stores multiple registers of data
 - Address input specifies which register to read or write

Register File

 


- Stores multiple registers of data
 - Address input specifies which register to read or write

Register File

 


- Stores multiple registers of data
 - Address input specifies which register to read or write
- Register file is a form of **Random-Access Memory (RAM)**

Register File

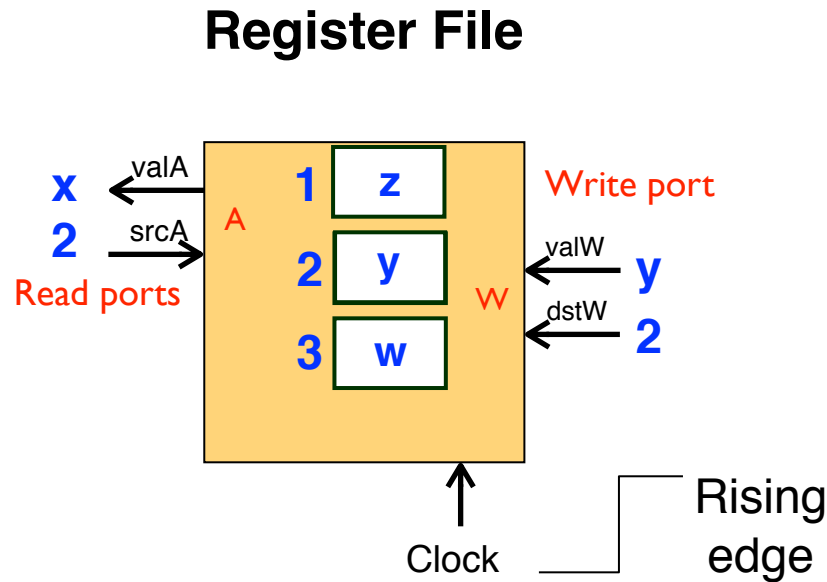


- Stores multiple registers of data
 - Address input specifies which register to read or write
- Register file is a form of **Random-Access Memory (RAM)**
- Multiple Ports: Can read and/or write multiple words in one cycle. Each port has separate address and data input/output

Register File

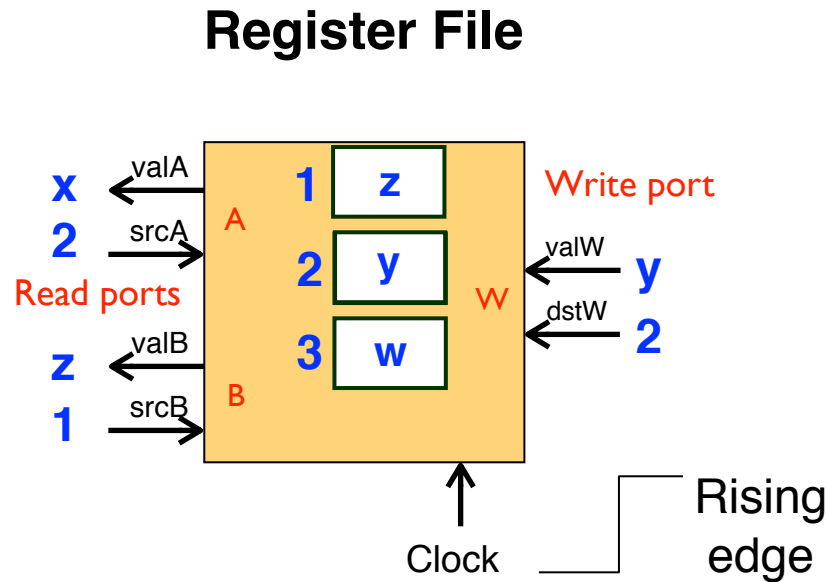


- Stores multiple registers of data
 - Address input specifies which register to read or write
- Register file is a form of **Random-Access Memory (RAM)**
- Multiple Ports: Can read and/or write multiple words in one cycle. Each port has separate address and data input/output


Register File Implementation

 


Register File Implementation

 


Register File Implementation

 


Register File Implementation

 

Register File Implementation

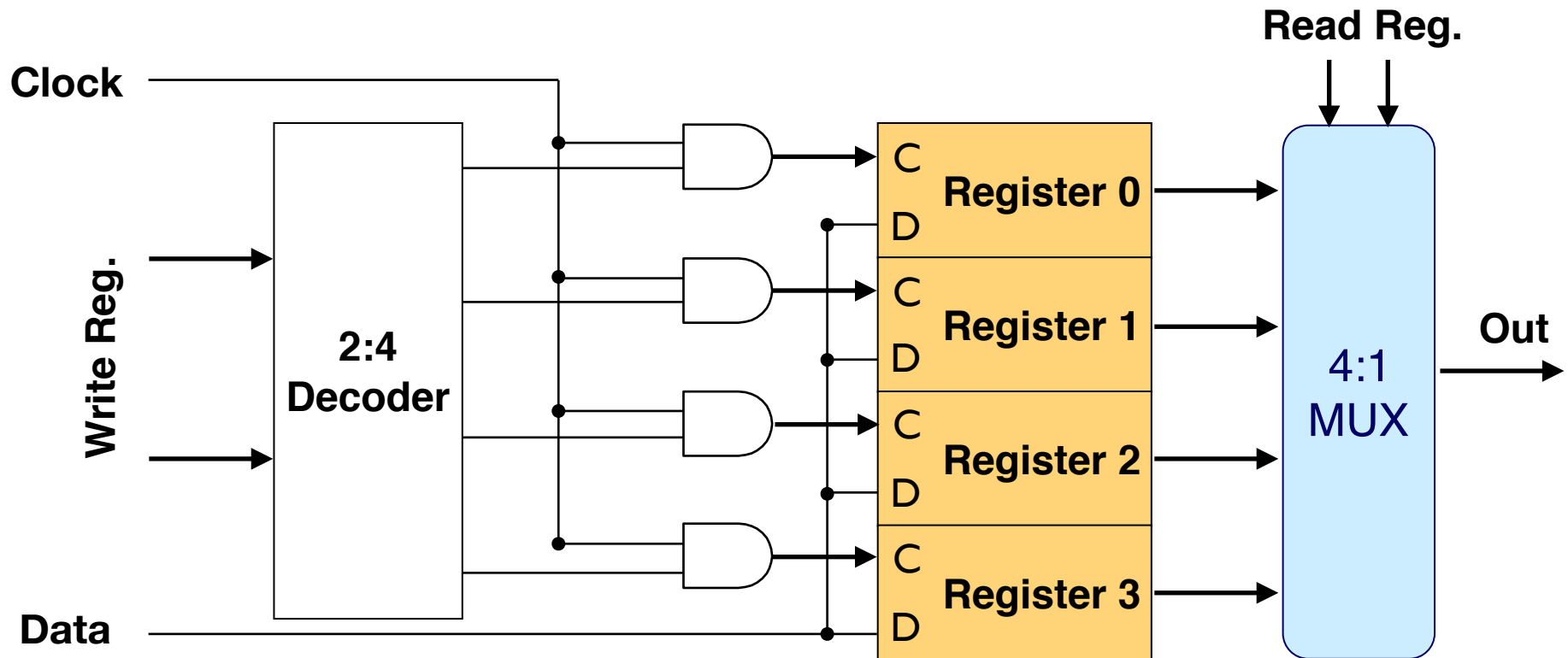


Putting It Together: Accumulator Example

 

- Accumulator circuit
- Load or accumulate on each cycle

Putting It Together: Accumulator Example

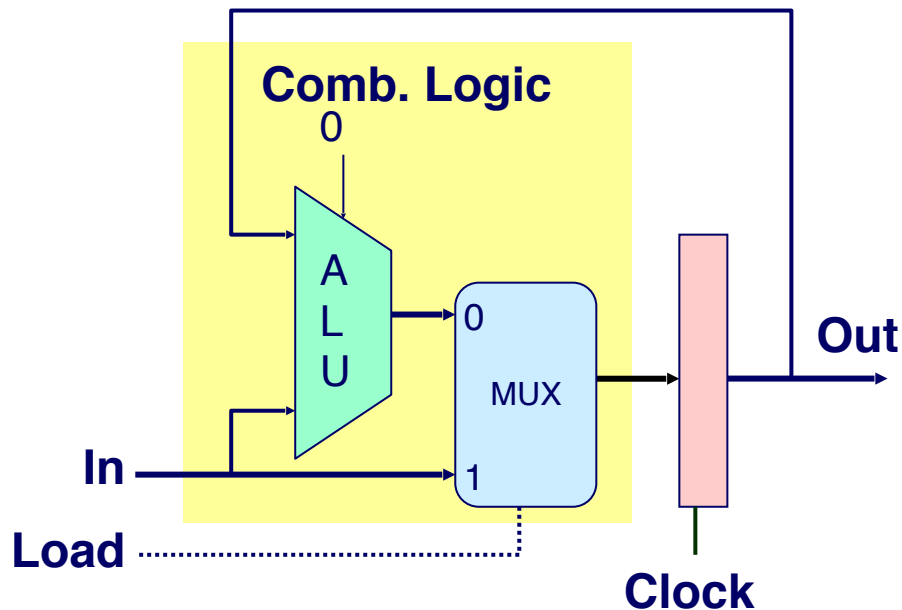

- Accumulator circuit
- Load or accumulate on each cycle

